

# 6.S188

Build a Digital Clock from the Eighties

Lecture 1A

# Overview of Class

- **6.S188 Build a Digital Clock from the Eighties**
- Level: U
- Units: 1-0-2...PNR credit as far as I understand it
- Prereqs: none
- Class Website: **eightiesclock.mit.edu**
- Instructor:
  - Adam Hartz ([hartz@mit.edu](mailto:hartz@mit.edu))
  - Joe Steinmeyer ([jodalyst@mit.edu](mailto:jodalyst@mit.edu))
- Schedule: January 5 – January 30
  - Lecture: Tuesdays & Thursdays, 11:00-12:30, room 34-301
  - Open Lab hours: Lab open every weekday 9am-5pm
  - Office hours: See calendar on front page of class, room 38-630


# Schedule/ “Syllabus”

- Two lectures every week and a lab or two where you build something.
- Outline:
  - Week 1:
    - Lecture 1A: Origins of Digital Logic
    - Lab 1A: Relay Logic
    - Lecture 1B: Logic Theory and Design
    - Lab 1B: Diode, Transistor Logic, ICs
  - Week 2:
    - Lecture 2A: Combinational Logic
    - Lab 2A: Adder
    - Lecture 2B: Stateful Logic
    - Lab 2B: Counter
  - Week 3:
    - Lecture 3A: Clocks
    - Lab 3A: Digital Clocks (oscillators) and few other things
    - Lab 3B: Start Building Actual Digital Clock From the Eighties
  - Week 4: Continue/Finish Building Clock From the Eighties
    - Build Digital Clock From the Eighties
    - Build Digital Clock From the Eighties
- No Psets, just do the labs, build the stuff
- No Exams

*This is a fresh class.  
Never run before.  
It is going to be a mess.*
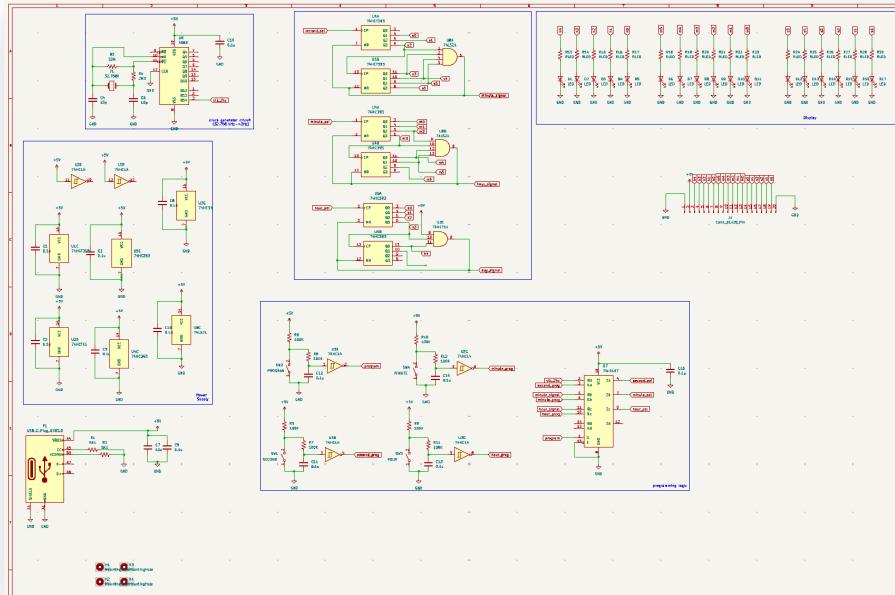
# “Digital Clock From Eighties”?

- Make a Clock that Displays the Time in Binary




We'll build up to this

You wanna make it more complicated, be our guest, but we'll have PCB blanks of one or two version if you want to build that way


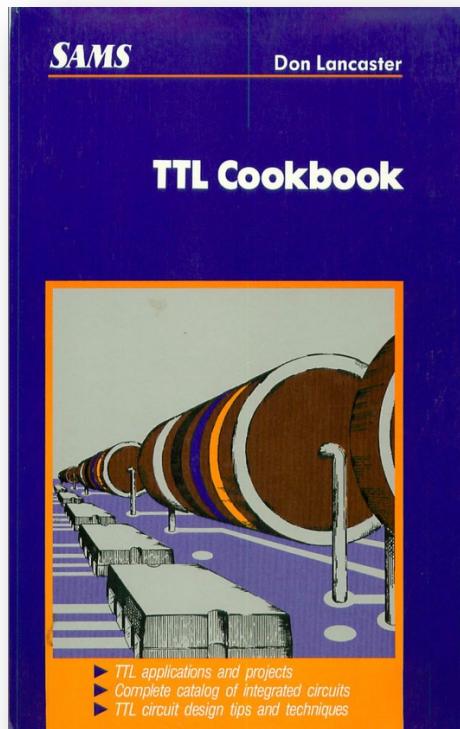
# EECS Evolves Quickly...

- So quickly it is hard to say this is “eighties” or “seventies” clock...it is kinda wrong...



One of texts we'll use as reference

*Author reflecting on changes in field from 1972 to 1982....*

What has changed explosively, though—in case you have been asleep for the last five years—is the microprocessor revolution. Very simply and very bluntly, if it is electronic and doesn't have a microprocessor in it, it is not worth doing. And that applies to ALL electronics, radio, radar, television, communications, power control, hi-fi, video disks and recorders, appliances, cameras, pagers, satellite receivers, data acquisition, process controls. Everything electronic. You name it.

Very few people are dumb enough to still go out and design an electronic something by taking a bushel basket of TTL or other general purpose logic family and then hand-wiring everything together. Today you do everything you can with changeable software, making any remaining hardware very general and flexible.

Don Lancaster  
January, 1982


*What we're doing*

# Why Do This?

- Iunno we thought it would be fun and a way to “touch some grass” in the field of EECS.
- Designs are so ridiculously complicated at this point that in day-to-day or year-to-year it can be very hard to have a sense of what is actually happening....
  - Send the build up to Vivado or to Cadence or whatever and stuff comes back...maybe it works.
- Why not start at ground up?

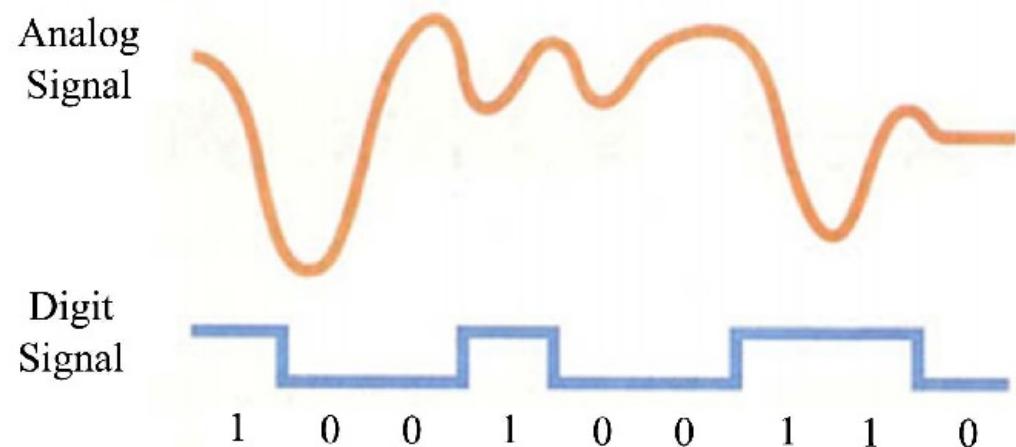
# Digital Electronics

- Thinking of electrical voltages not as continuous signals that can be one of many values (analog)...instead classify all voltages into one of two values.
- It is a choice and it makes designing fundamental units easier


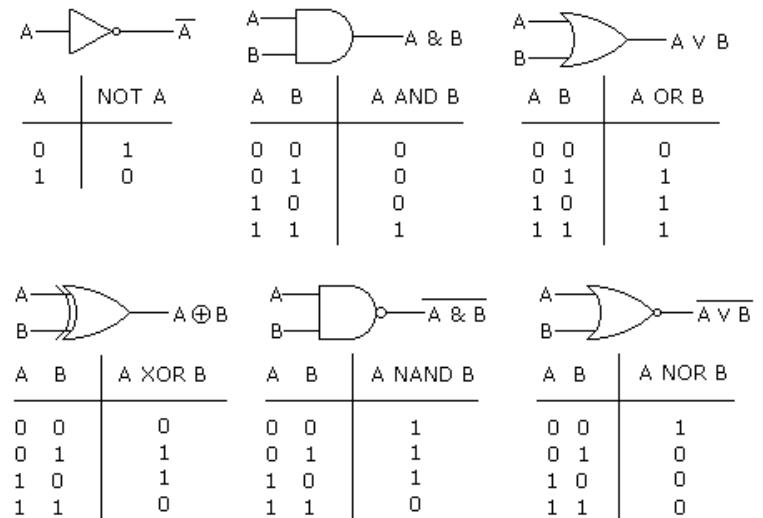
# Simpler worldview...

- Leads to simpler set of foundational circuits.
- These are usually very easy to build and make work reliably.
- This allows us to scale their production massively and make up for (and surpass) the initial limitations of classifying things as 0's and 1's.



The figure displays seven logic gates with their corresponding truth tables:

- NOT**: Input A, Output  $\bar{A}$ . Truth table:

A	NOT A
0	1
1	0
- AND**: Inputs A, B, Output  $A \text{ AND } B$ . Truth table:

A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1
- OR**: Inputs A, B, Output  $A \text{ OR } B$ . Truth table:

A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1
- XOR**: Inputs A, B, Output  $A \oplus B$ . Truth table:

A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0
- NAND**: Inputs A, B, Output  $\bar{A} \text{ AND } \bar{B}$ . Truth table:

A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0
- NOR**: Inputs A, B, Output  $\bar{A} \text{ OR } \bar{B}$ . Truth table:

A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0
- NOT AND**: Inputs A, B, Output  $\bar{A} \text{ AND } B$ . Truth table:

A	B	$\bar{A} \text{ AND } B$
0	0	0
0	1	1
1	0	0
1	1	1
- NOT OR**: Inputs A, B, Output  $\bar{A} \text{ OR } \bar{B}$ . Truth table:

A	B	$\bar{A} \text{ OR } \bar{B}$
0	0	1
0	1	0
1	0	0
1	1	0

<https://cs.lmu.edu/~ray/notes/digitallogic/>

# Scalability

- Modern digital chips have the equivalent of *billions* of logic gates on them at this point.
- This scale and complexity was only achievable because the designs started with very simple, robust circuits.
- And goodness have we scaled and continued to scale

# Moore's Law...

- Original argument/prediction of how we'd scale computation...
- It has been correct so far since we kinda keep redefining what it means so that it keeps getting satisfied.
- It is a little bit of a meme/lie at this point...it represents more of an idea and vague definition of continued progress


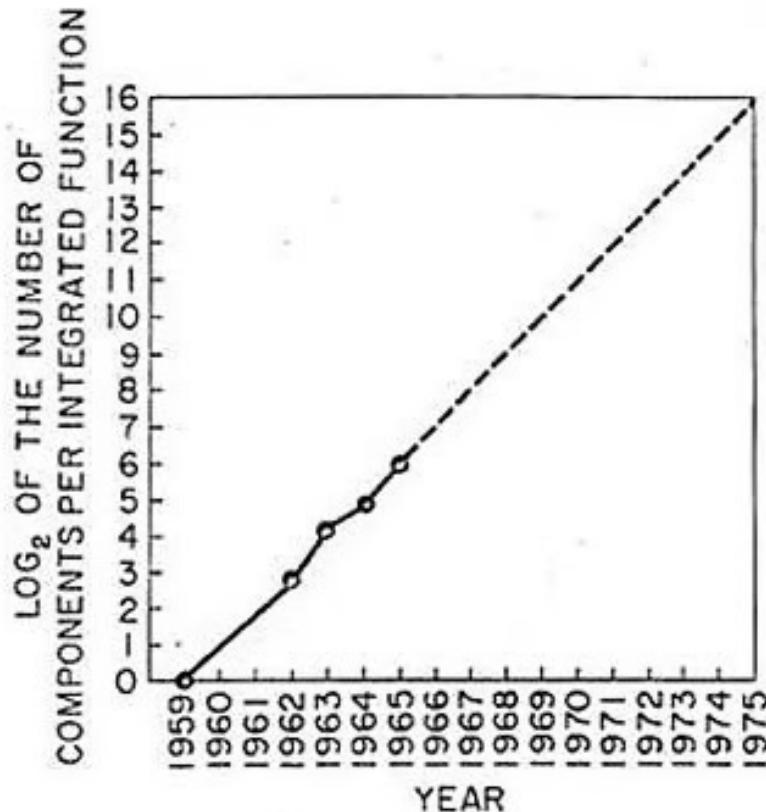


Fig. 2 Number of components per integrated function for minimum cost per component extrapolated vs time.


<https://ourworldindata.org/moores-law>
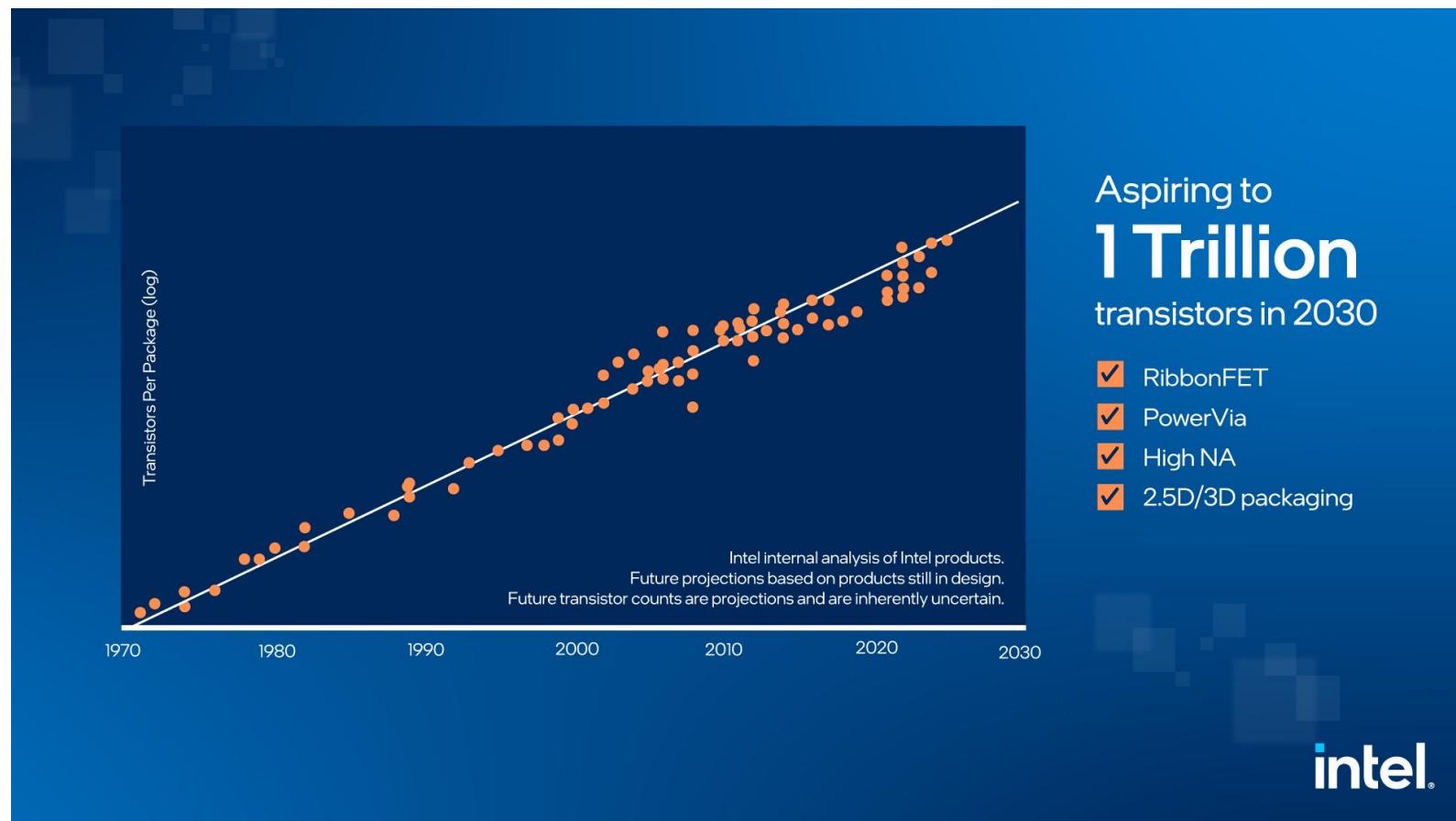
# Intel's Attempt at Explaining Moore's Law




<https://newsroom.intel.com/press-kit/moores-law>

# The AI is not self-aware

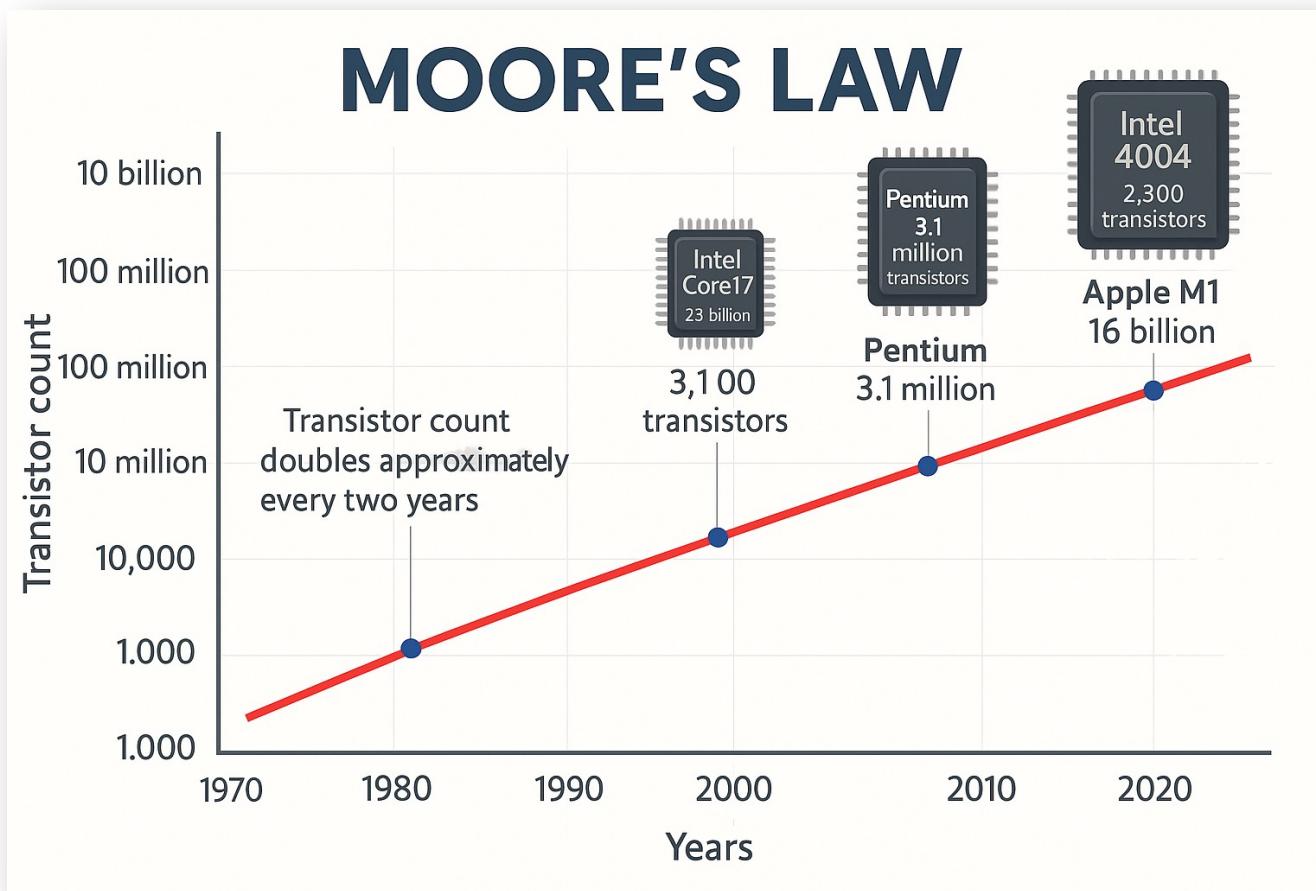

<https://sem/wiki.com/wikis/industry-wikis/moores-law-wiki/>

# Actually Pretty Good Plot

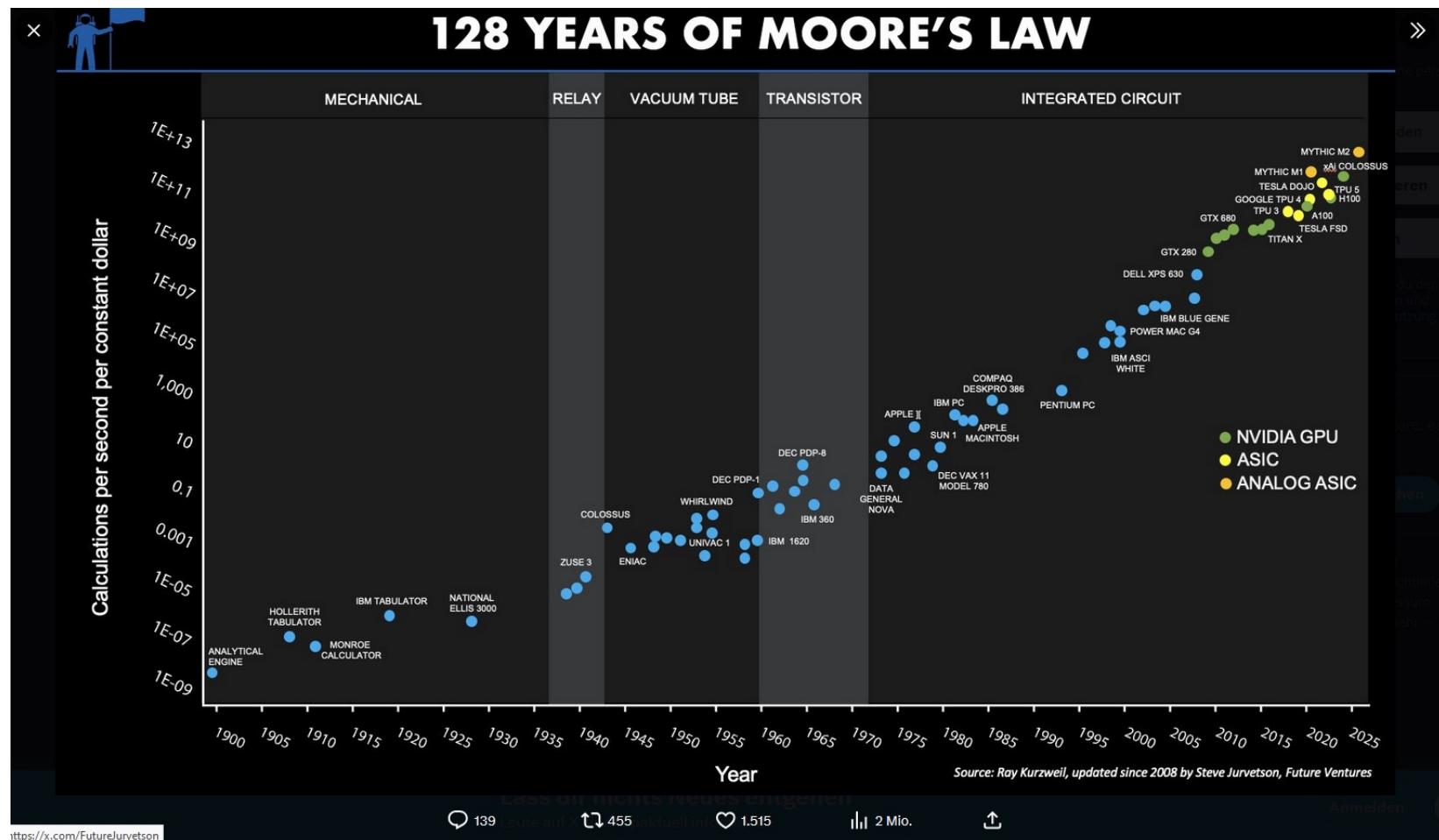

[https://www.reddit.com/r/singularity/comments/1h55mxm/moores\\_law\\_update/](https://www.reddit.com/r/singularity/comments/1h55mxm/moores_law_update/)


# State of the Art is Wild

- I think these are going for \$40K-ish
- Each of the 72 Blackwell GPUs has 208 billion transistors on it.
- Digital Electronics are Unfathomable



<https://futuretimeline.net/blog/2024/03/22-nvidia-ai-chip-208-billion-transistors.htm>



# Zeitgeist

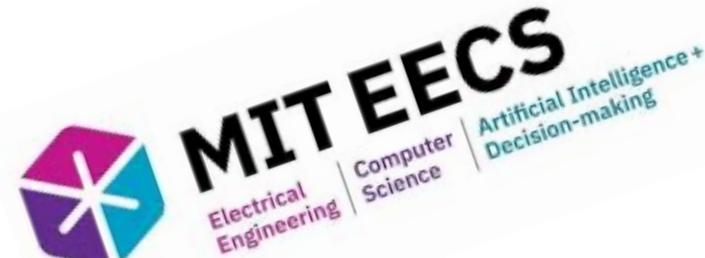

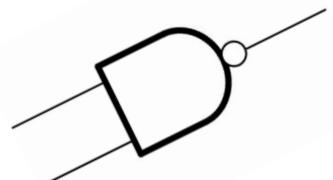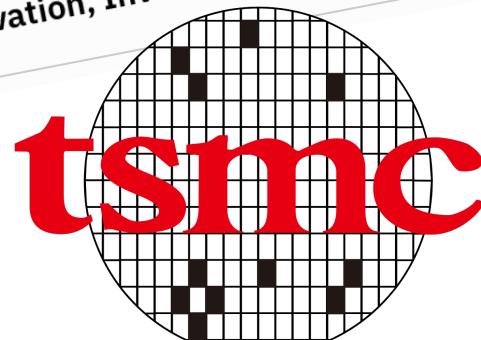
6.S187 Deploying Generative AI: Healthcare, Business Analytics, Education, Innovation, Investment §




# But I guess...where did this come from?

- Great...this is what we're doing now in 2025.
- Where did it come from?
- Why did we go this route?

# Stuff Leads to Other Stuff

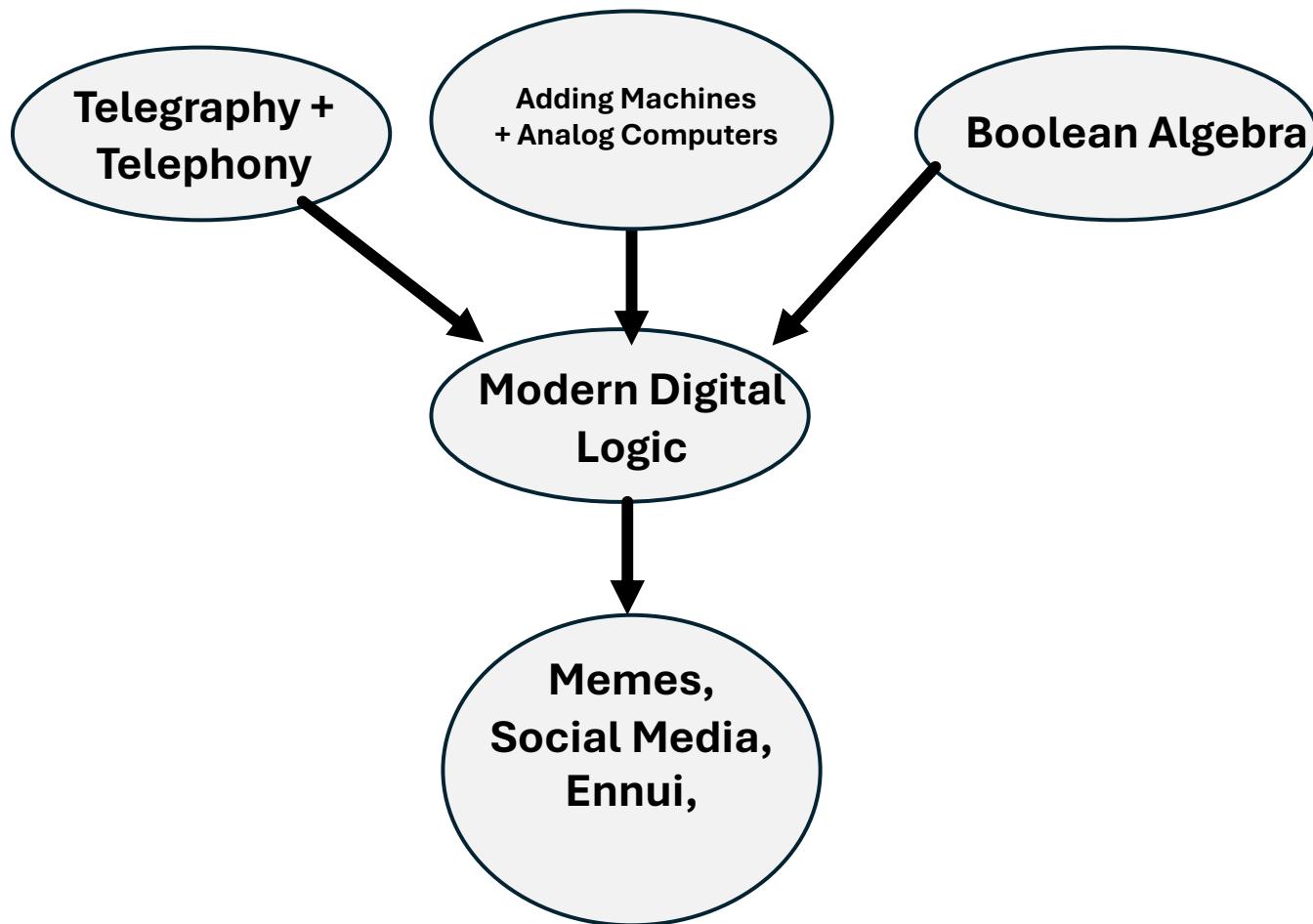

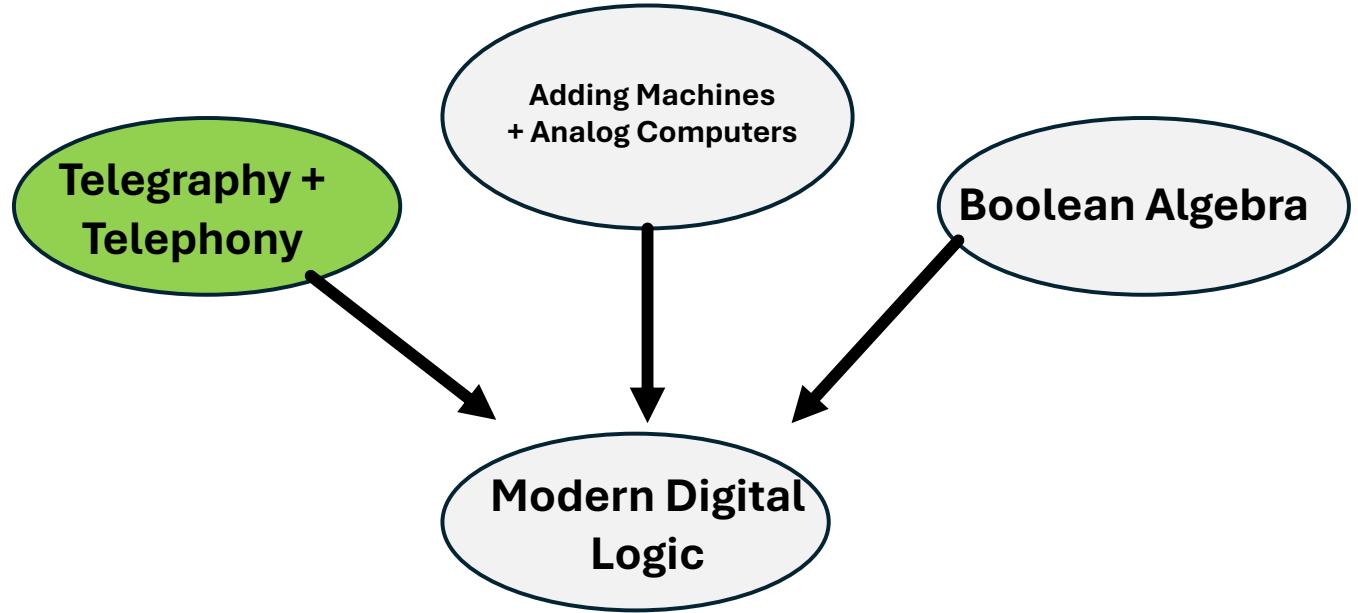


# Telegraphy

Digital Communication Before they Knew what Digital Communication Was


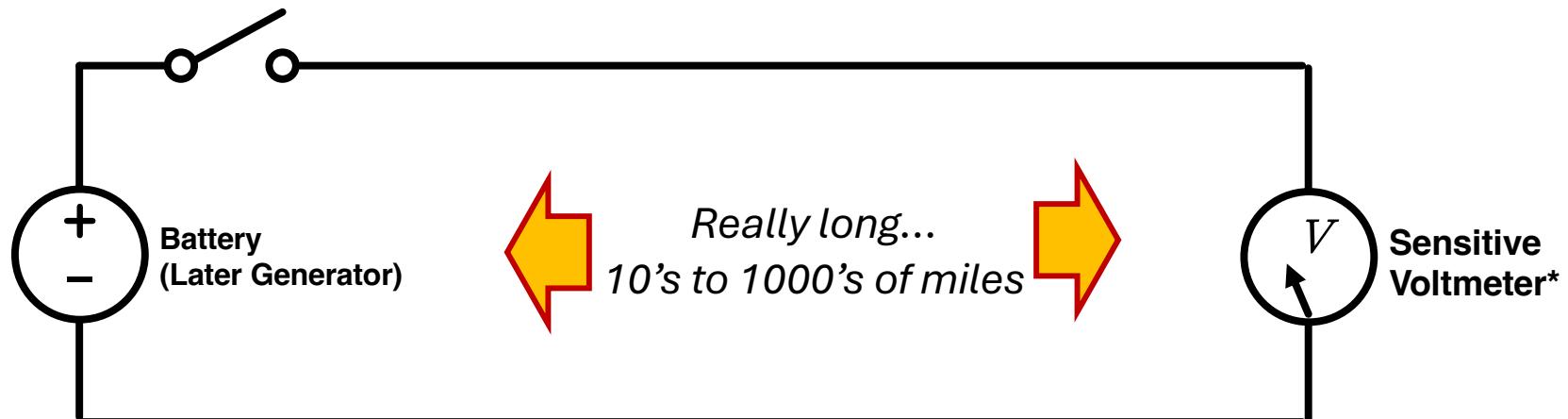
# Telegraphy/Morse Code (1830s)

- Samuel Morse (also a ok-ish painter)
- Encode information using ON-OFF values of differing lengths
- Basic digital communication


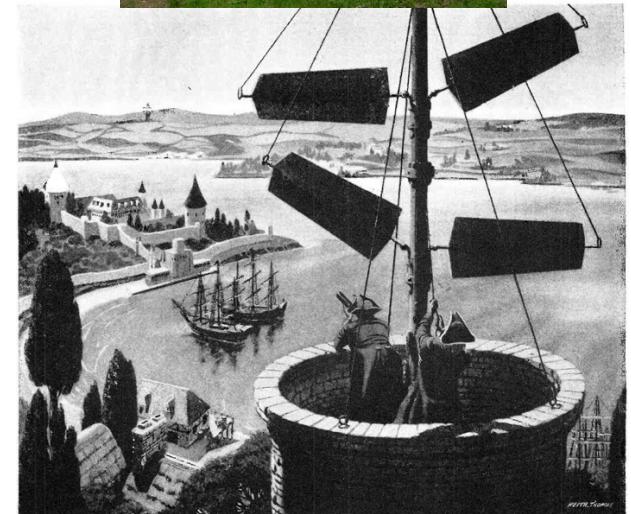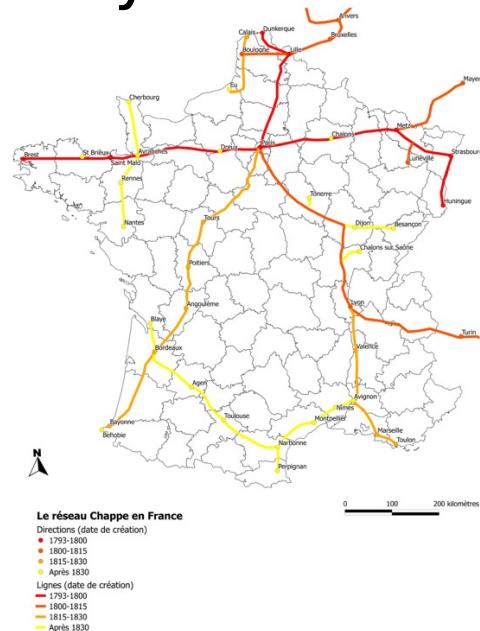
# Mechanical Telegraph (Semaphores)


- The original telegraph was made of chains of towers operated by people that would relay signals



[https://en.wikipedia.org/wiki/Optical\\_telegraph#/media/File:Signaling\\_by\\_Napoleonic\\_semaphore\\_line.jpg](https://en.wikipedia.org/wiki/Optical_telegraph#/media/File:Signaling_by_Napoleonic_semaphore_line.jpg)
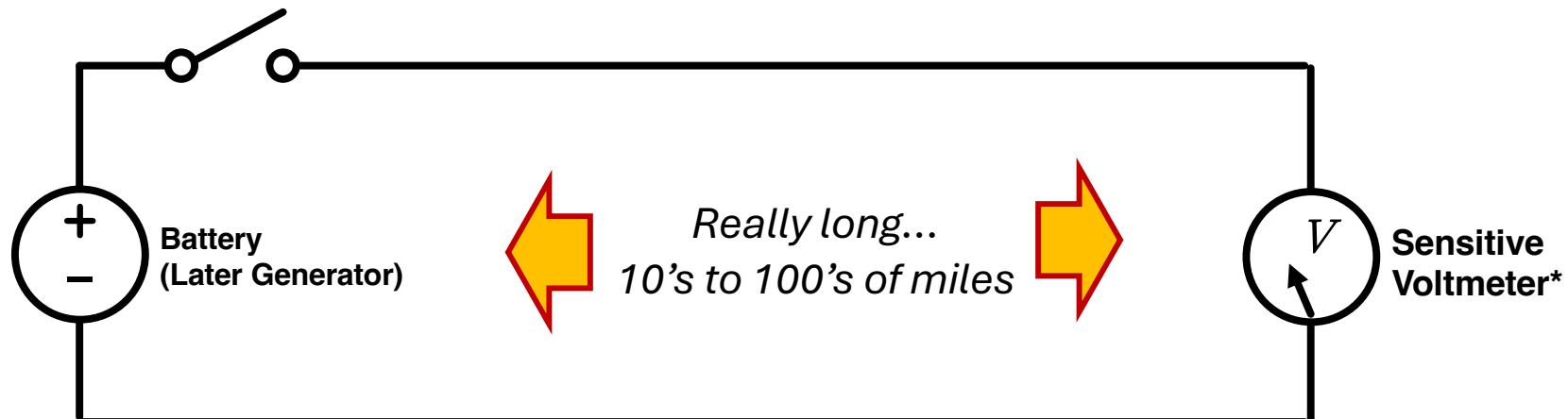
# Electric Telegraphy (1830s)

- Samuel Morse (also a decent painter) and many others developed electric telegraphy
- Encode information using voltage on/off pattern
- Basic digital communication




# How to Actually encode information?

- Same problem we deal with today when we send information.
- Rarely is signal encoded as:
  - Signal = “1”
  - No signal = “0”
- You run into lots of synchronization issues

# Synchronization Issues...

- Consider this signal...

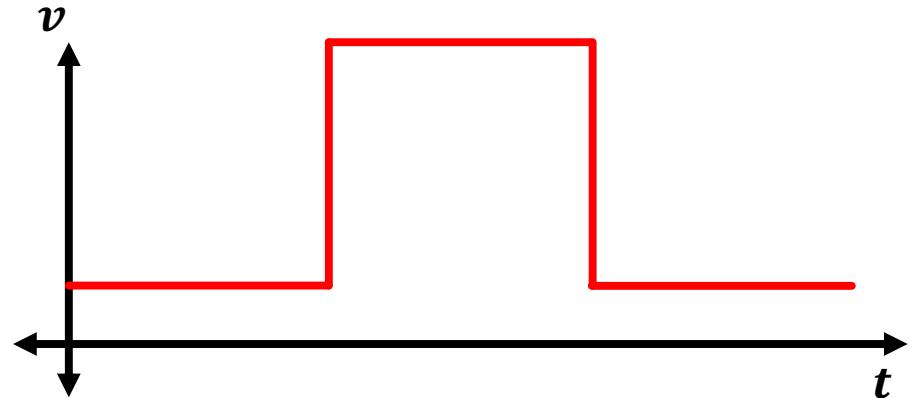


- Is this a 010? Is this a 001100? Is it a 000111000?
- Or is it no signal...followed by a 1 followed by a 0?
- Very confusing...

- In transmitting binary data...you usually need to be able to express **three** things...
  - 1
  - 0
  - no signal
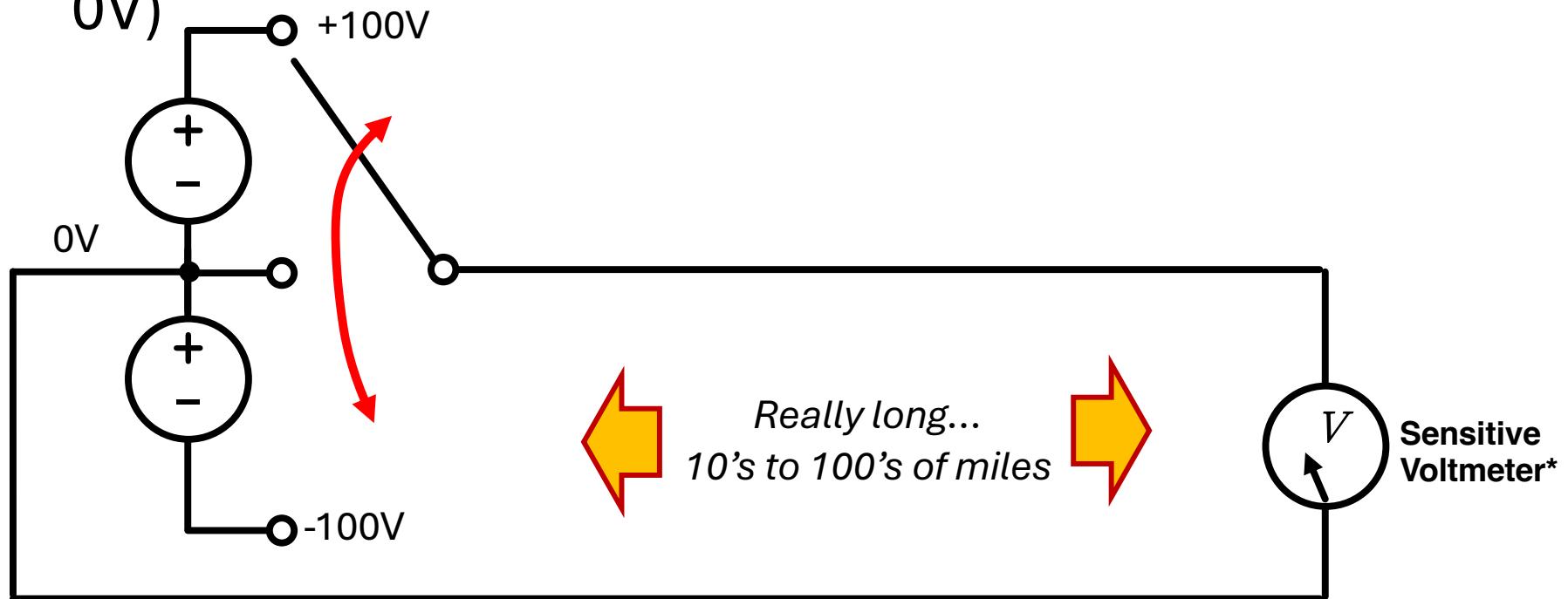
# Early Variants of Telegraphy

- A lot of European systems actually encoded three levels (large positive, large negative, and 0V)




- This actually required significantly more complicated detection equipment than just on/off signals

# Morse Code

- What Samuel Morse (and Joseph Henry) and Alfred Vail did was develop an encoding scheme that just involved on-off values
- They then used duration as an additional axis to get more expression
  - Short on pulse is a “1”
  - Long on pulse is a “0”
  - No signal is a no signal

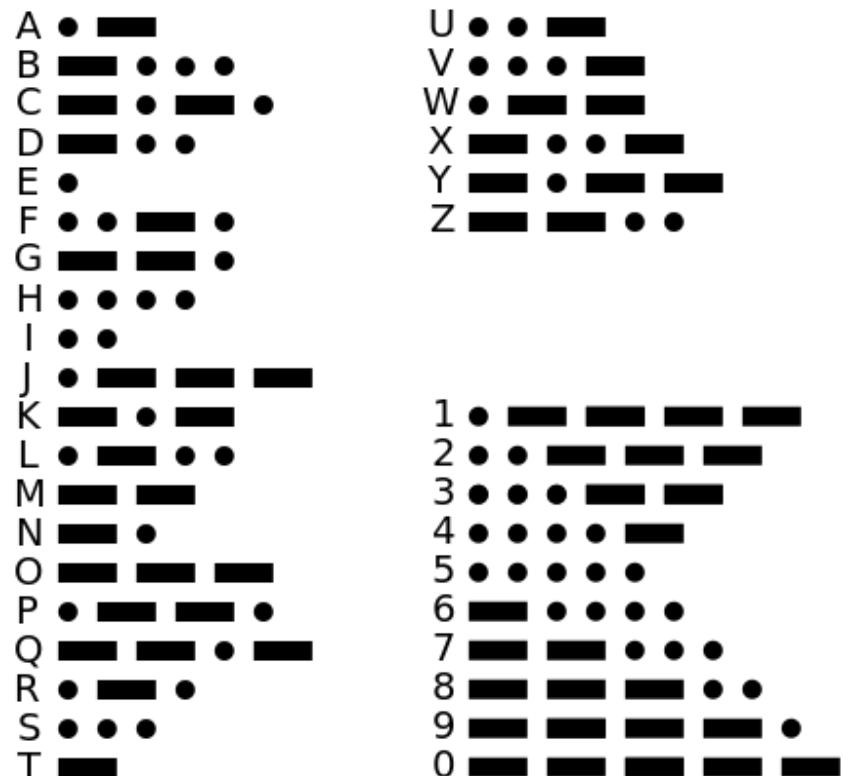
# Morse Alphabet (one version anyways)

- This allowed significantly simpler equipment and infrastructure and was actually easier to record, interpret
- It was also easy to sync data rates since silence meant “no signal”
- Proved easy to port to wireless 50 years later



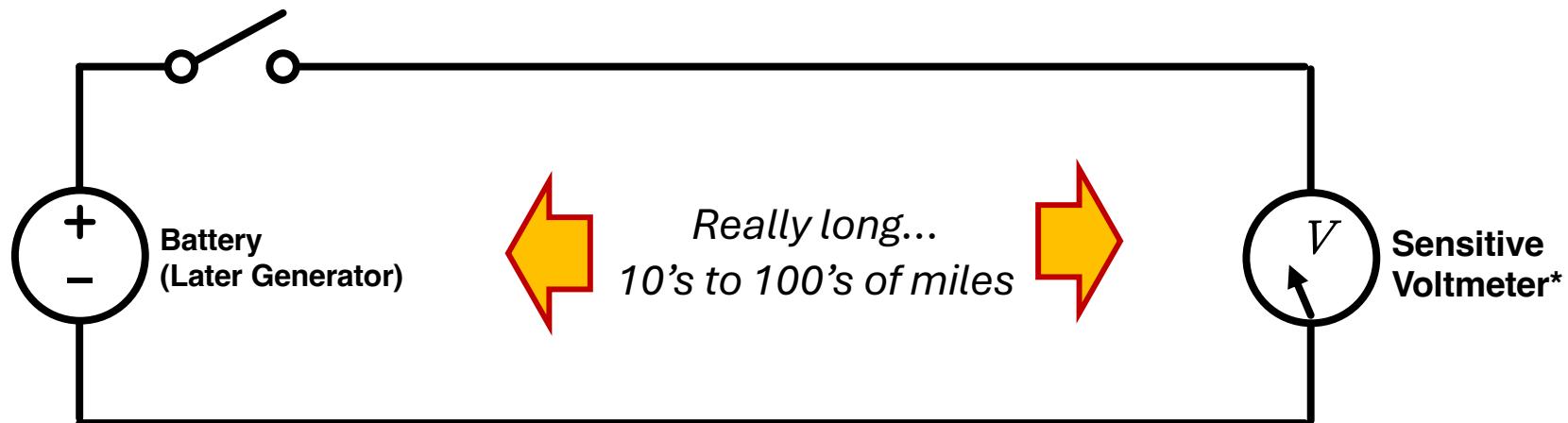
# Why digital? Why not analog?

- Well, first we had no meaningful signals in analog format anyways.
- Also losses were so great (and poorly understood) that having anything other than the harsh 1/0 interpretation of signal proved problematic



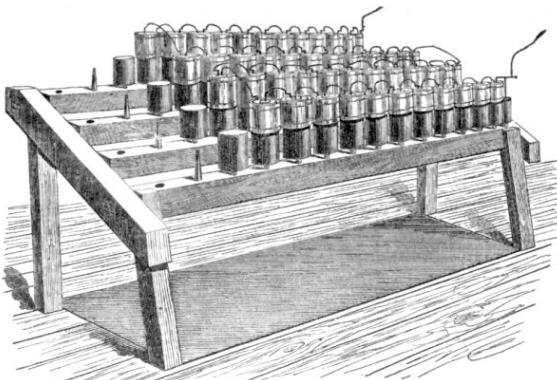
# Powering Telegraphy

- How did they do it?
- Generators weren't a thing until 1870s so used giant cell stacks in parallel/series combos (electrical batteries)



*Grove Battery*

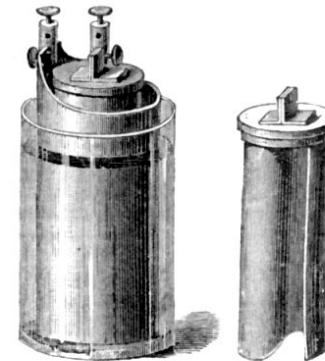

*Grove Cell*

Fig. 141.—A Grove's Cell. Fig. 142.—The Platinum.

*Zinc, Platinum/Carbon, Sulfuric Acid battery*


- Sources report you'd need about 2V per 10-to-20 miles of telegraph would work

# How Would it Work?




- More Complicated than this...and a bit different...

# How Would it Work (More Detail)

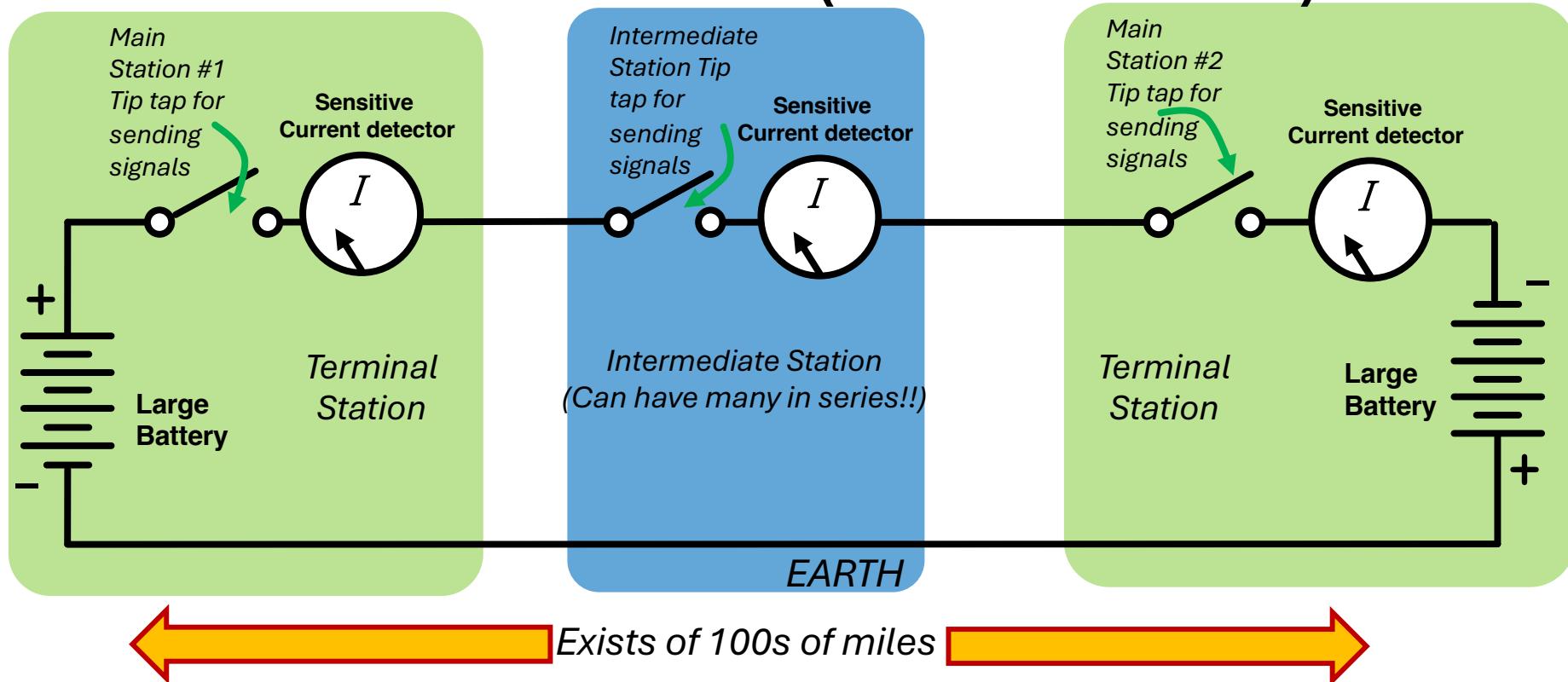


- Note opposite battery orientations...why?
- In reality the “return path” was usually Earth...why?
- How Did they make sensitive Current Meters?

# Leakage! Too

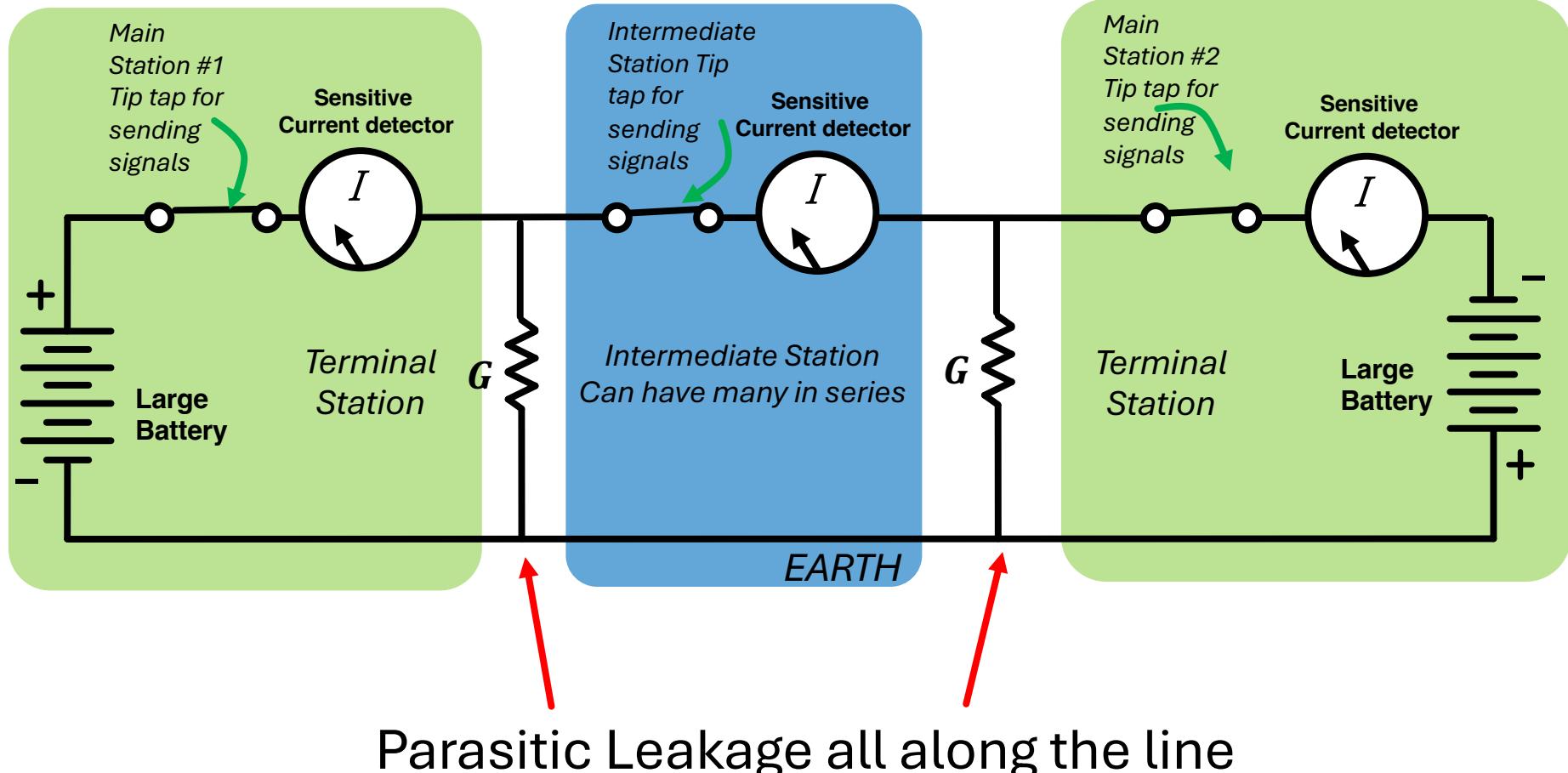
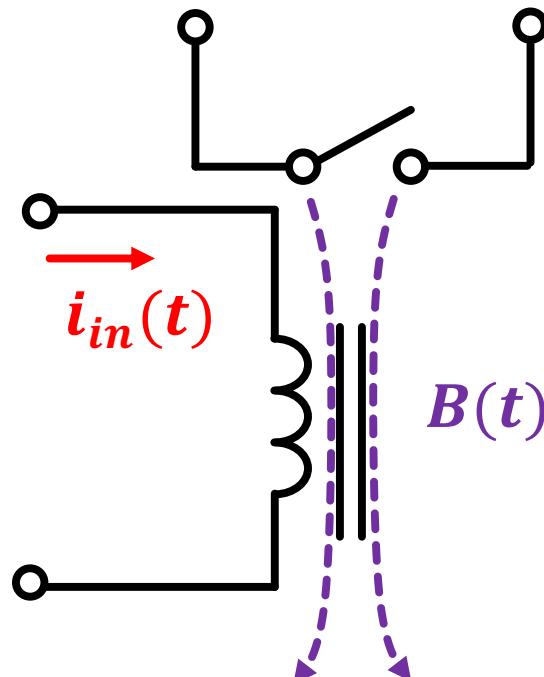
# Sense Current Using a Relay...what is a relay?


- An input set of terminals connected to a coil
- Coil can induce magnetic field
- Magnetic Field can influence position of nearby switch
- Incorporate that Switch Into a Local Circuit




<https://www.digikey.com/en/products/detail/omron-electronics-inc-emc-div/G2R-1-E-AC120/36>

6.S188 Eighties Clock

# Incorporate the Relay into a Circuit

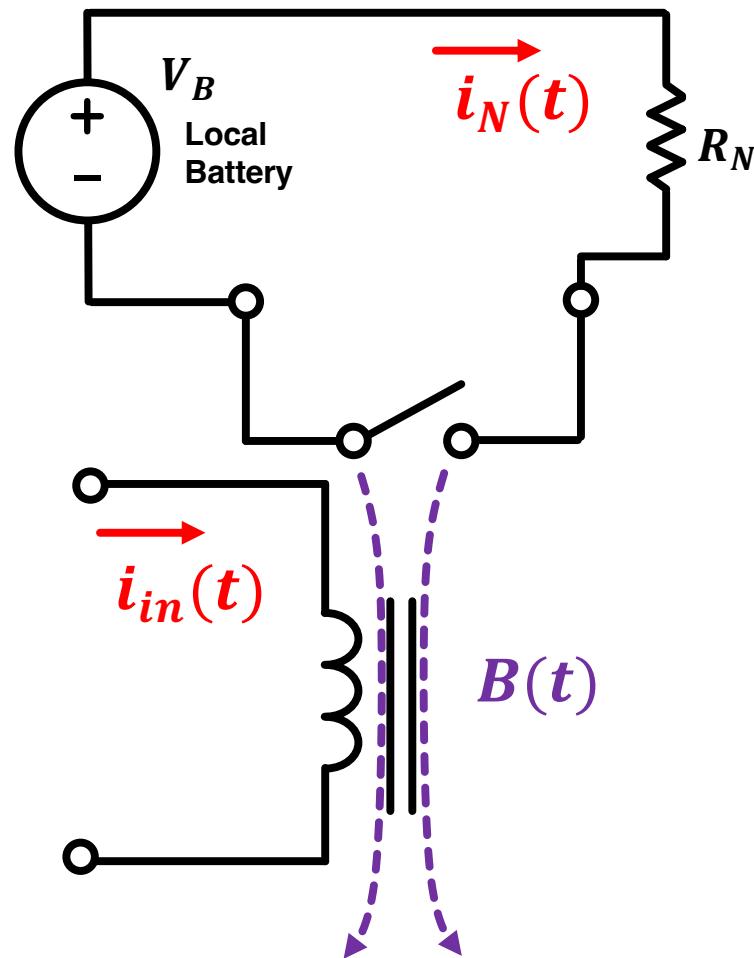


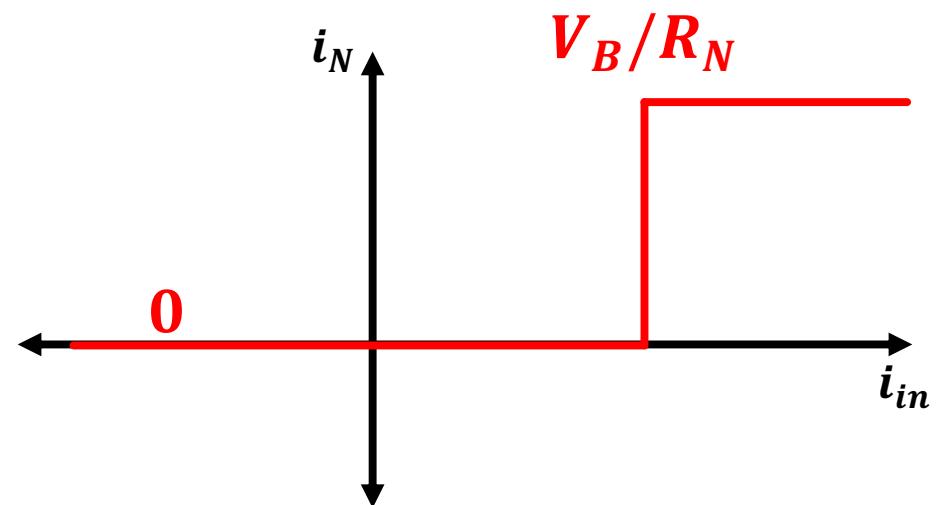- How will this circuit operate?
- What will its In/Out relationship look like?




- No current in secondary circuit will flow until current in coil passes some threshold
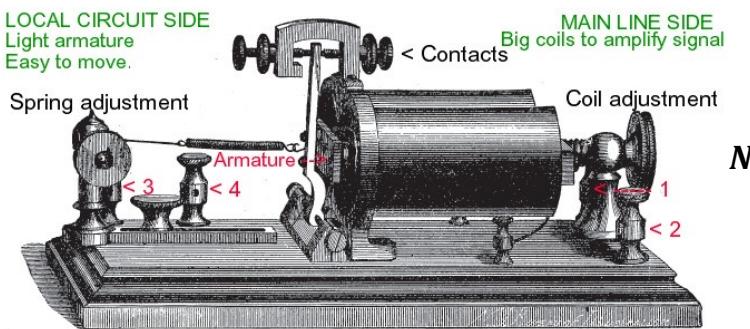
# This Input/Output Relationship can be engineered



- A ton of effort went into designing these relays to be very sensitive
- More windings of coil (increase induced field)
- Design a really nice switch
- Make sure it doesn't bounce...
- List goes on


# Returning to our Telegraph Circuit

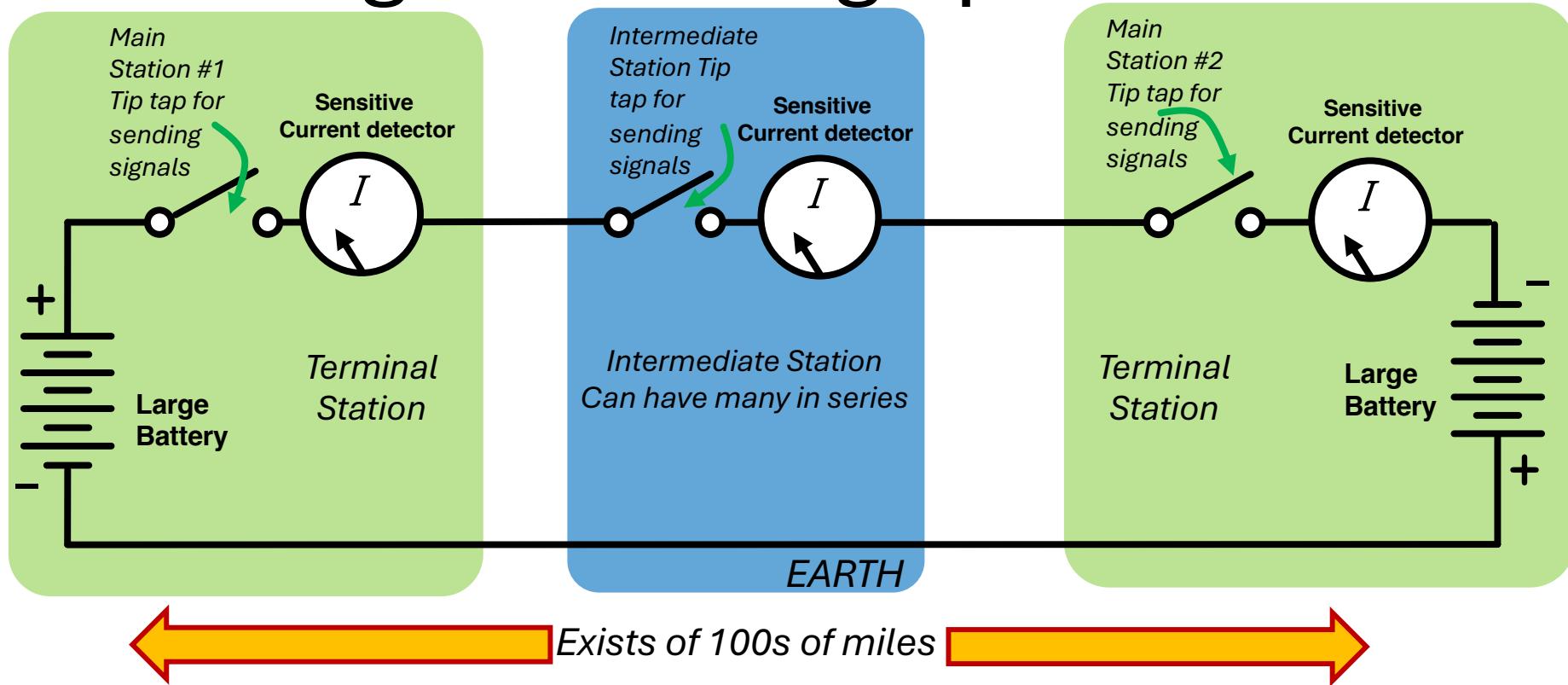

- Each station would have a local sensitive current meter built around a relay and a sounder!

# A Relay-based Current Detector:


Noise Maker:  
Electromagnetic tapper

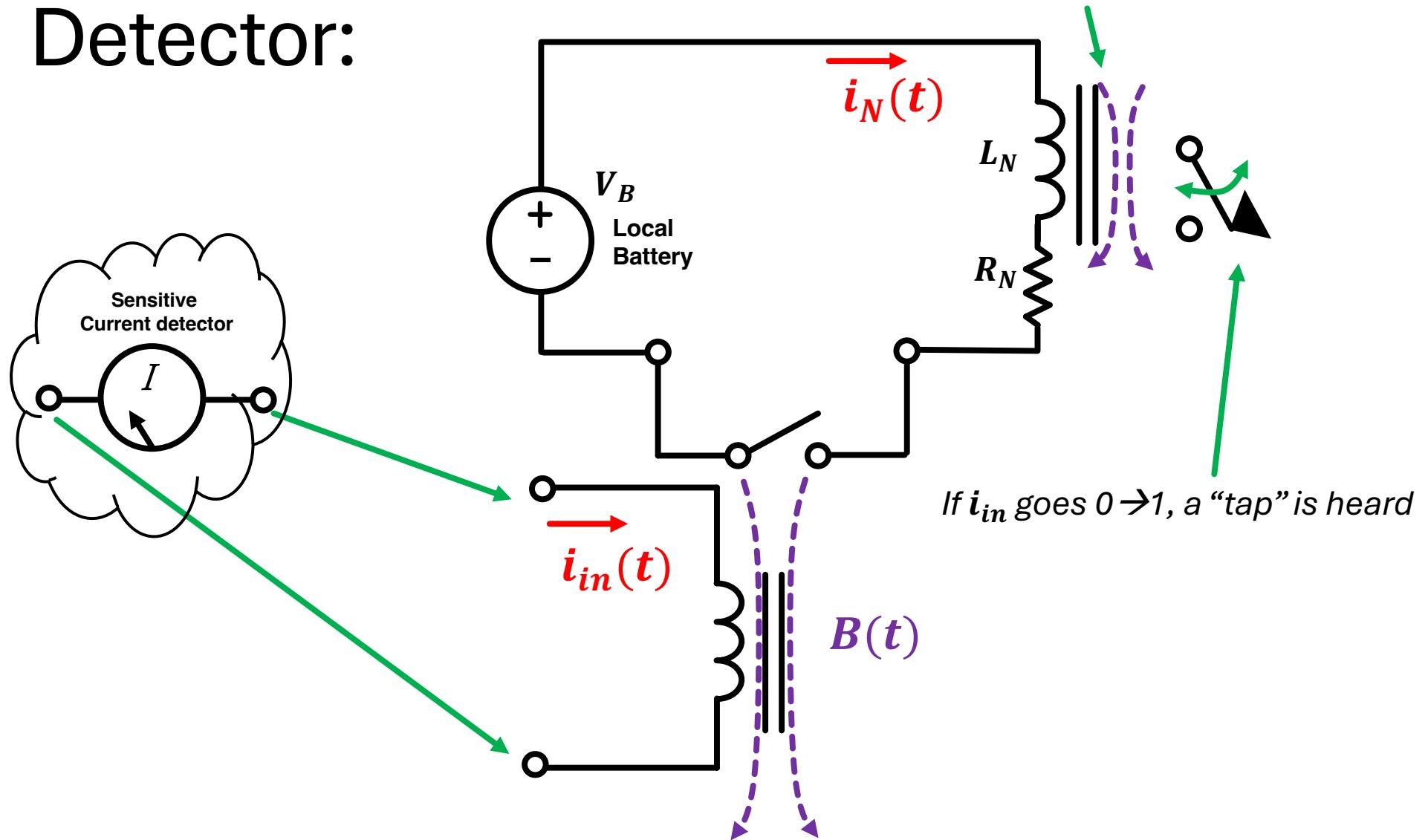

# Amplification

- Many miles from the terminal station  $i_{in}$  (and  $v_{in}$ ) will be small due to parasitic losses in the line. They would lack the ability to make much signal for a local listener
- A well-designed relay acted as an **amplifying device** for the signal so that the operator could easily hear the message!
- Not a strictly electrical amplifier. (but an electromechanical amplifier)

# Telegraph system

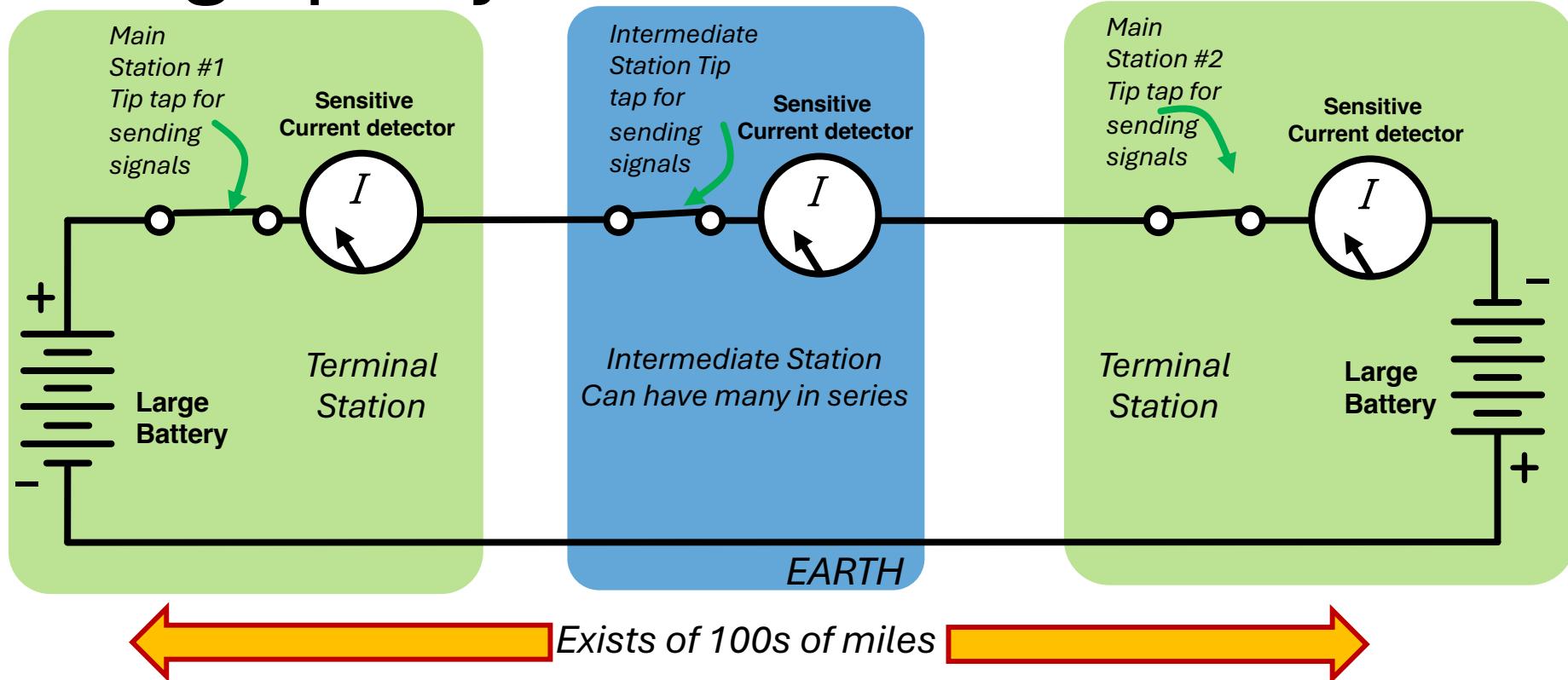


- At rest all stations would have their keys closed in a listen/propagate mode

# Telegraph Operation

- Each run of telegraph was a “party line”, meaning all stations on that run could listen in
- At “rest” all stations kept their keying switches closed!
  - Current therefore almost always flowed through the entire system!
  - Wasted power, but actually was beneficial for crappy early batteries
- If a station needed to broadcast, that station would open up their key, breaking entire circuit!
- All stations on line would detect this break in current and know to wait for start of message
- Transmitter would then send message

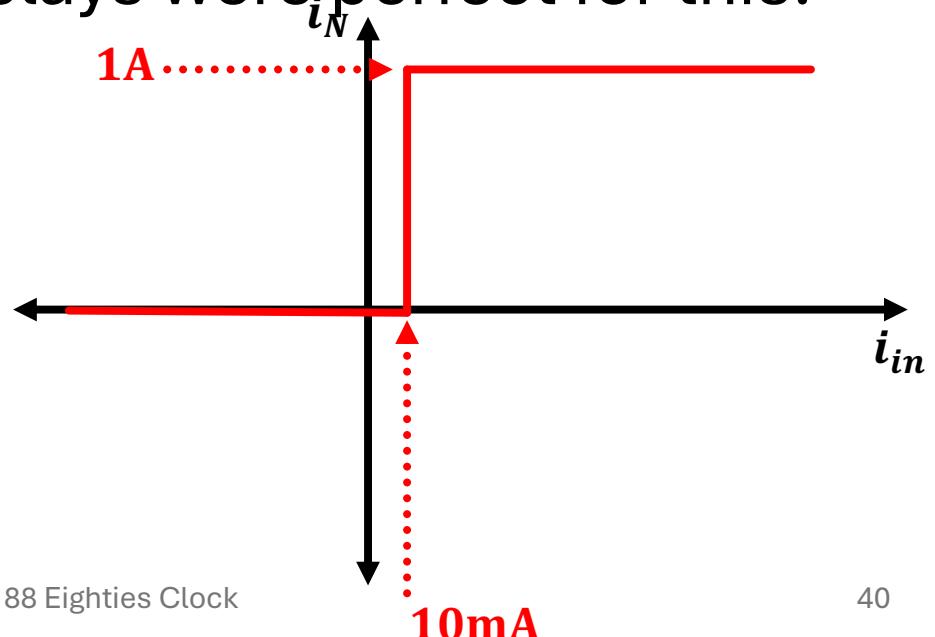
# Noise

- Noise in these systems was disgusting!
  - Parasitic leakage
  - Earth Ground
  - Leakage from nearby circuits
- A digital communication scheme was used (on-off signaling) because of all this.  
Electromechanical relays were perfect for this!



# Build Up Network of these Circuits

- North East US telegraph network, 1853

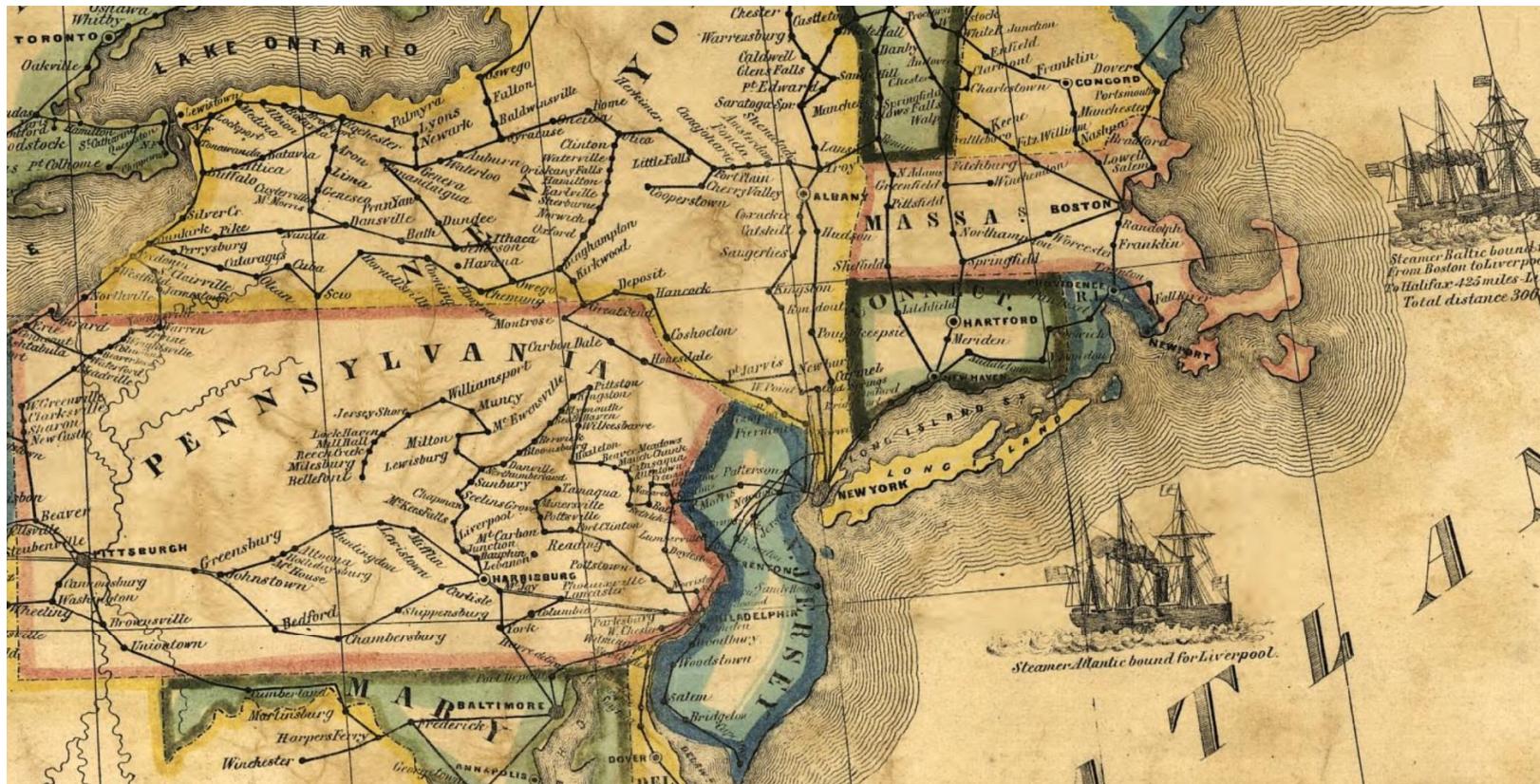


<https://www.loc.gov/resource/g3701p.ct000084/?r=0.577,0.18,0.283,0.154,0>

# Telegraph Network Europe 1856



# Build Up Network of these Circuits

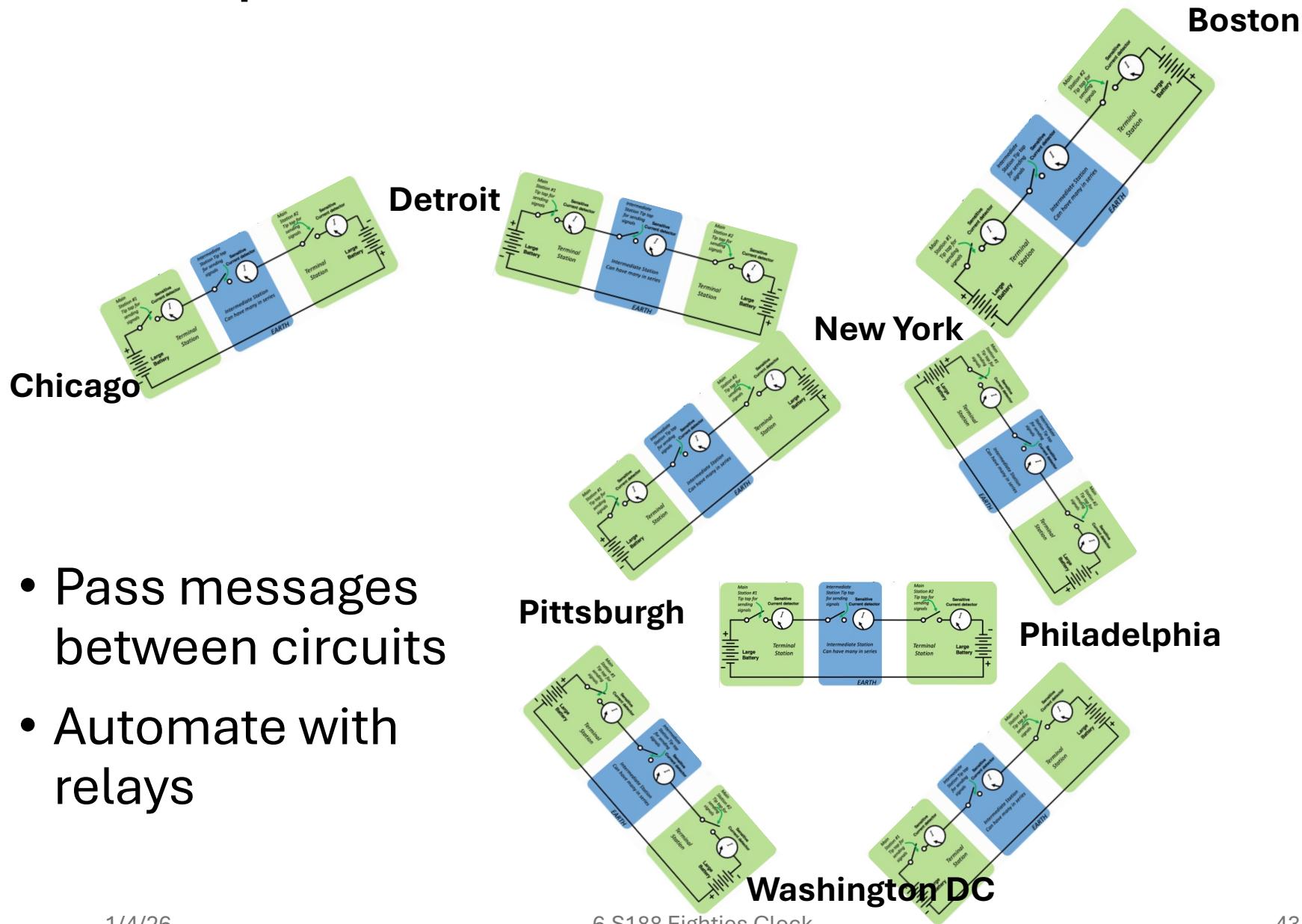

# People were intimately exposed to the telegraph (and follow-on telephone)




Stockholm Central  
Telephone/Telegraph Tower



New York 1887
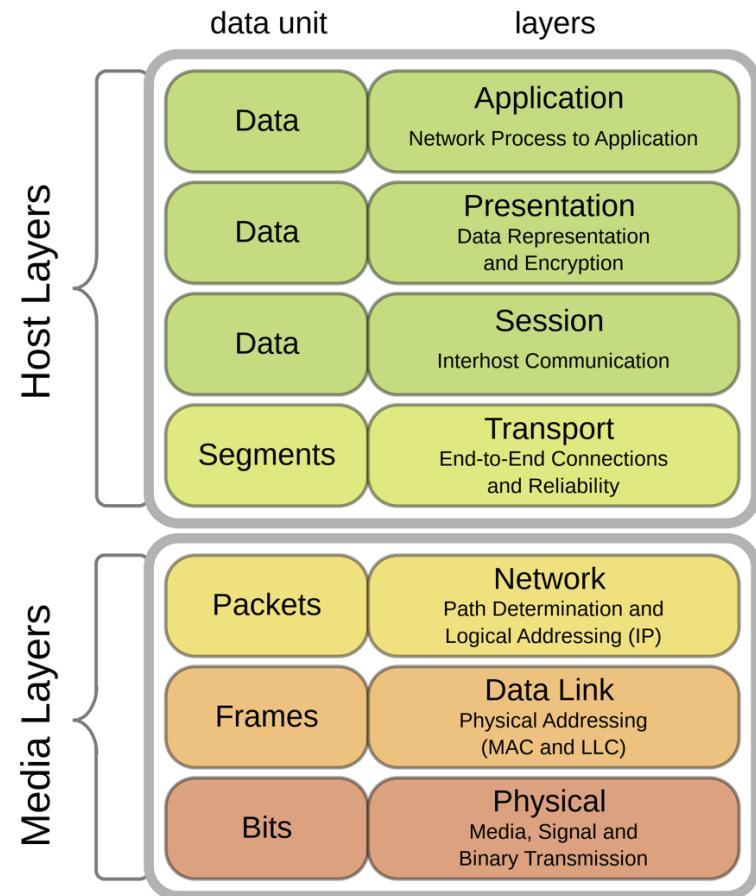
# Telegraph Operation

- Had to develop an entire communication protocol!
- Morse was your alphabet (in US), but then you had to have addressing, message-begin/end/qualifiers, forwarding, etc...
- Much of our modern “protocol stack” can be reverse-applied to what they came up with!
- Early telephone and telegraphy had very complicated routing systems




# American Telephone and Telegraph

- Known as “Ma Bell” this company developed from the 1880s up through the 1950s before being broken up in anti-trust actions
- Was the largest employer in the US.
- Company rivaled federal government in size and operating costs.
- Poured massive resources into improving their system.
- Spun out Bell Laboratories from which tons of EECS developments and inventions were produced and very liberally licensed



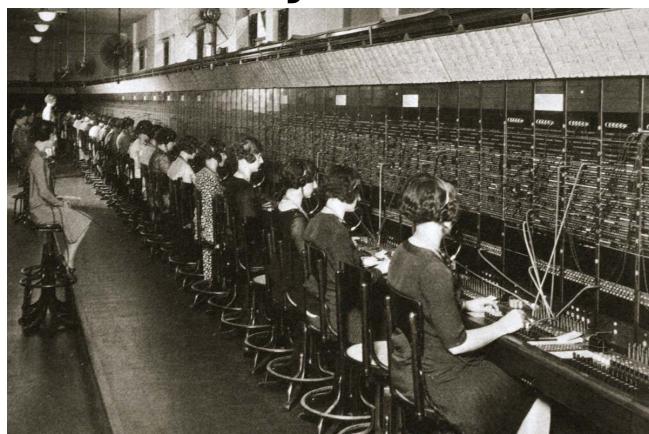
# Telephone Relay Stations

- A standard telephone relay station serving 10,000 customers would have about 60,000 relays in it.
- Hundreds of these throughout the country.


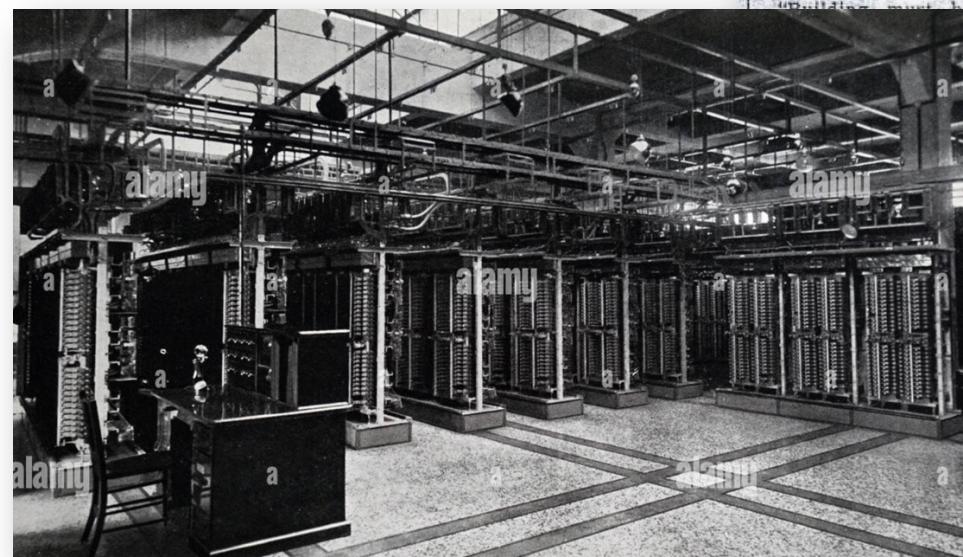
<https://www.alamy.com/stock-photo-the-leeds-automatic-telephone-exchange-circa-1920-131277159.html?imageid=AC1DD1CB-8FA5-4119-94A8-E90646857EDB&pn=1&searchId=baae1e609757033cbe6a70eebbec1d9&searchtype=0> 1/6/26



6.S188 Eighties Clock

**CONDITIONS ARE IMPOSED**



TELEPHONE COMPANY ALLOWED TO USE SITE.

Opposition Practically Withdrawn as Result of Report Presented by City Engineer Lauregaard.

The proposed new telephone exchange building in Irvington will be erected at East 24th and Stanton street, permission for its construction having been granted unanimously by the city council yesterday. The permit is subject to numerous restrictions which must be accepted by the telephone company before the building permit may be used. A \$5000 bond is required from the company to insure compliance with the conditions imposed. These conditions are as follows:

"Building must be of residential rounds must be no sign of any building; committed to add any two as is proposed; no garages will be permitted two years of number of operators after two years reduced to ten; be utilized as any purpose other than telephone." Practically withdrawn of City Engineer which he held charge building the proposed site service throughout
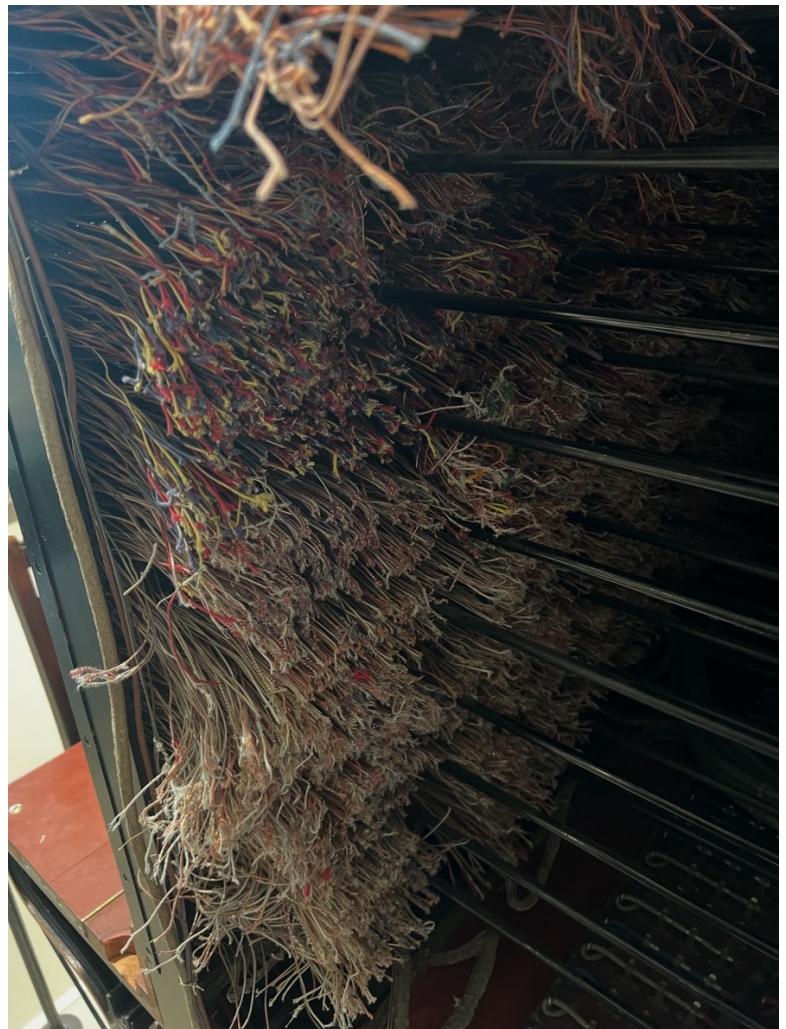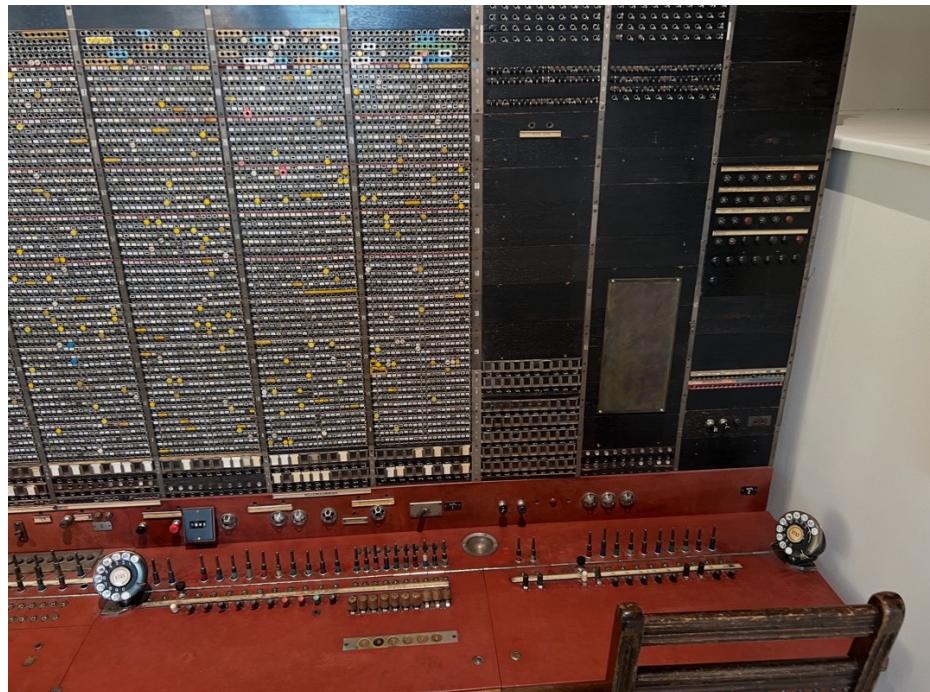
<https://alamedahistory.org/2012/02/19/mystery-building-at-ne-24th-and-stanton-has-always-been-a-telephone-exchange/>




<https://www.newscientist.com/article/mg25734260-100-a-message-for-today-from-last-centurys-vast-telephone-exchanges/>

# Electromechanical Relay

- The entire telephone and telegraph network was built around electromechanical relays that were extremely well-engineered.
- Western Electric (the Bell subsidiary that specialized in manufacturing) produced thousands of types of specialized relays.
- Extremely optimized technology

<https://www.ebay.com/item/114161685726>



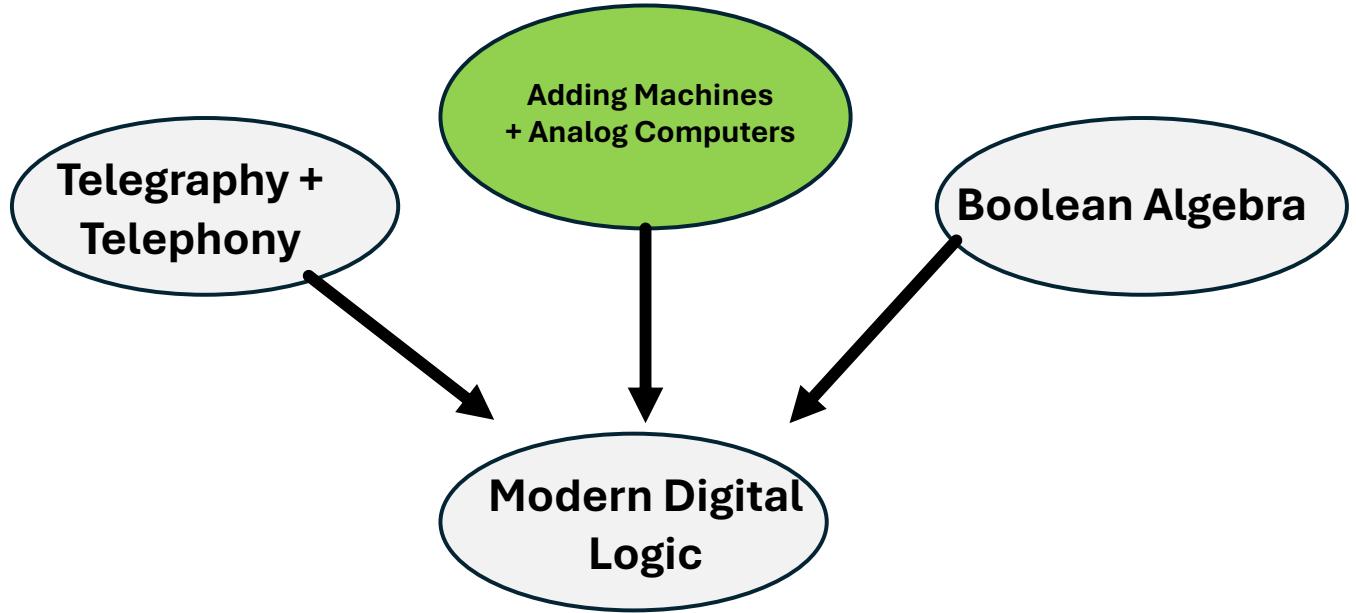

# Adding Machines

Doing Math and Maybe More Electromechanically

# Charles Babbage (1823)



- Designed the Difference Engine (built by Joseph Clement)
- Purely mechanical numerical solver that worked in 10's complement
- Programmed by several people including Ada Lovelace



<https://www.britannica.com/biography/Charles-Babbage>

<https://cronatec.ch/how-did-the-difference-engine-work/>

# Adding/Tabulating Machines

- 1870s and onwards featured tons of startups developing machines that could do arithmetic and/or tabulate information using gears and motors.



Divide by Zero on the Friden STW10 Mechanical Calculator



76K Share Save ...


[https://www.youtube.com/watch?v=7Kd3R\\_RIXgc](https://www.youtube.com/watch?v=7Kd3R_RIXgc)



<https://lcamtuf.substack.com/p/a-brief-history-of-counting-stuff>
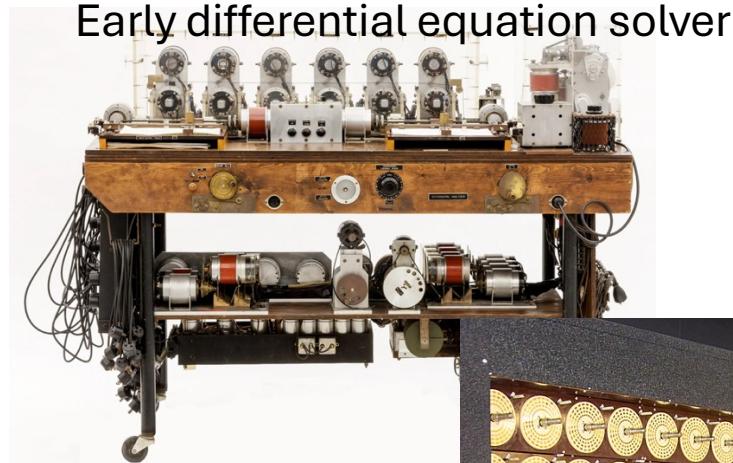
# Electromechanical “Computing”

- Wasn’t just limited to arithmetic.
- Electromechanical machines were developed to solve differential equations or perform other mathematical operations like



Alan Turing et al's “Bombe”  
<https://en.wikipedia.org/wiki/Bombe>

<https://spectrum.ieee.org/the-shocking-truth-behind-arnold-nordsiecks-differential-analyzer>


# Vannevar Bush

- MIT's Vannevar Bush took the electromechanical calculator approach to the extreme.
- The “Differential Analyzer” in 1930s



*MIT building 13 was named after him*

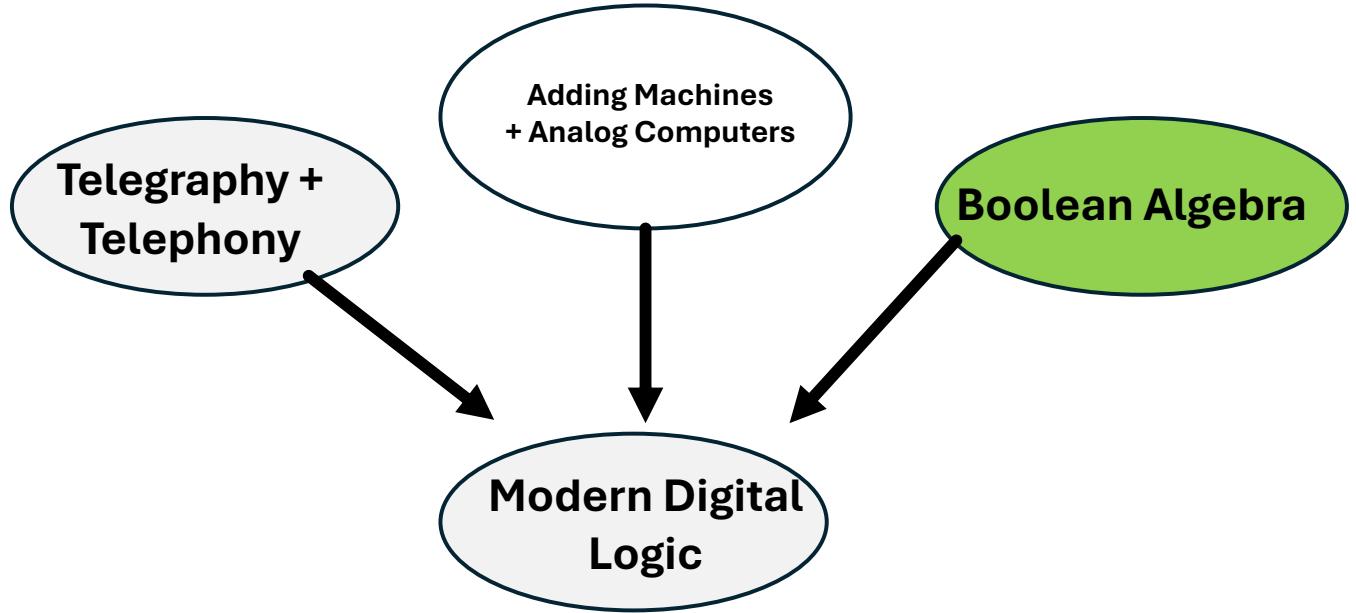- Could solve very challenging differential equations purely electromechanically
- One of his grad students was Claude Shannon who's project was to add some improvements onto the Differential Analyzer using relays to route signals....



# Boolean Algebra

A different type of math

# George Boole (1815-1864)

- Faculty at Queen's College in Cork, Ireland
- Mathematician and philosopher
- Wrote *The Laws of Thought* (1854) in which he offered an attempt at mathematical logic.



<https://www.ucc.ie/en/heritage/history/people/ucc-staff/professor-george-boole/>

# Few other folks also contributed

- De Morgan cleaned up and formalized some of Boole's work
- William Hamilton also
- The rules/identities/etc...form basis of what we have today..

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\bar{AB} = \bar{A} + \bar{B}$	$\bar{A + B} = \bar{A}\bar{B}$

# Boolean Algebra

- This work is a weird text...half math and half philosophy
- It is/was completely removed from what we want to think of it (being applied to computer science)

2nd. Evil of imperfection is not absolute evil.

3rd. Natural evil is either a consequence of evil of imperfection, or it is compensated with greater good, or it is a consequence of moral evil.

4th. That which is either a consequence of evil of imperfection, or is compensated with greater good, is not absolute evil.

5th. All absolute evils are included in reputed evils.

To express these premises let us assume—

$w$  = reputed evil.

$x$  = evil of imperfection.

$y$  = natural evil.

$z$  = moral evil.

$p$  = consequence of evil of imperfection.

$q$  = compensated with greater good.


$r$  = consequence of moral evil.

$t$  = absolute evil.

Then, regarding the premises as Primary Propositions, of which all the predicates are particular, and the conjunctions *either*, *or*, as absolutely disjunctive, we have the following equations:

$$w = v \{x(1 - y)(1 - q) + y(1 - x)(1 - z) + z(1 - x)(1 - y)\}$$
$$x = v(1 - t).$$
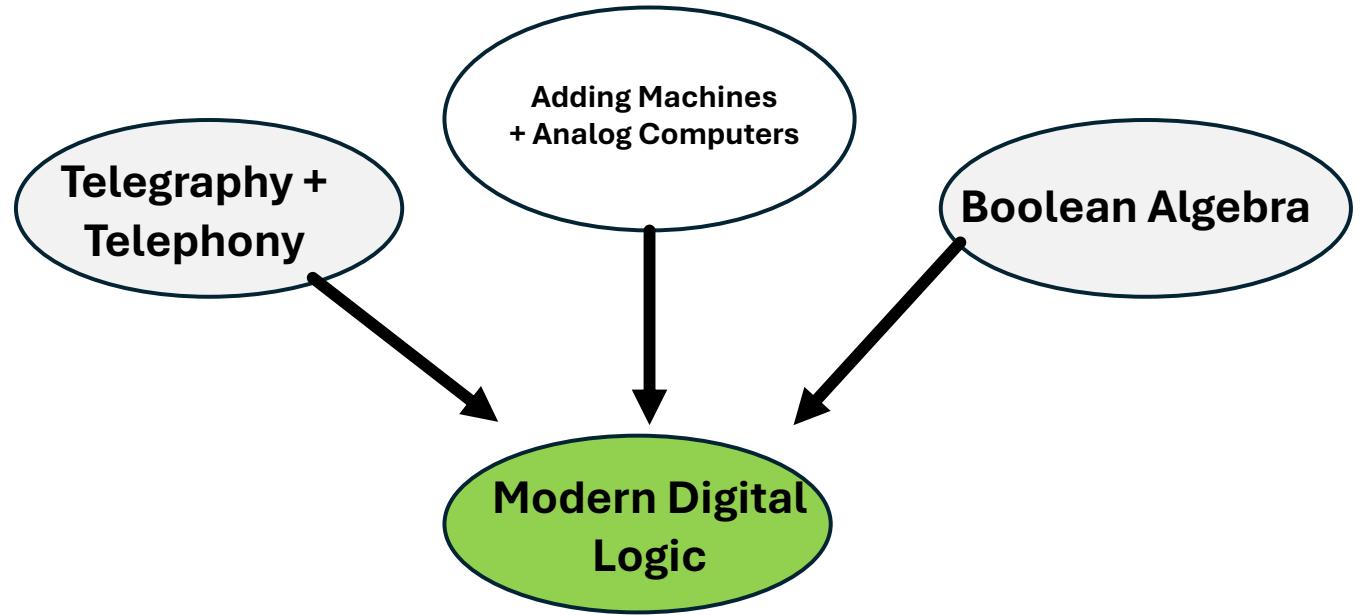
$$y = v \{p(1 - q)(1 - r) + q(1 - p)(1 - r) + r(1 - p)(1 - q)\}$$
$$p(l - q) + q(l - p) = v(1 - t).$$
$$t = vw.$$



# Claude

# Claude Shannon


- Undergrad at University of Michigan in EE and Math
- Took a philosophy elective while at Michigan that covered Boole's Algebra one week.
- Came to MIT for grad school.
- Got job working for Vannevar Bush to improve differential analyzer



<https://www.lindahall.org/about/news/scientist-of-the-day/clause-shannon/>
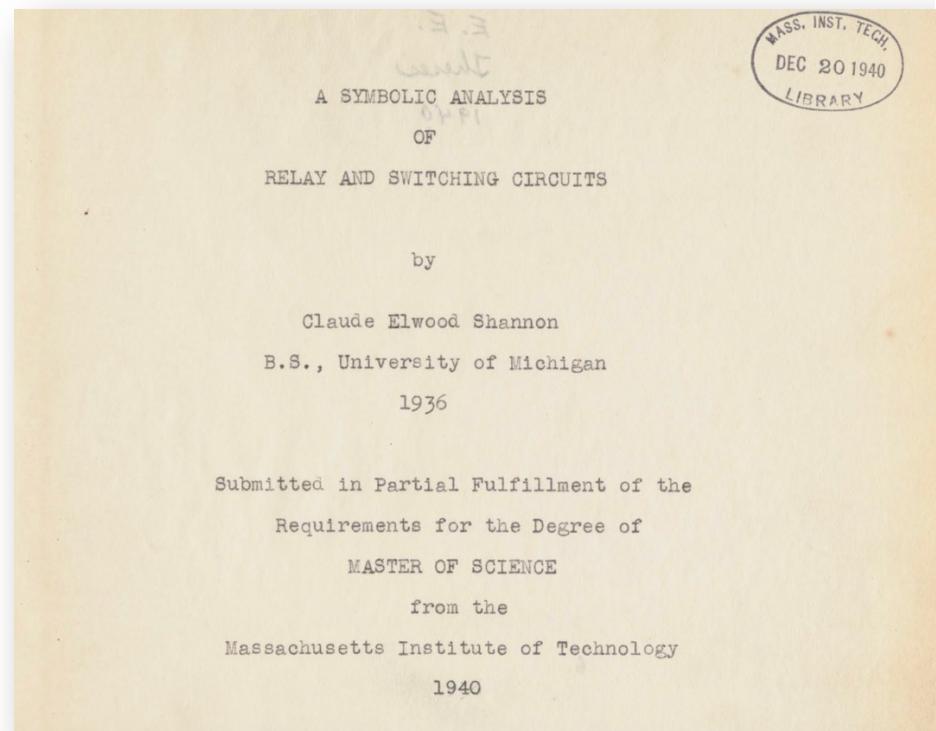
# Claude Shannon

- His PI wanted him to integrate some relays into the differential analyzer.
- He started doing it and kinda realized the Boole's logic stuff from that philosophy class would describe.
- Wrote his M.S. thesis on it.



<https://dspace.mit.edu/handle/1721.1/11173>

# Whole Thesis is Good Reading

hinderance of the circuit formed by connecting the circuits a-b and c-d in parallel. A relay contact or switch will be represented in a circuit by the symbol in Fig. 1, the letter being the corresponding hinderance function. Fig. 2 shows the interpretation of the plus sign and Fig. 3 the multiplication sign.

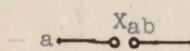


Fig. 1

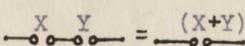


Fig. 2

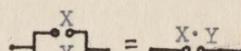


Fig. 3

This choice of symbols makes the manipulation of hinderances very similar to ordinary numerical algebra.

- Many figures are hand-written
- Links switching circuits to Boolean Algebra

Term “hinderance” which you never see again


Analogue with the Calculus of Propositions. We are now in a position to demonstrate the equivalence of this calculus with certain elementary parts of the calculus of propositions. The algebra of logic (1), (2), (3) originated by George Boole, is a symbolic method of investigating logical relationships. The symbols of Boolean algebra admit of two logical interpretations. If interpreted in terms of classes, the variables are not limited to the two possible values 0 and 1. This interpretation is known as the algebra of classes. If, however, the terms are taken to represent propositions, we have the calculus of propositions in which variables are limited to the values 0 and 1\*,

- Links his circuits to algebra by Boole

*Actual typo...must not have had time to retype whole page*
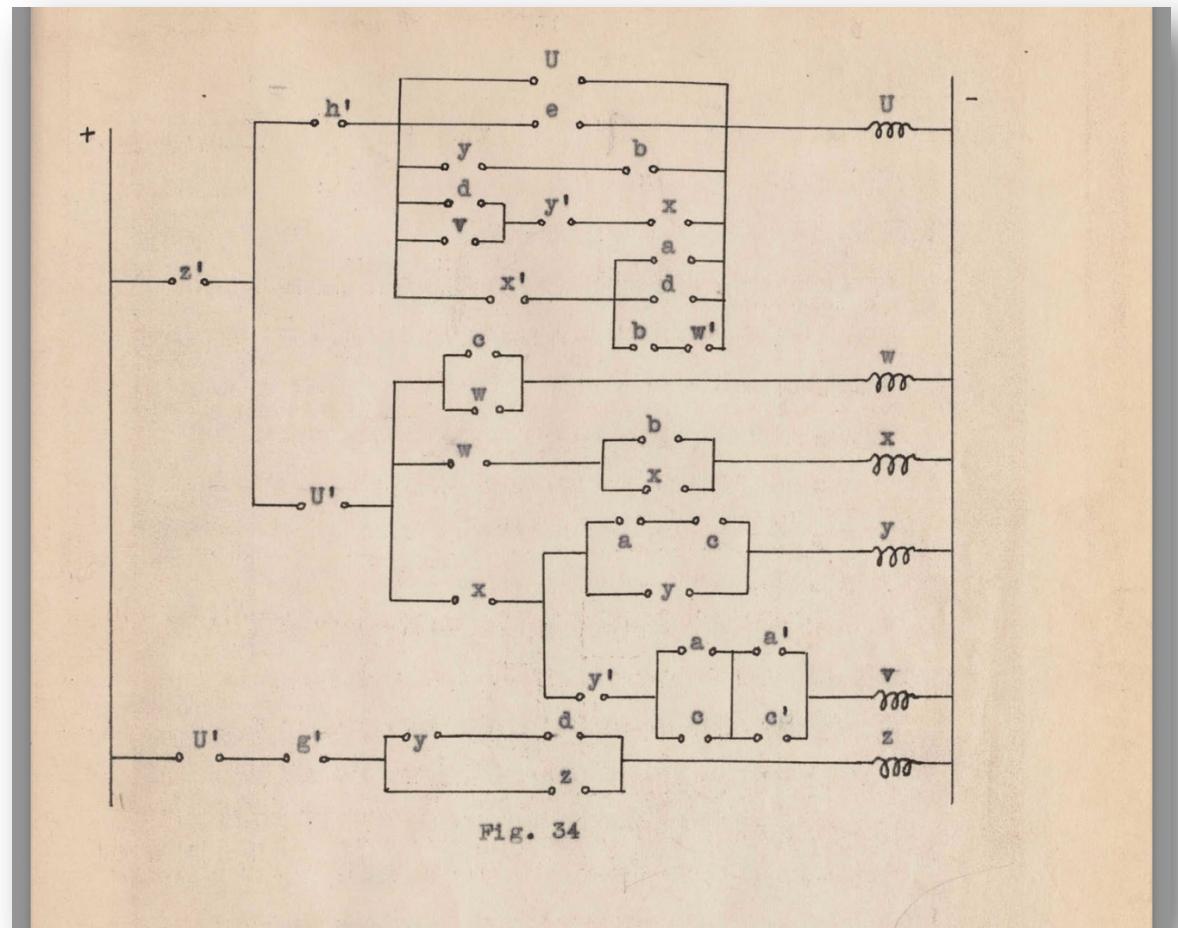
# Quite Complicated Examples/Circuits

- Not a modern logic gate symbol to be found!
- Just relay coils and switch on/off locations linked with equations



# Claude's Future Work Section...

- Numerous example problems
- Final one is to find prime numbers up to 100,000,000 using the Sieve of Eratosthenes

A Factor Table Machine


A machine is to be designed which will automatically print a table of factors and primes of all the integers from 1 to 100,000,000. If a number is prime, it is to be so marked; if composite, its least factor is to be printed beside it. The principle which will be used is that of the sieve of Eratosthenes (6). Let the natural numbers be written in order;

1, 2, 3, 4, 5, 6, 7, 8,.....

Now consider the prime numbers in order, 2, 3, 5, 7, 11, 13, 17..... Each 2nd number after 2 in the row of natural numbers has the least prime factor 2; each third number after 3 which is not a multiple of 2 has the least prime factor 3; each 5th number after 5 not divisible by 2 or 3 has the least prime factor 5, etc. Any number P not having a prime factor less than itself is, of course, a prime. It is customary in tables
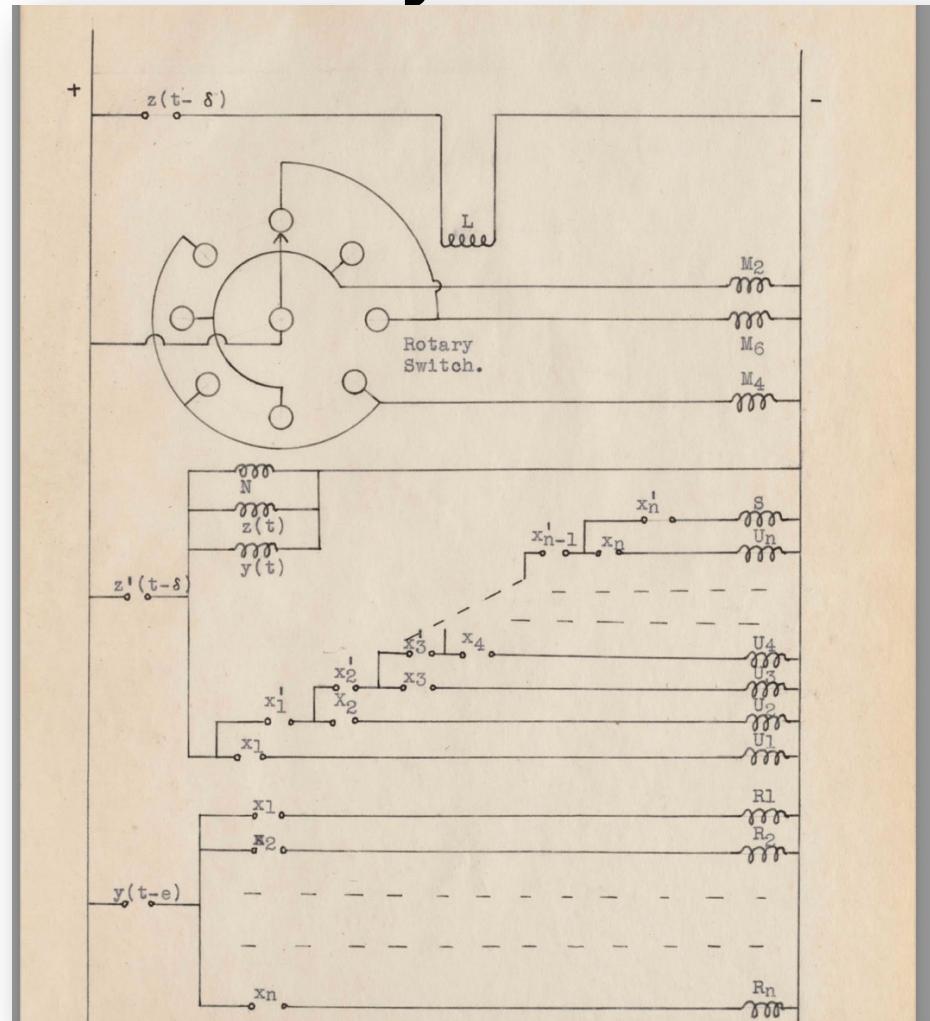
# Includes Schematic for System

- It is legit but still a little bit of a thought-experiment at the end




# Final Mic Drop

- Conservatively estimates that his circuit could...

As to the practicability of such a device, it might be said that J.P. Kulik spent 20 years in constructing a table of primes up to 100,000,000 and when finished it was found to contain so many errors that it was not worth publishing. The machine described here could probably be made to handle 5 numbers per second so that the table would require only about 2 months to construct.

# Return to Claude

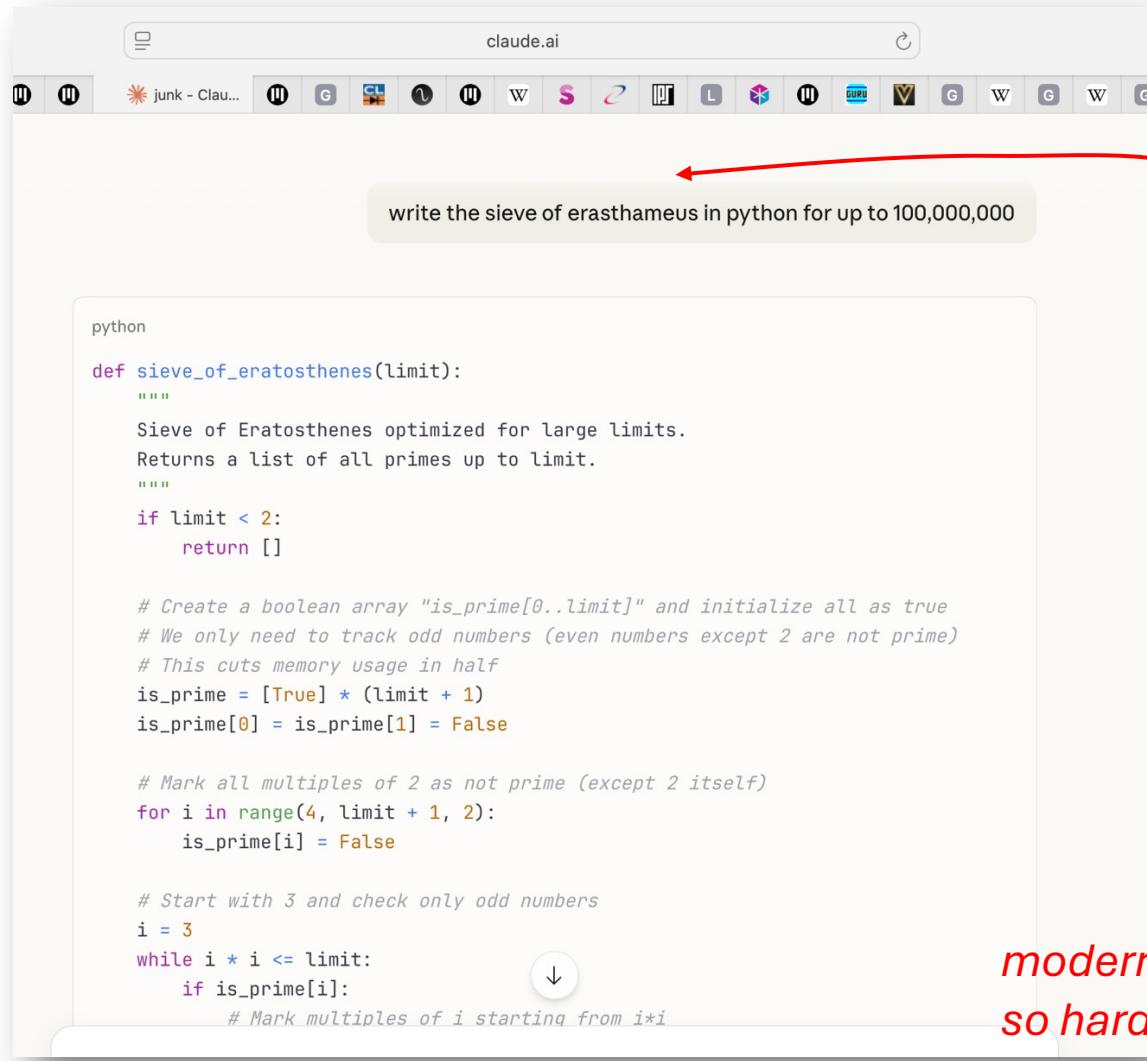

claude.ai

junk - Clau...

write the sieve of erasthameus in python for up to 100,000,000

```
python

def sieve_of_eratosthenes(limit):
    """
    Sieve of Eratosthenes optimized for large limits.
    Returns a list of all primes up to limit.
    """
    if limit < 2:
        return []

    # Create a boolean array "is_prime[0..limit]" and initialize all as true
    # We only need to track odd numbers (even numbers except 2 are not prime)
    # This cuts memory usage in half
    is_prime = [True] * (limit + 1)
    is_prime[0] = is_prime[1] = False


    # Mark all multiples of 2 as not prime (except 2 itself)
    for i in range(4, limit + 1, 2):
        is_prime[i] = False

    # Start with 3 and check only odd numbers
    i = 3
    while i * i <= limit:
        if is_prime[i]:
            # Mark multiples of i starting from i*i
            for j in range(i * i, limit + 1, i):
                is_prime[j] = False
```

modern typo...life is so hard

# Run it

- Hmm...

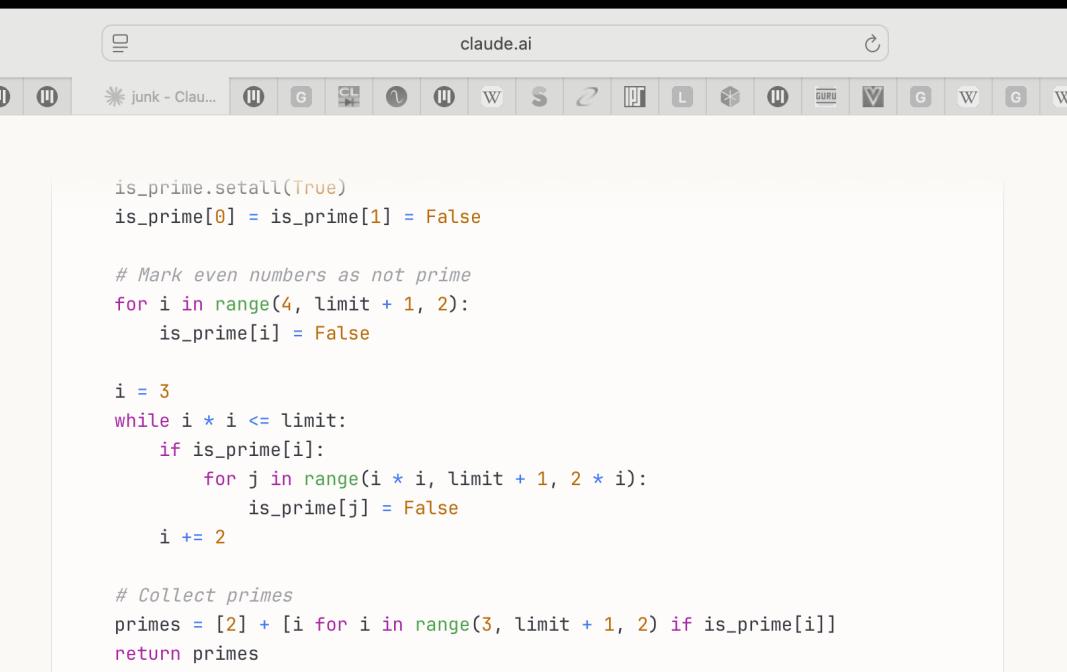

```
is_prime.setall(True)
is_prime[0] = is_prime[1] = False

# Mark even numbers as not prime
for i in range(4, limit + 1, 2):
    is_prime[i] = False

i = 3
while i * i <= limit:
    if is_prime[i]:
        for j in range(i * i, limit + 1, 2 * i):
            is_prime[j] = False
    i += 2

# Collect primes
primes = [2] + [i for i in range(3, limit + 1, 2) if is_prime[i]]
return primes
```


The first version uses ~100MB RAM and takes 5-10 seconds on a modern CPU. The bitarray version uses ~12.5MB RAM. Both will find all 5,761,455 primes up to 100 million.



```
jodalyst@jodalysts-MacBook-Air ~ % python3 sieve.py
Finding all primes up to 100,000,000...
Found 5,761,455 primes in 7.05 seconds
First 10 primes: [2, 3, 5, 7, 11, 13, 17, 19, 23, 29]
Last 10 primes: [99999787, 99999821, 99999827, 99999839, 99999847, 99999931, 99999941, 99999959, 99999971, 99999989]
Largest prime: 99,999,989
jodalyst@jodalysts-MacBook-Air ~ %
```

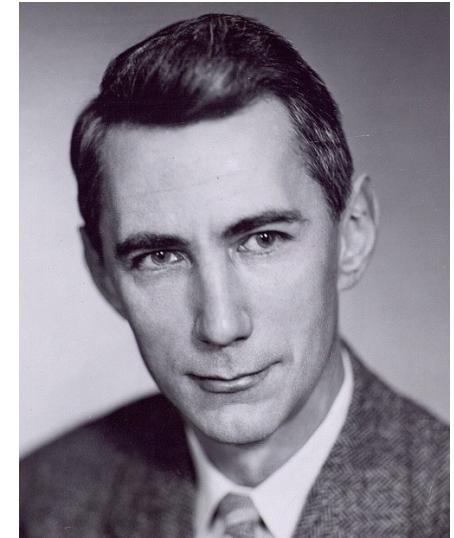
# Claude Shannon

- After his MS thesis, the guy never really did anything else. Kinda peaked in college and burned out.
- JK JK jk JK JK



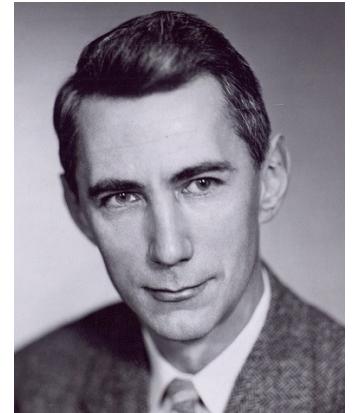
# Unbelievable

- Got to work with Einstein during internship at Princeton
- Worked at Bell Labs
- Invented signal-flow graphs
- Proved one-time-pad cryptographic security
- Developed *all* of information theory
- Defined what a bit is
- Foundational work in NLP
- Early implementations of AI and Maze-learning
- Faculty at MIT from 1950s to late 1970s.


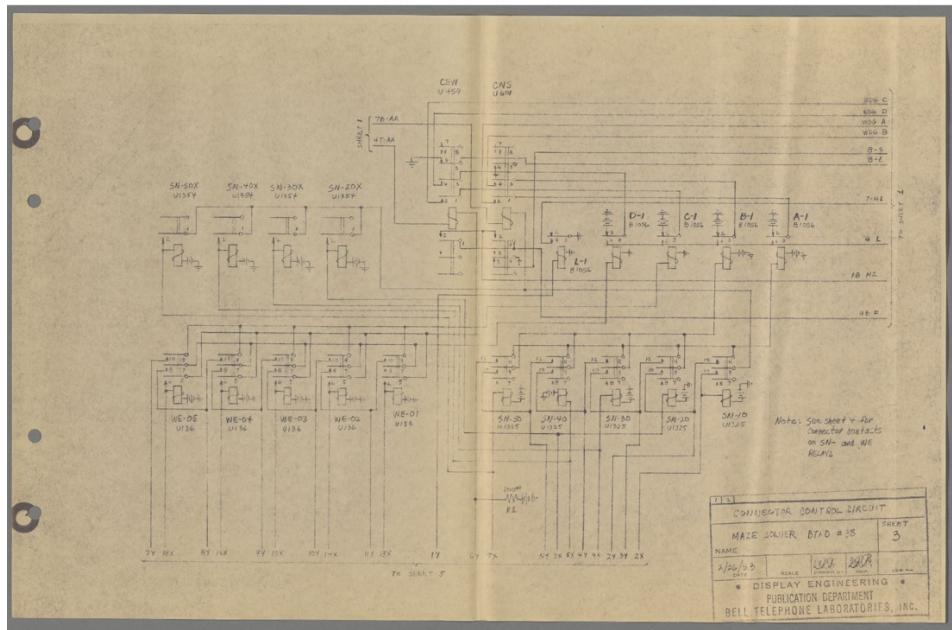
# Theseus by Claude

- Early maze-solving mouse design built entirely using relay logic




<https://mitmuseum.mit.edu/collections/object/2007.030.001>



~1953

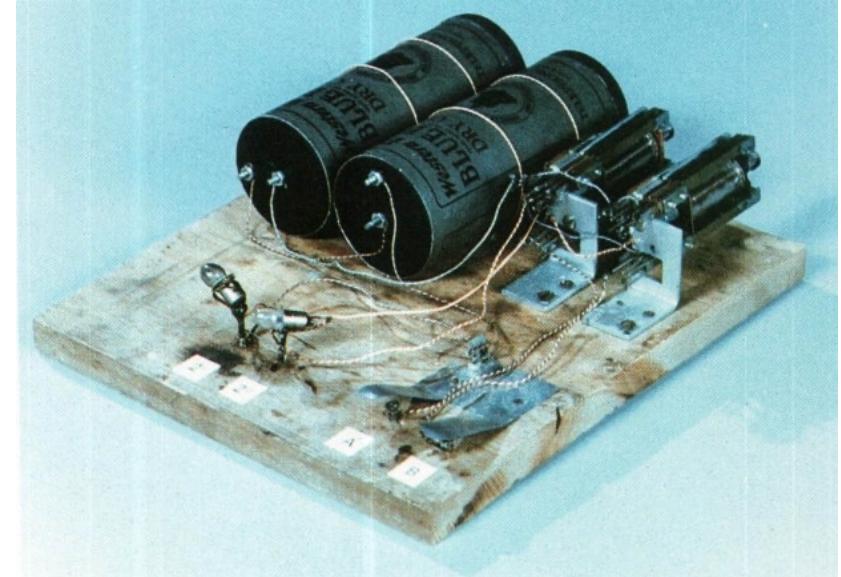
# Relay Logic Really Took Off

- Relays were so ubiquitous and robust thanks to AT&T that coupled with Shannons theory, digital design really expanded rapidly.
- In 1937, George Stiblitz at Bell Labs took two relays, wired them up in a weird way and could add two base-2 numbers



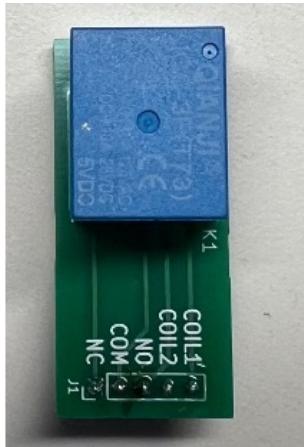
# Computation with Relays

- You really can do all modern digital logic that we see around us with relays.
- Have some easy to use “modern” relay modules for you to mess with



SPDT relay


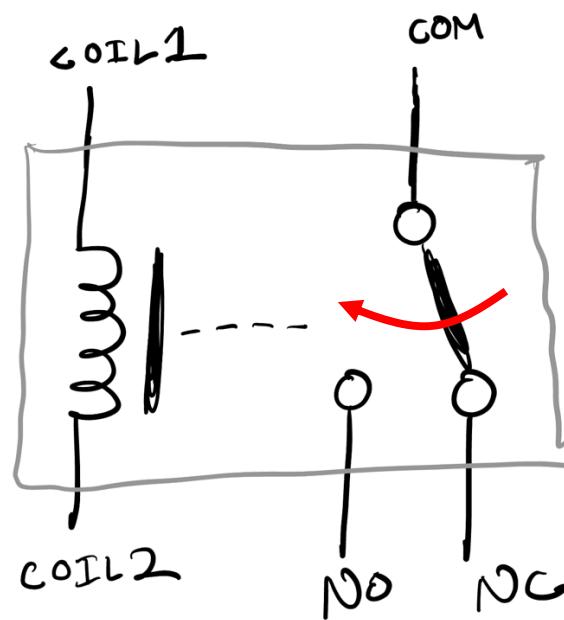


# Consider this Circuit

- Inputs are A and B
- $C = f(A, B)$ . What is f?

- $f(0,0) = 0$
- $f(0,1) = 0$
- $f(1,0) = 0$
- $f(1,1) = 1$


- AND function!

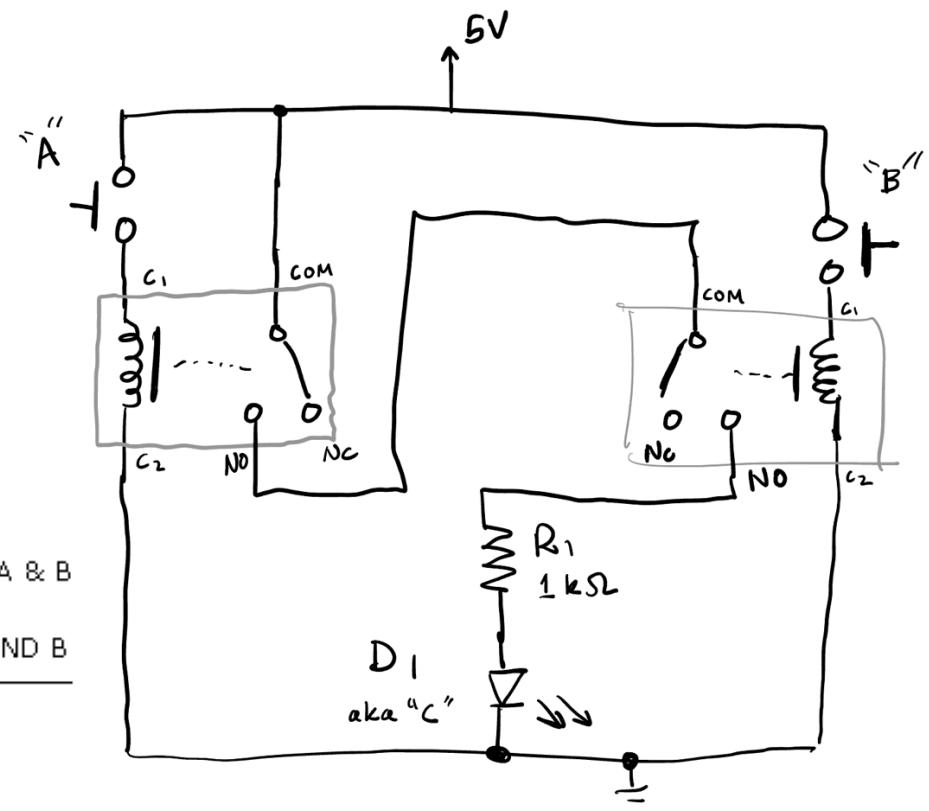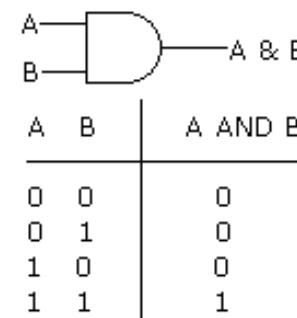

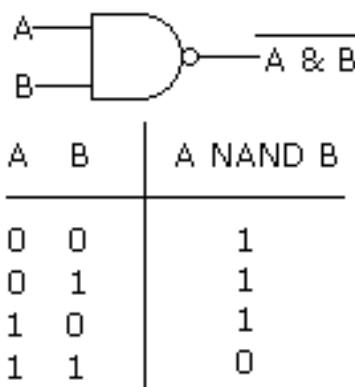
# Now this one...

- Inputs are A and B
- $C = f(A, B)$ . What is f?

- $f(0,0) = 1$
- $f(0,1) = 1$
- $f(1,0) = 1$
- $f(1,1) = 0$



- Not-AND...I function!


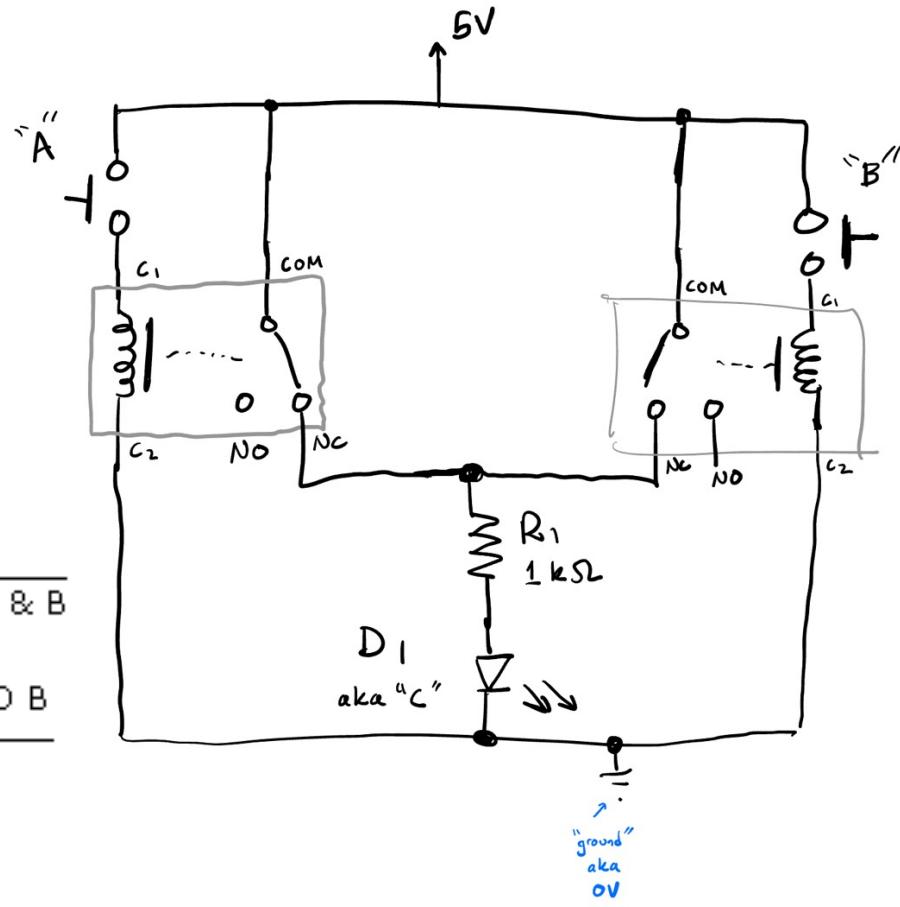


# And this one...

- Inputs are A and B
- $C = f(A, B)$ . What is f?


- $f(0,0) = 1$
- $f(0,1) = 0$
- $f(1,0) = 0$
- $f(1,1) = 0$

- Not-OR...N

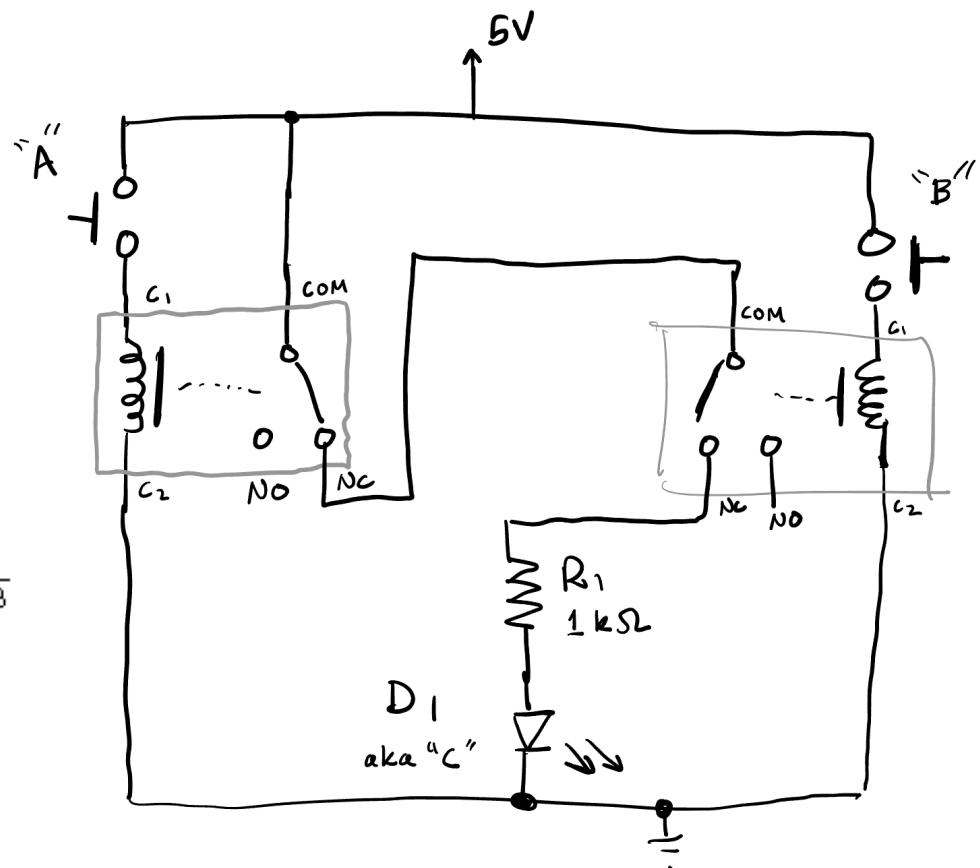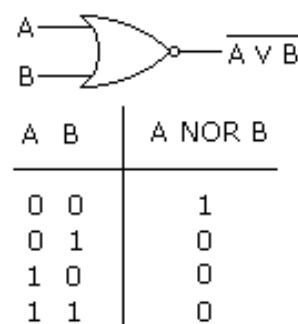

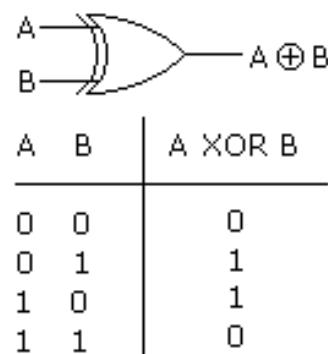
# Now this nasty one...

- Inputs are A and B
- $C = f(A, B)$ . What is  $f$ ?
  - $f(0,0) = 0$
  - $f(0,1) = 1$
  - $f(1,0) = 1$
  - $f(1,1) = 0$




- Either-Or-but more...Exclusive aka XOR

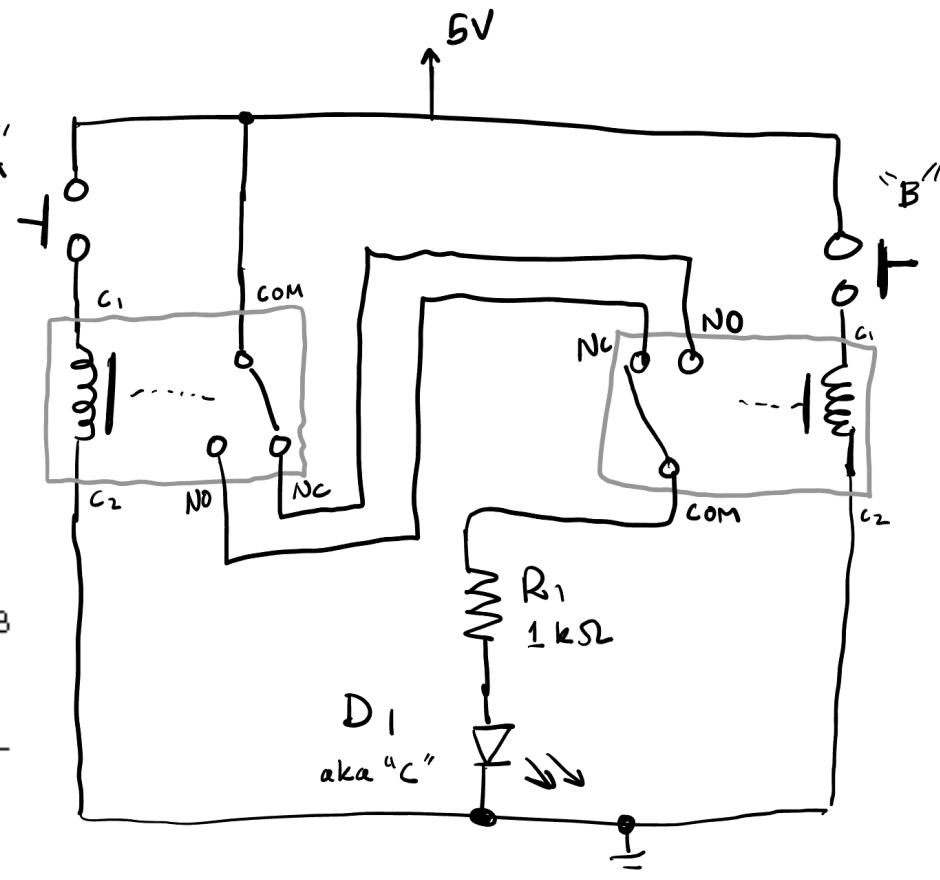


# Lab 1A


- Electromechanical Digital Logic

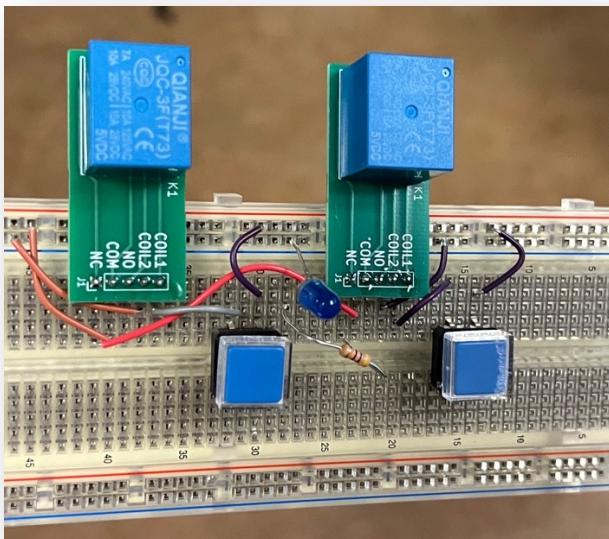

Relay-only NAND Gate

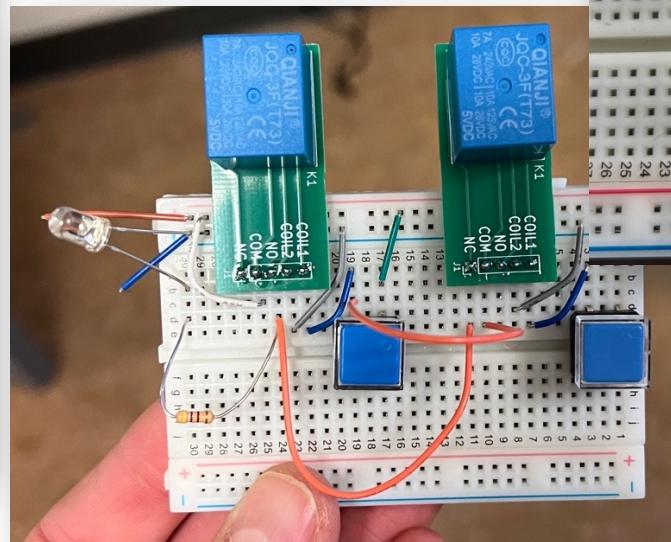

Relay-only SR Latch

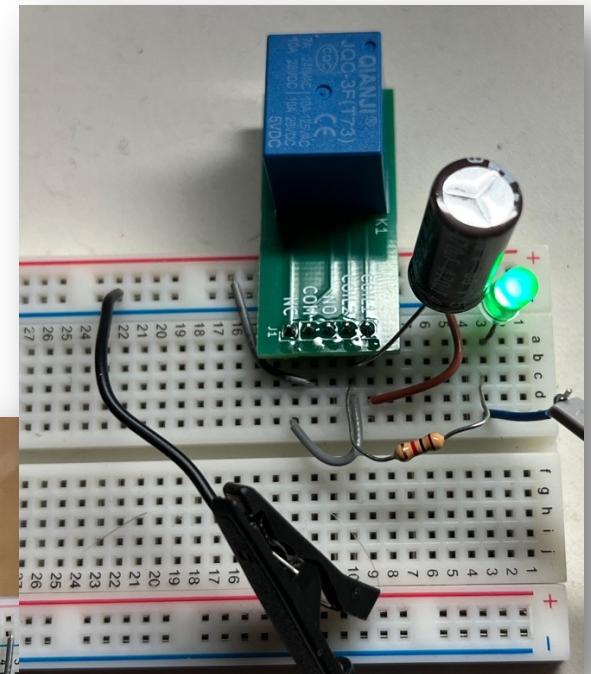

Relay-only oscillator

# Zuse computers

- German engineer who built fully-functioning computers with floating point operations using ONLY relays.


Zuse Z11



[https://en.wikipedia.org/wiki/Z11\\_\(computer\)](https://en.wikipedia.org/wiki/Z11_(computer))
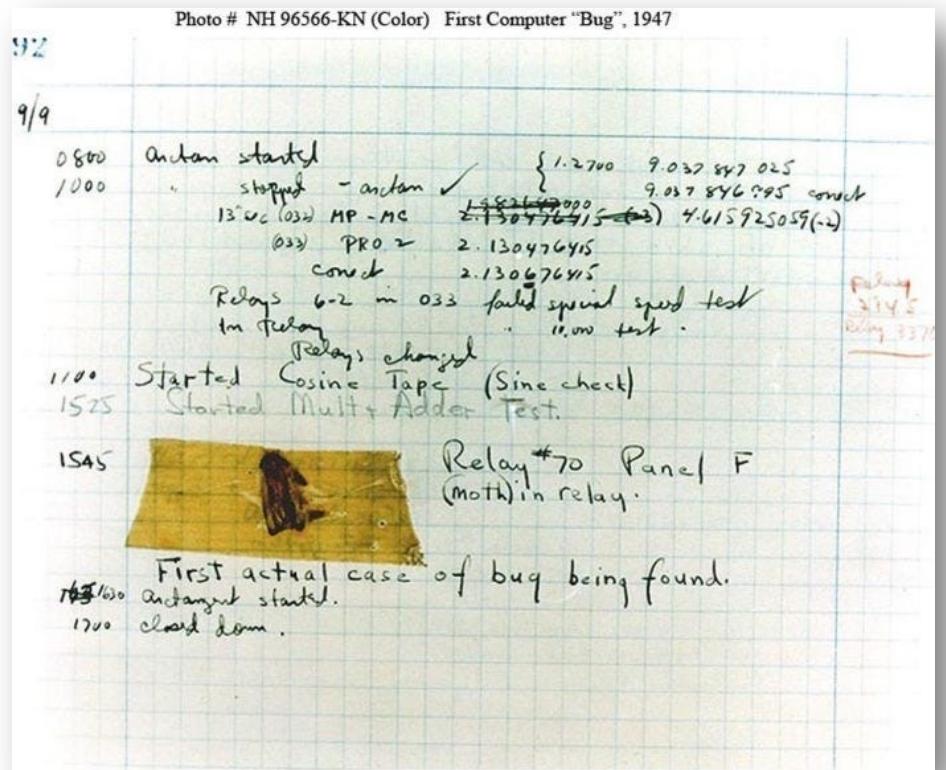
# First "Bug"


- A moth got crushed under a relay contact in Harvard's Mark II relay-based computer
- Its guts prevented the switch from closing.
- Often claimed that this was Grace Hopper's discovery
- Real story is more complicated




<https://lunduke.substack.com/p/the-story-of-the-first-computer-bug>
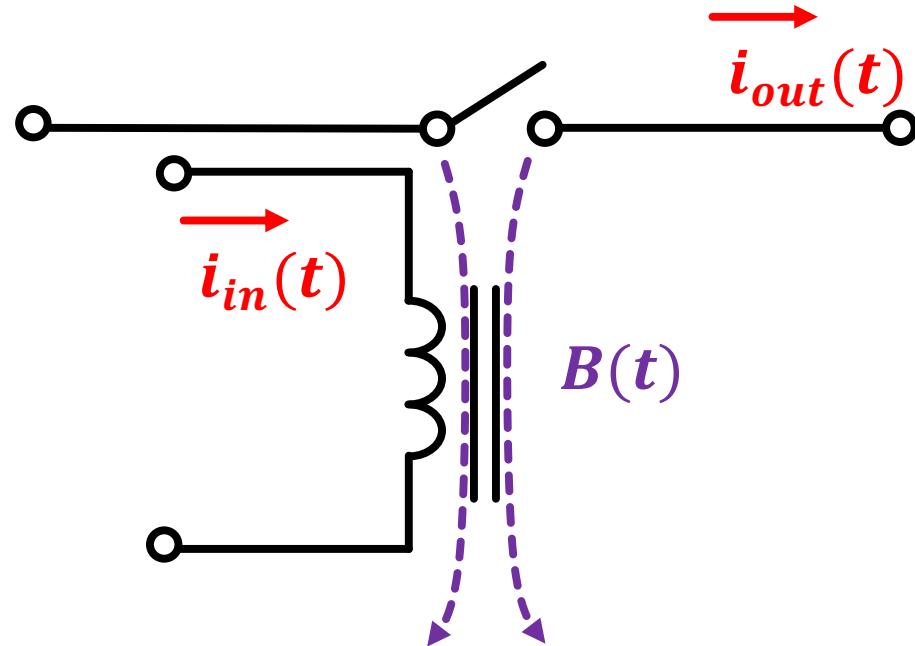
# Relays Really Are the *Ideal* Digital Component

- It is *literally* an electrically-controlled switch.


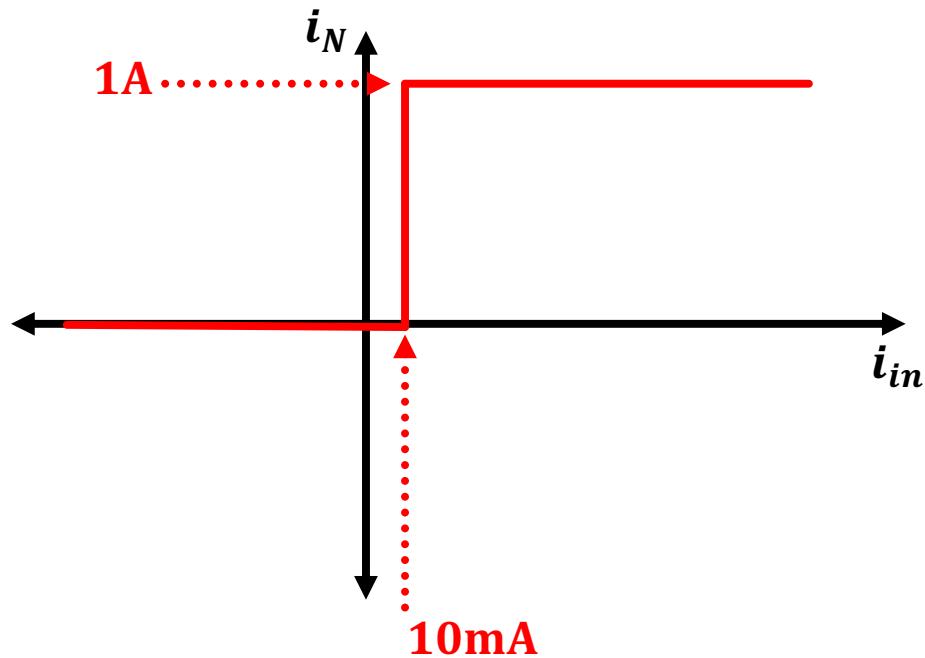
# What are some Characteristics of this I/O Relationship?




- Reliably and Reproducibly Nonlinear!
- Amplifies!
- It is essentially exactly what we want for digital logic.

*This is what gives us the Boolean Algebra in circuit form!*
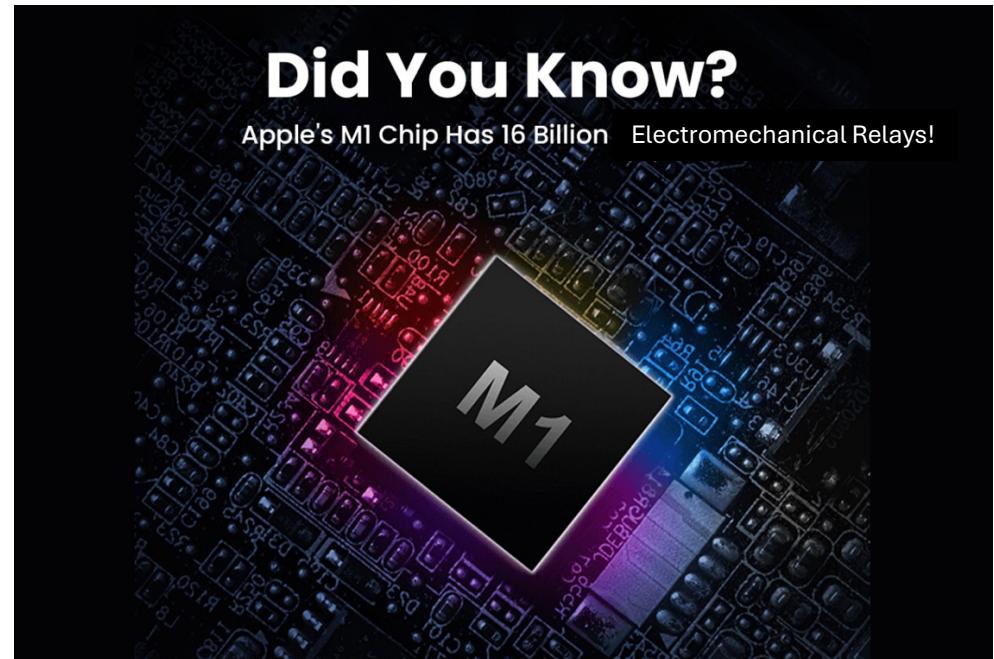
# And so that's how our story ends...


- The next eighty years of engineering was focused on making better and better electromechanical relays.



*I also remember a couple years back when all the 6-1's got pissed that they removed a mandatory class in electromechanical relays from the curriculum.*

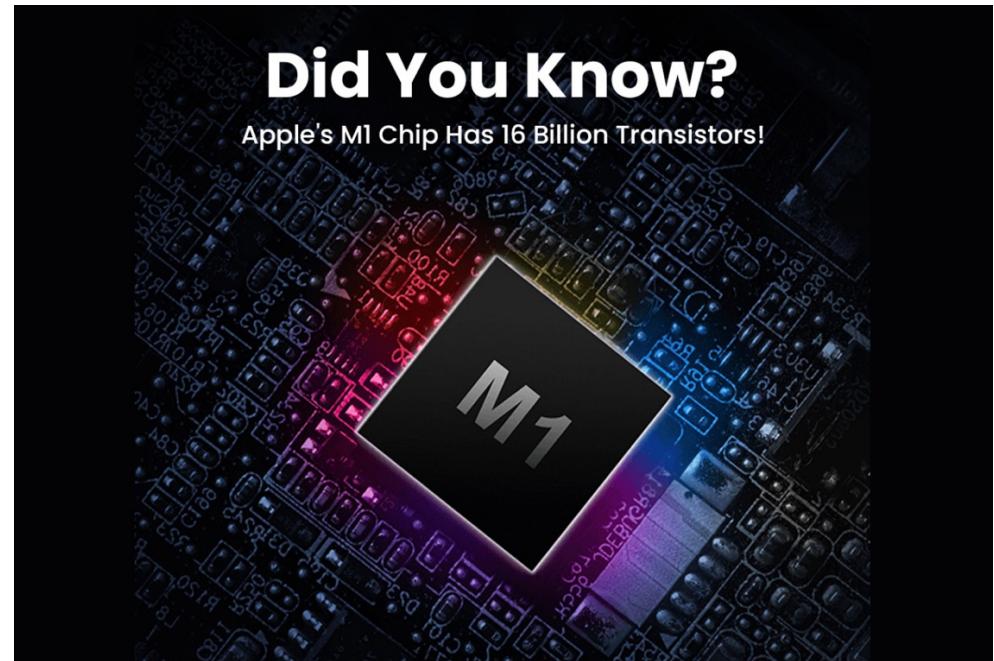
# JK JK JK JK...wrong timeline

- The next eighty years of engineering was focused on making better and better electromechanical relays.



*I also remember a couple years back when all the 6-1's got pissed that they removed a mandatory class in transistors from the curriculum.*

# Problems with Relays?

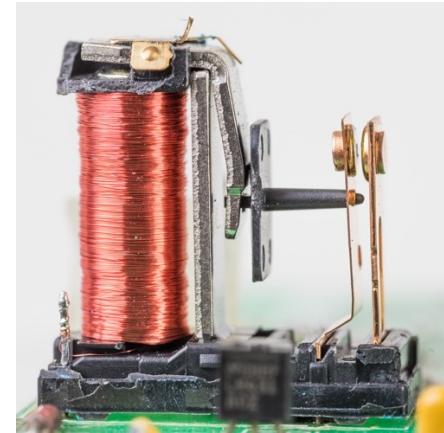


- They are **electromechanical** devices so they are pretty slow (never could operate at GHz...or MHz...and barely kHz) X
- Relays can be made to be pretty robust, but still...Course 2 almost always lets us down eventually (mechanical contact wear in extreme cases) X
- Use a lot of powers X
- Very hard to scale down X

# How to Fix?

- Everything in digital circuit design since Relays have really been less ideal\*.
- Vacuum Tubes, Diodes, Transistors...
  - All of these technologies aren't actually electrically-controlled switches where the flow of electricity can turn on/off another flow...
  - They are analog devices that can be incorporated into circuits that approximately act that way within certain ranges of operation.
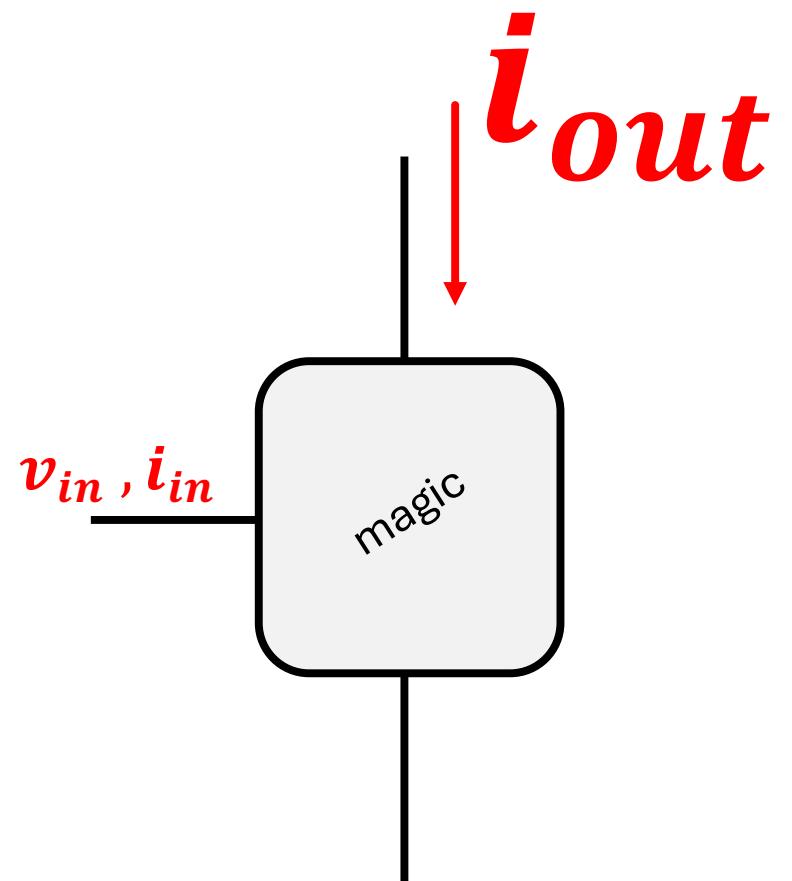
# What was wanted...

- Some magical device that could quickly and cheaply and robustly allow a small electrical signal to modulate a **BIG** electrical signal
- Just like a relay but better



# First Attempt: Vacuum Tubes




- Vacuum Tubes were invented around 1906 and were the first purely electronic amplifying device.
- Could be used to operate as electrically controlled switches
- Could be made to operate at higher speeds (MHz) 
- On a per-operation basis, were more robust and more power efficient than relays 
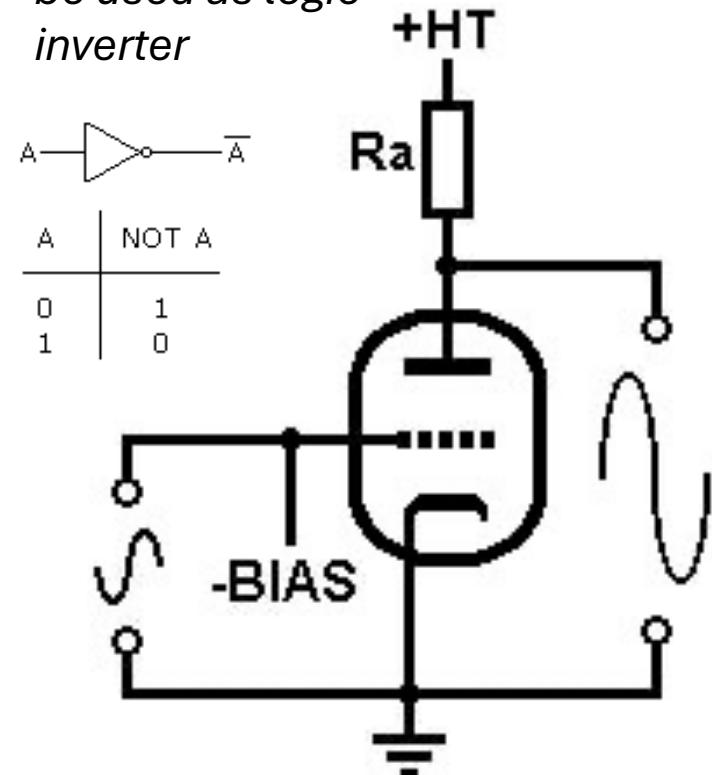
# First Attempt: Vacuum Tubes

- Downsides:
  - Needed hundreds of volts to operate
  - Pretty delicate and could fail regularly
  - Couldn't really scale (easily)
- Also...vacuum tubes weren't actually electrically controlled switches...they were analog devices....they could only kind of act like that in certain situations. Had to build them into circuits that approximated switching behavior



*Tube amplifier could be used as logic inverter*



<https://www.valvewizard.co.uk/gainstage.html>


# Second Attempt: Semiconductor Diodes

- Early passive semiconductor devices

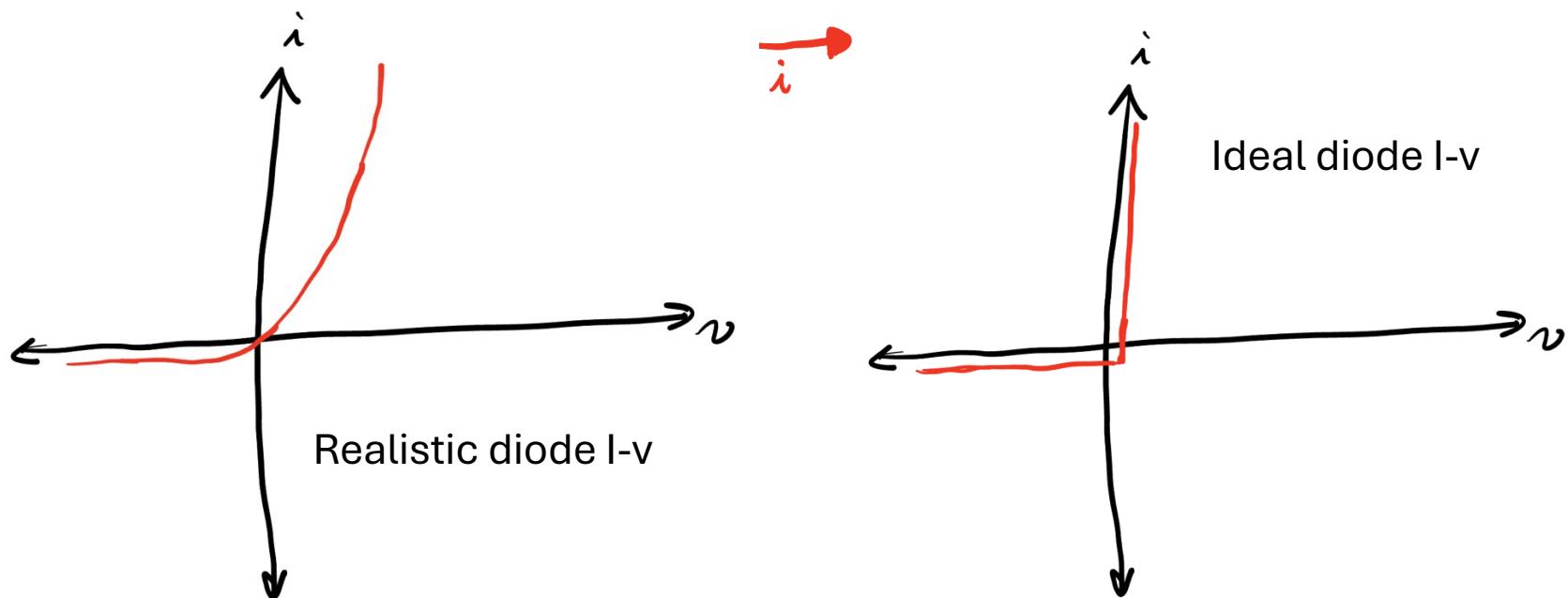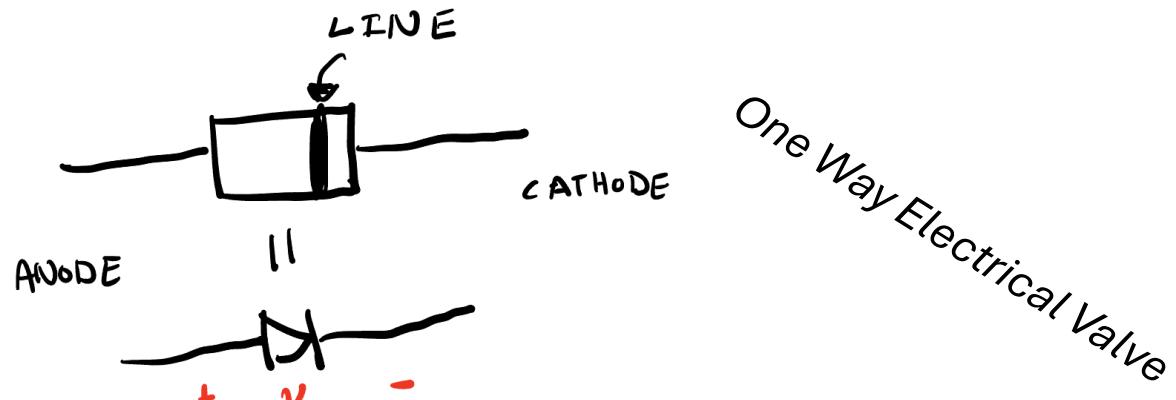
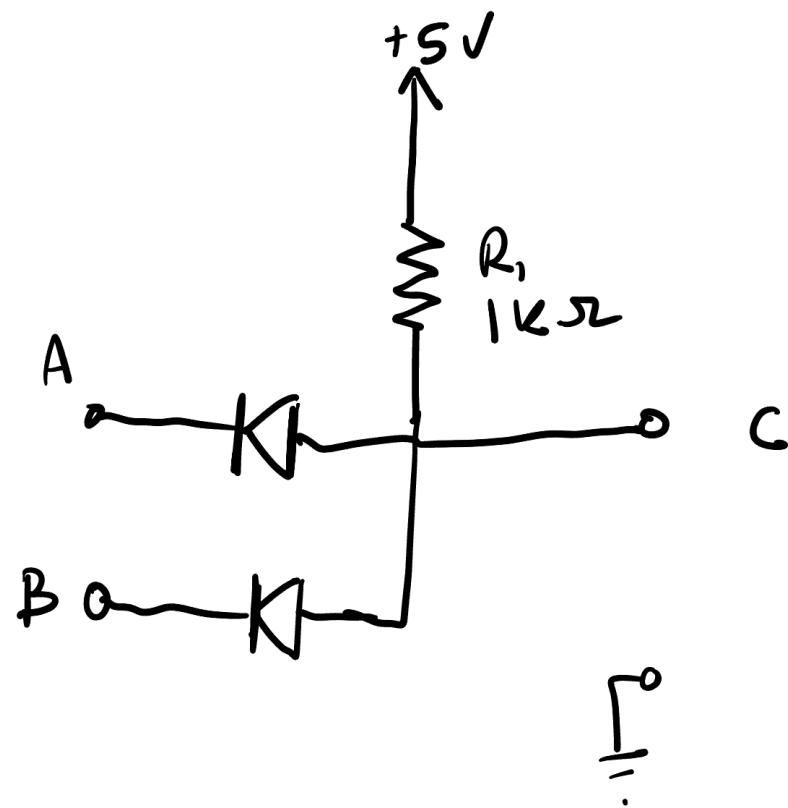
# Second Attempt: Semiconductor Diodes


- Could incorporate them into circuits...




# Second Attempt: Semiconductor Diodes

- Analyze using ideal diode behavior


$$\underline{A = 0V \quad B = 0V}$$

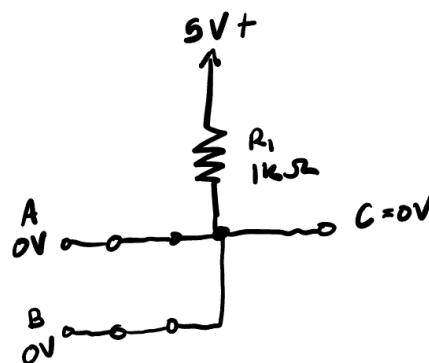



$$\underline{A = 0V \quad B = 5V}$$

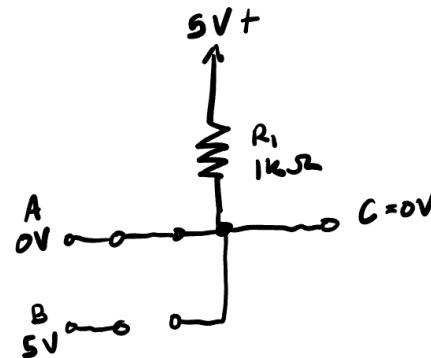

$$\underline{A = 5V \quad B = 0V}$$

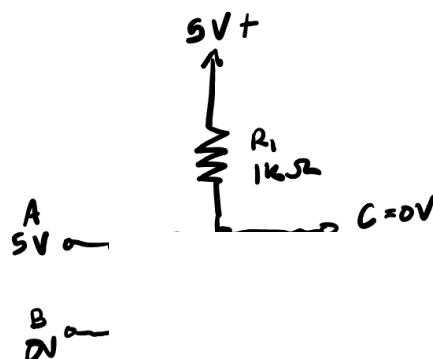

$$\underline{B = 5V}$$

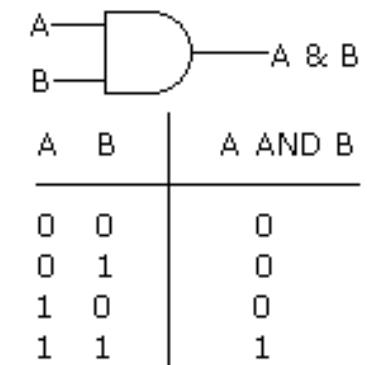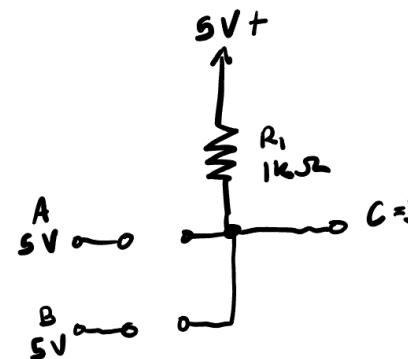

# Second Attempt: Semiconductor Diodes

- Benefits:

- Small
- Low voltage
- Power efficient
- Fast




- Bad things:

- Could not amplify...so actually could not do logical inversion (NAND, NOR, NOT)...so...as we'll see...couldn't do all logic.




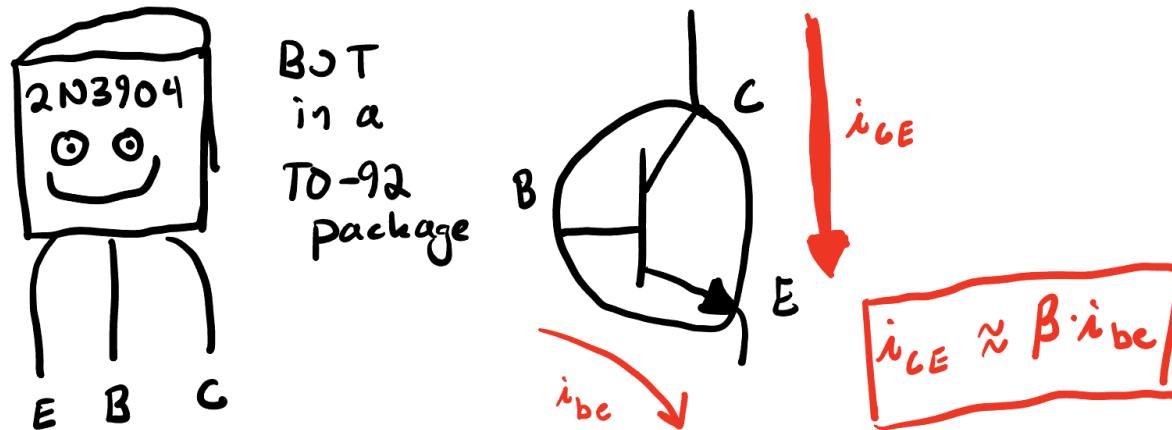
# Third Attempt: Transistors (1947)

- Like a low-voltage, fast, scalable vacuum tube.
- Transistors on their own were not digital.
- You had to build them into special circuits that could be used in a digital way.





# Different Flavors of Transistor Design

- First there was Diode-Transistor Logic

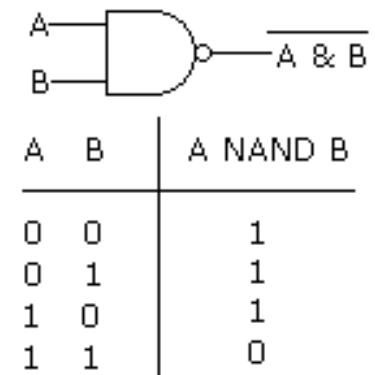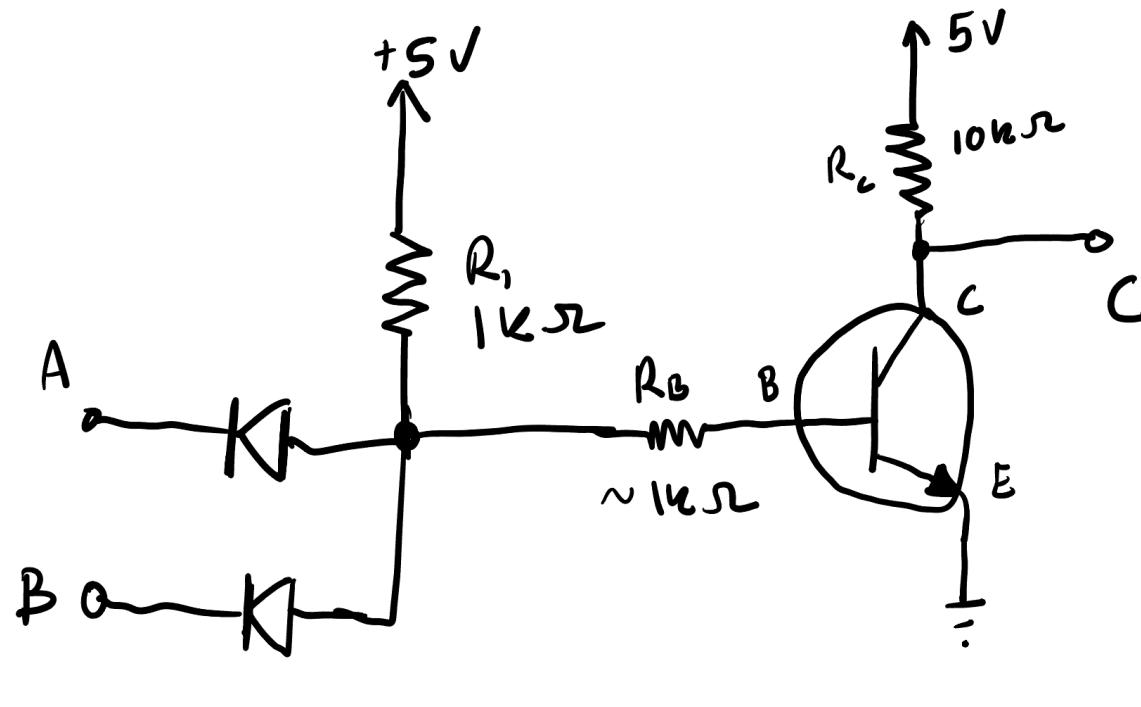

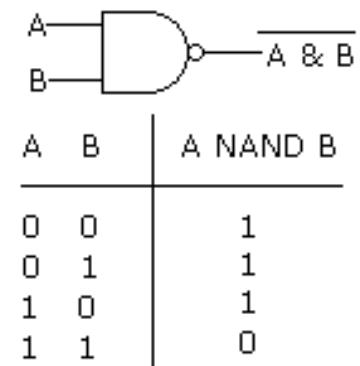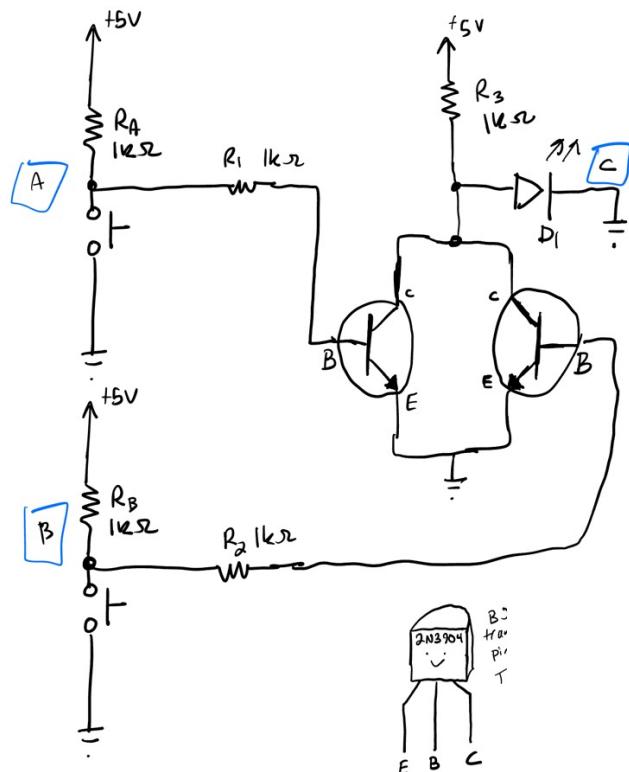
# Different Flavors of Transistor Design

- Then there was Resistor-Transistor Logic


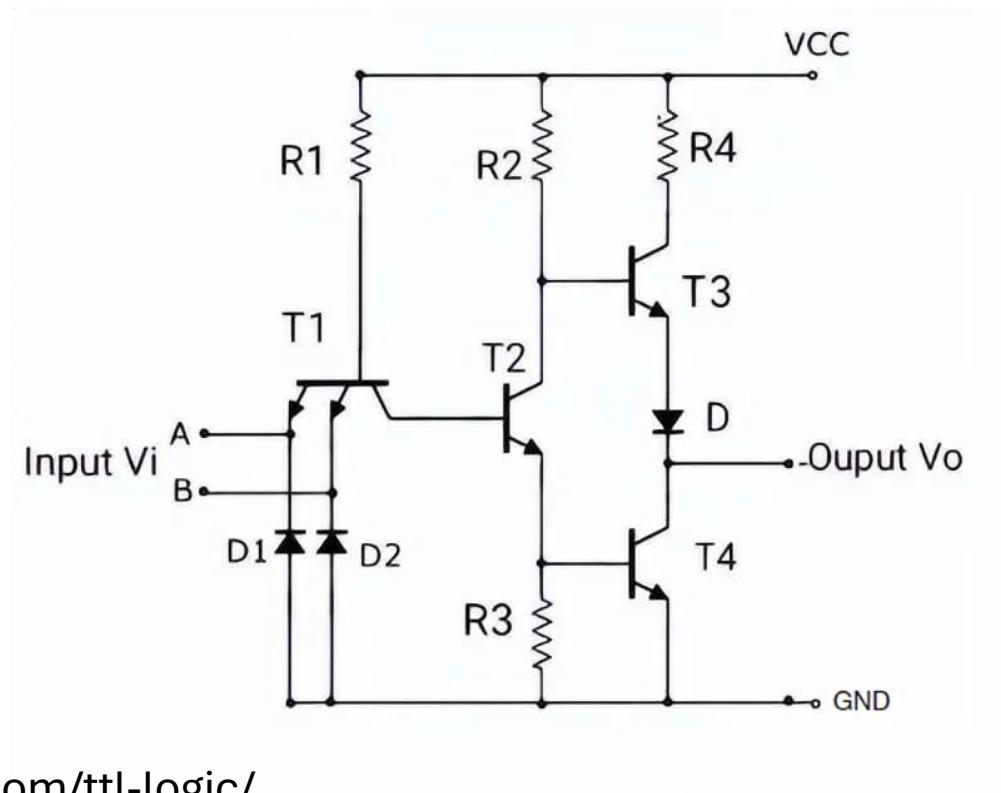
# Different Flavors of Transistor Design

- Then there was Transistor-Transistor Logic



<https://reversepcb.com/ttl-logic/>

# Different Flavors of Transistor Design

- Then there was Complementary-Metal Oxide Semiconductor Circuits (CMOS)
- This was a new thing with transistors! You could have transistors that worked in opposite ways!!!


# P and N channel devices

*Voltage at Gate  
(G)...modulates D-S  
current*

P -Channel



N-Channel


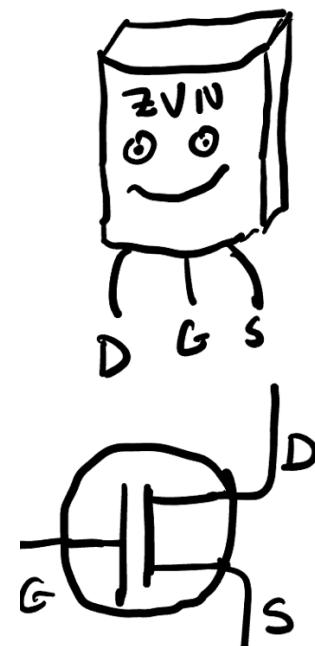


Complementary



When  $v_G$  High, SD no connected  
When  $v_G$  Low, SD connected

When  $v_G$  High, SD connected  
When  $v_G$  Low, SD no connected

# CMOS circuits (Inverter)

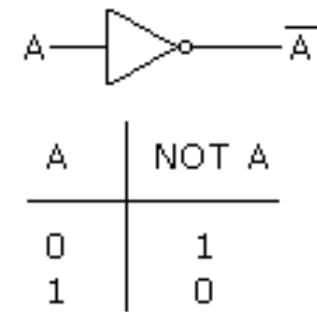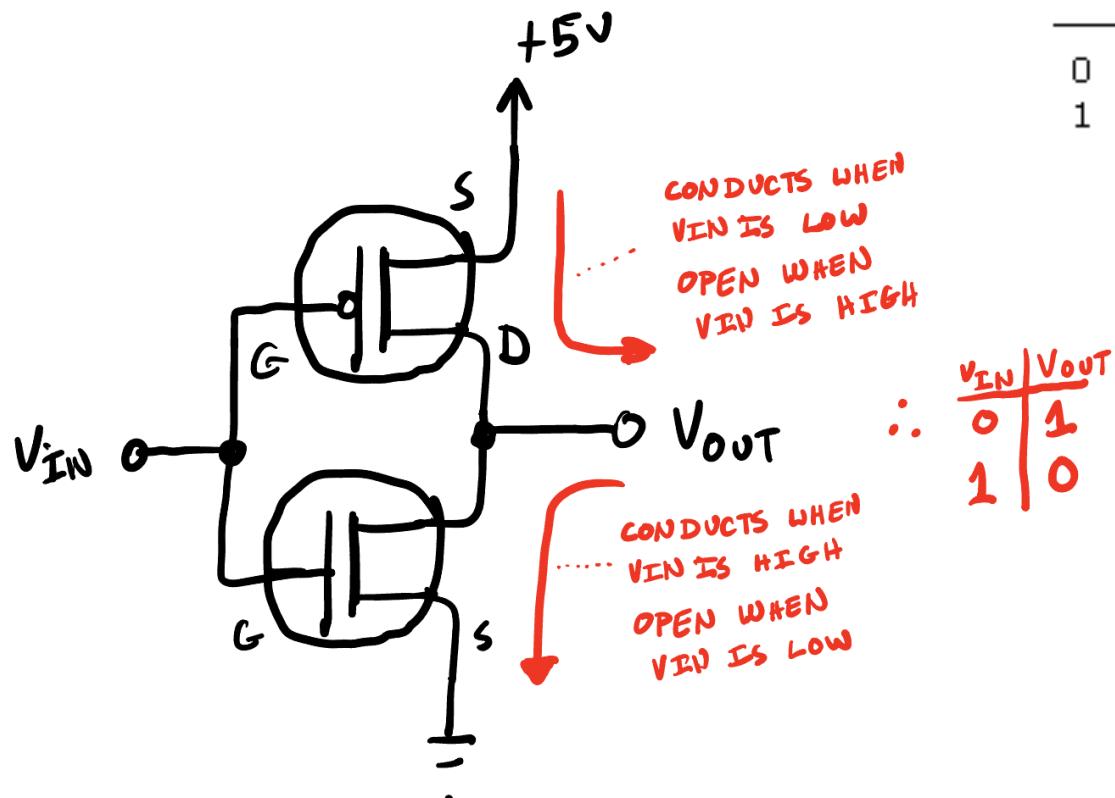

# CMOS Gate

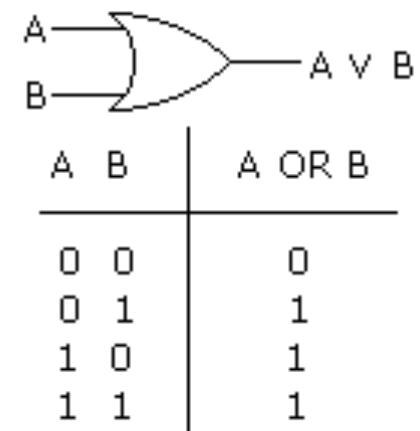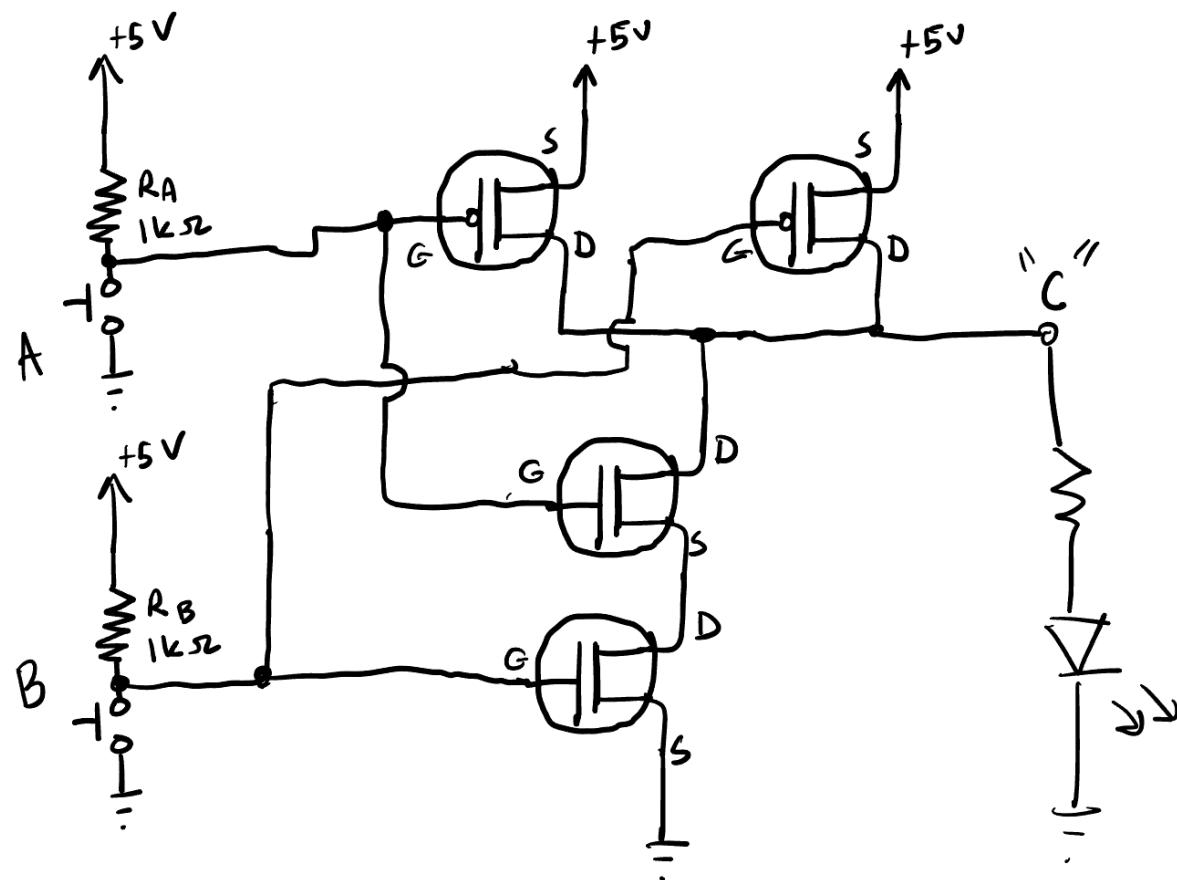


# Transistor (CMOS) Benefits

- Benefits:
  - Low voltage
  - Very Power efficient
  - Fast
  - **Could be scaled down in size! (exponentially so)**
- Downsides:
  - On their own, they are not digital devices. We have to incorporate them into specialized circuits.
  - Always fighting against their inherent analog nature.
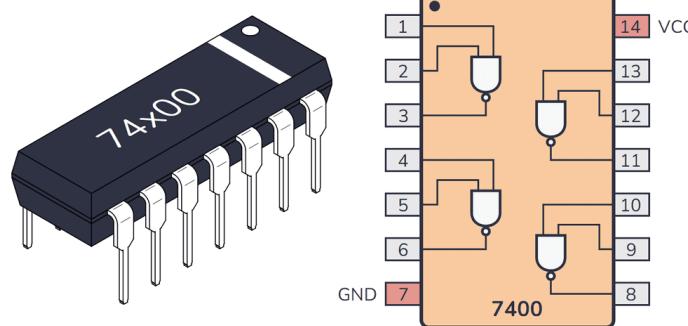
# Scaling...

- Transistors could be made so small that by the 1960s they could start to merge multiple transistors into single devices and package them together.
- Didn't have to build the gates anymore...you could just buy them and stick them together like lego bricks



# Lab 1B

- Electrical-only Logic Gates


CMOS OR Gate



CMOS NOT Gate



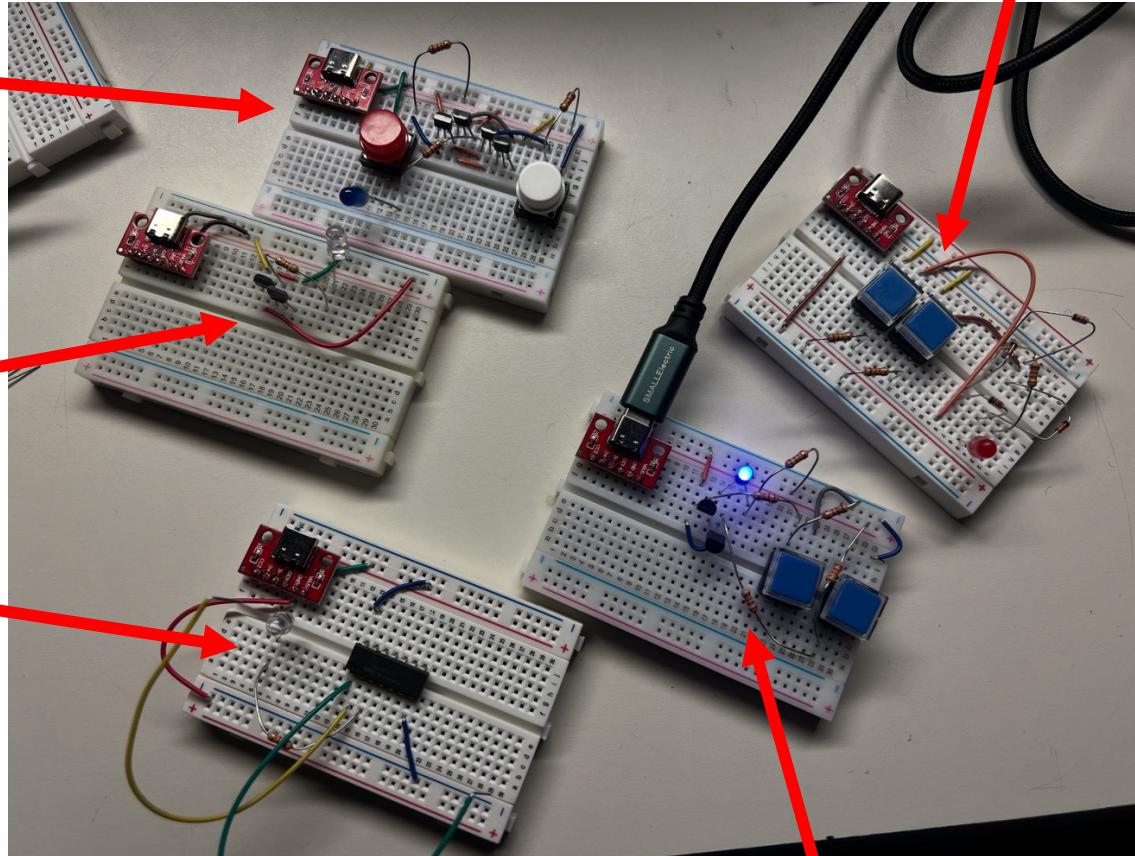All-included  
integrated quad  
XOR package



RTL NAND gate

# End

- That's where we'll end today
- Next time we'll start designing with these logical elements