

# 6.S188

Build a Digital Clock from the Eighties

Lecture 1B:  
Designing Digitally


# Ok we actually want to design stuff

- Claude Shannon showed how we could actually design complicated digital circuits using math.
- We don't use regular, normal human math\*
- We have to use Boolean Algebra/representation an algebra where things take on only one of two values (0 or 1)

*\*though what is “normal human math” really anyways, Joe?*
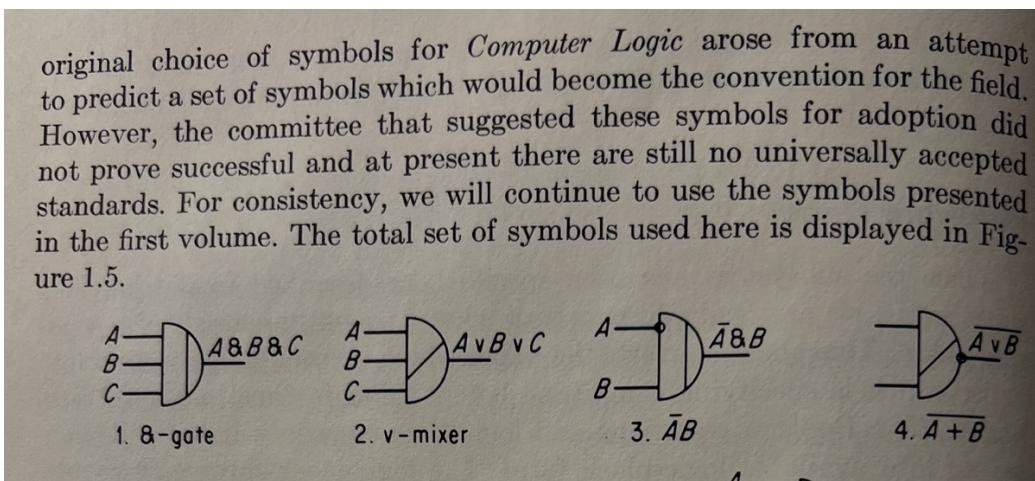
# Standardizing


- Prior to late 1950's *how* exactly you'd do digital design wasn't super streamlined.
- A lot of the logic gates weren't standardized..



*The Logic of Computer Arithmetic* Ivan Flores 1963

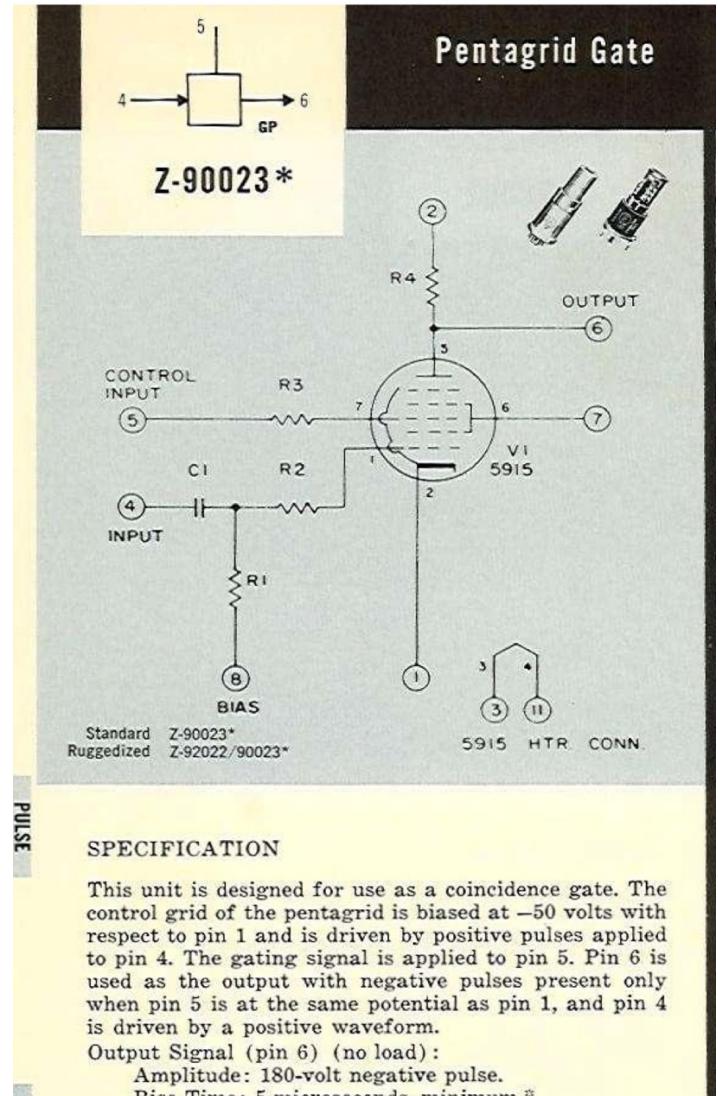
# Buying Logic

- Even prior to the late 1950's you couldn't really just happily design "logic" without intimate knowledge of the underlying circuits.
- Eventually startups started releasing logic you could buy and stick together.



506 EAST FIRST STREET  
SANTA ANA, CALIFORNIA

TELEPHONE  
Kimberley 7-5651

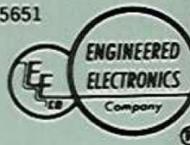

RUGGEDIZED SERIES PRICE LIST  
Effective Date: February 1, 1960

Terms, FOB point, and footnotes, e.g., ①, ②, etc., will be found at the end of the price lists.

PART NUMBERS	DESCRIPTION ③	1-9		10-24		25-49		50-99		100-199		200-499	
		1-9	10-24	25-49	50-99	100-199	200-499						
Z-92000/8336 or	Flip-Flop	14.55	14.10	13.25	12.35	10.95	10.70						
Z-92001 *		Same											
Z-92002/8339 or	Flip-Flop	14.75	14.30	13.40	12.50	11.10	10.80						
Z-92003 *		Same											
Z-92004/8342 or	Flip-Flop	14.80	14.35	13.45	12.55	11.15	10.85						
Z-92005 *		Same											
Z-92007/90052*	Flip-flop	14.05	13.50	13.05	12.55	12.00	11.50						
Z-92008/90059 or	Flip-Flop	14.75	14.30	13.40	12.50	11.10	10.80						
Z-92009 *		Same											
Z-92010/90166 *	Flip-Flop	14.95	14.45	13.65	12.65	11.20	10.90						
Z-92011/90015 *	Blocking Oscillator	21.70	21.00	20.45	19.75	18.90	18.10						
Z-92012/8318 *	One Shot	12.90	12.50	11.75	10.95	9.80	9.50						
Z-92013/8889 *	One Shot	10.90	10.60	10.00	9.35	8.35	8.15						
Z-92018/90002 or	Gate Circuit	13.60	13.20	12.40	11.55	10.30	10.05						
Z-92019 *		Same											
Z-92022/90023 *	Pentagrid Gate	11.25	10.80	10.45	10.10	9.60	9.25						
Z-92023/8321 *	Pulse Gate	10.90	10.45	10.15	9.80	9.35	8.95						
Z-92024/90001 or	Squaring Circuit	13.15	12.75	12.00	11.20	9.95	9.70						
Z-92025 *		Same											
Z-92026/90021 *	Sampling Circuit	12.65	12.15	11.75	11.35	10.95	10.40						




**\$11.25 for one AND gate in 1960...about \$130.00 in 2026 dollars**

# Transistors and Integrated Circuits

- Transistors on their own didn't scale stuff down too much.
- It was the ability to merge them into small complicated circuits using lithographic techniques that led to integrated circuits.
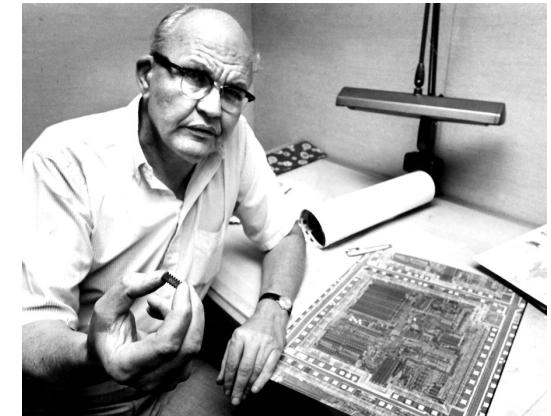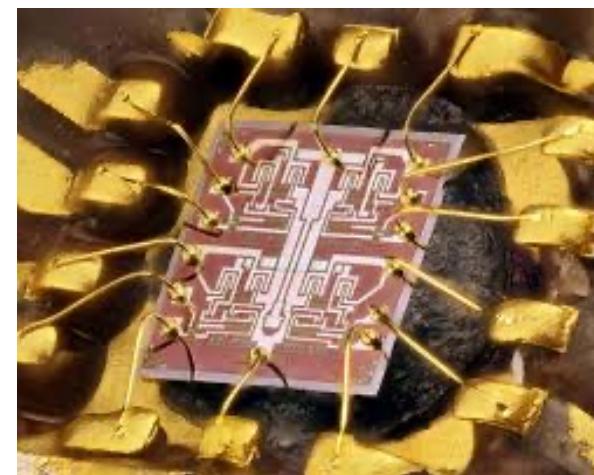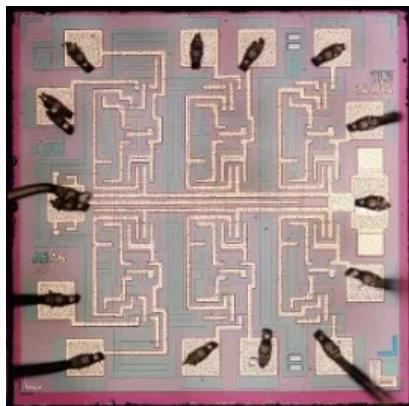
# Mid 1960s

- Texas Instruments got integrated circuits fabrication to a strong enough point that they could release devices that had multiple logic gates all in one package!



*Jack Kilby  
TI engineer...one of  
inventors of  
Integrated Circuits*

# 7400-series


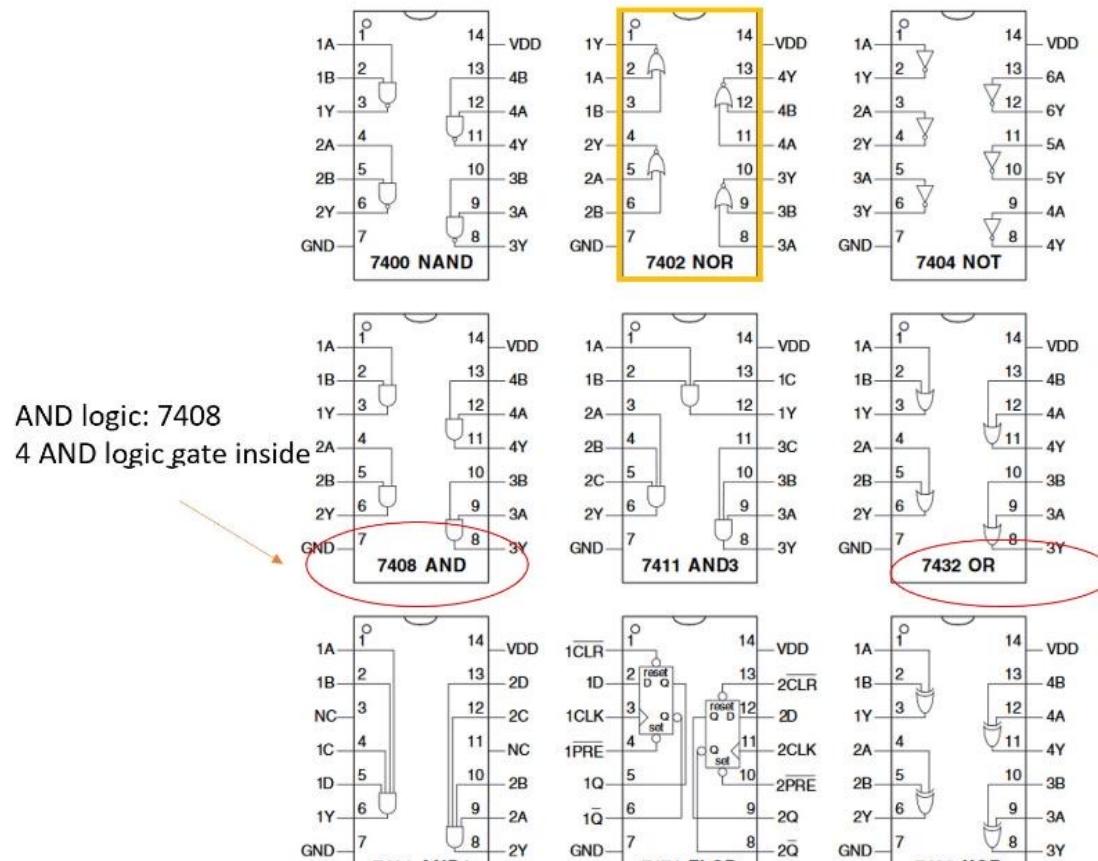


Figure eA.1 Common 74xx-series logic gates

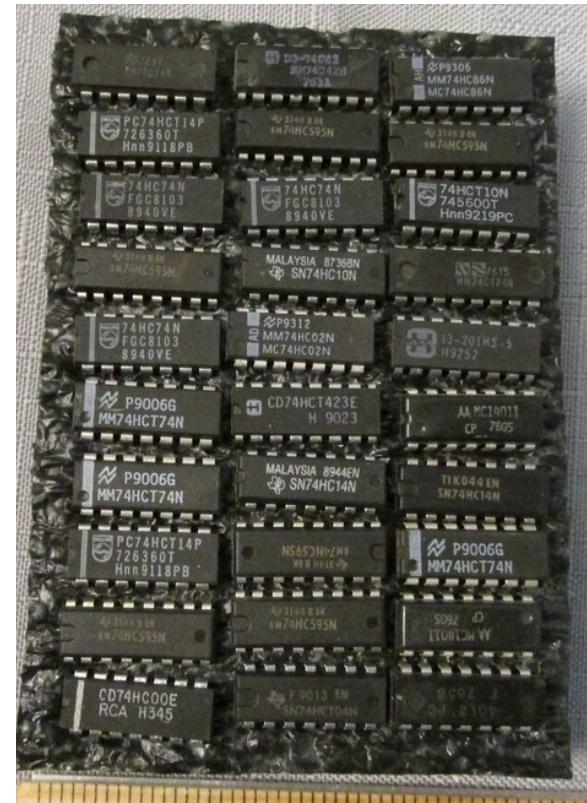


# Big Cost Savings (relatively)

- The 7400 cost \$6.65 in 1966 FOR FOUR NAND GATES...that's about \$66.50 in 2026 dollars...sooooo cheap (actually! This was a big deal)

*In 2026, an AMD Ryzen 5 5600G has the equivalent of about 2.5 billion NAND gates in it...and I saw them for like 80 bucks in December*


7400/74LS00  
Quad NAND Gate

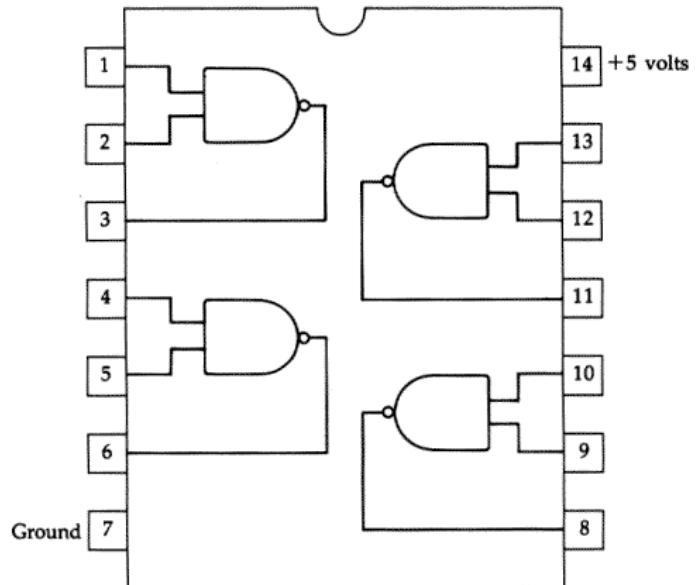

*So in 1966...you'd get 0.06 NAND gates per dollar  
In 2026, you get 31.25 million NAND gates per dollar*
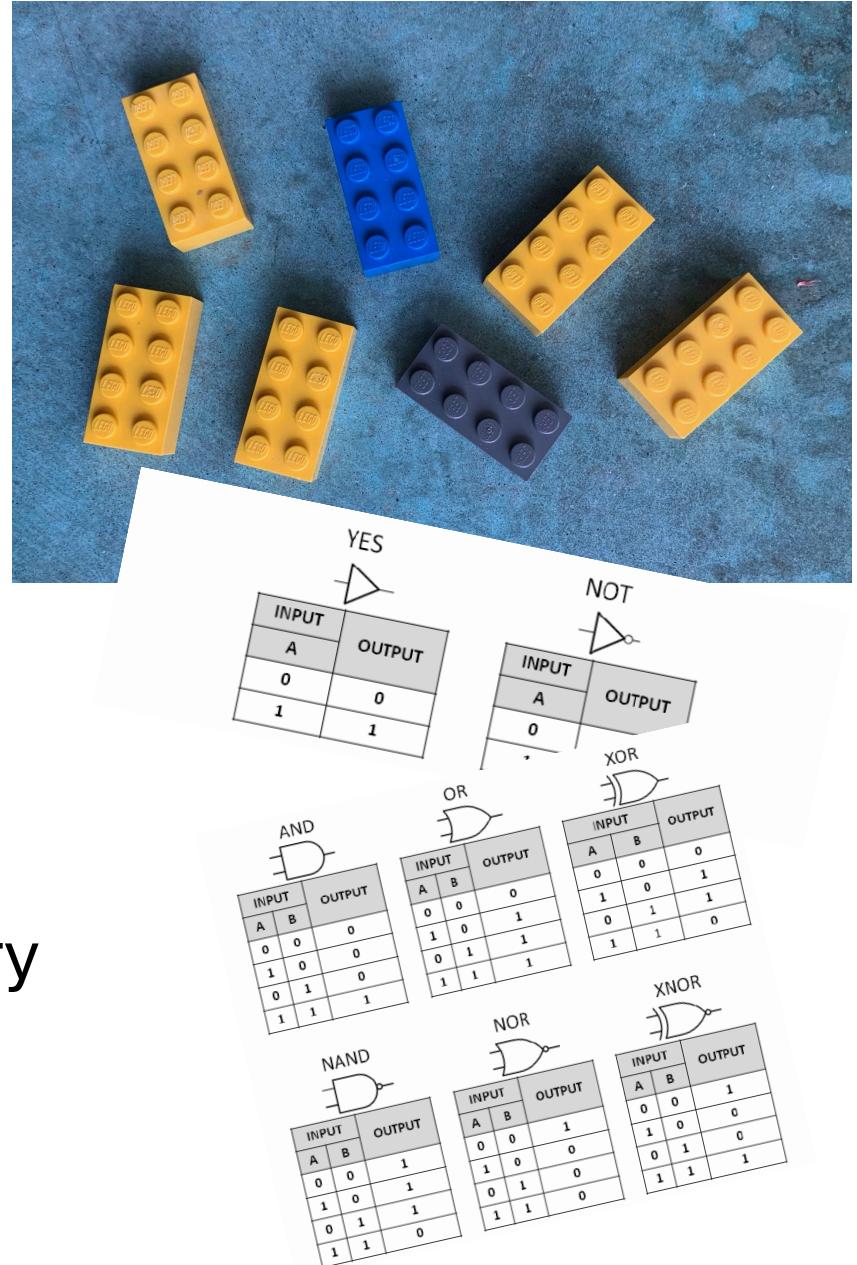
# So what did this mean?

- Design was much more accessible.
- Of course there was tons of gatekeeping.
- Older engineers would make younger engineers feel like sh\*t because they weren't having to design logic gates from scratch and had to worry less about voltage.
- Tale as old as time. Bunch of boomers



# Anyways....Let's design

- Let's design circuits as you would have in the mid 1960s and on...

# Boolean Starters

- Values are either 0 or 1.
- Can have variables like  $a$  or  $b$  (keeping in mind they can only represent 0's and 1's)
- Three core operations...
- **NOT** (logical inversion):
  - “NOT  $a$ ” is  $\bar{a}$
- **OR** (sometimes called Boolean sum):
  - “ $a$  OR  $b$ ” is  $a + b$
- **AND** (sometimes called Boolean product):
  - “ $a$  AND  $b$ ” is  $a \cdot b$  but can also implicitly:  $ab$  or  $a(b)$

NOT



INPUT	OUTPUT
A	
0	1
1	0

OR



INPUT	OUTPUT	
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

AND




INPUT	OUTPUT	
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

# Boolean Identities, Rules, Laws, Etc...

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

# The Simplest Digital Function Class

- One Bit Input:

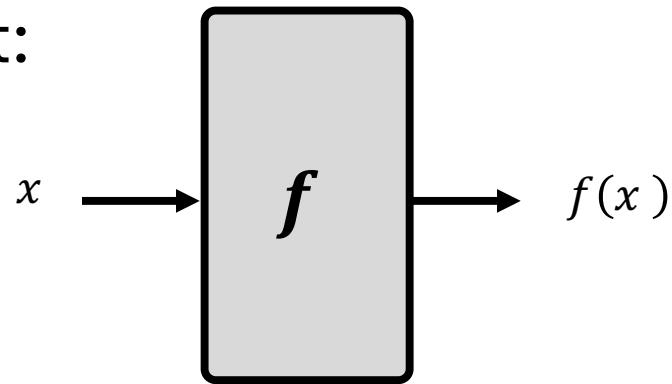


- How many possible 1-bit functions exist?

# 1-bit functions (input is a single value):

- How many possible 1-bit functions exist?
- Two (actually 4)...

Buffer (Yes) gate:

$x$	$f(x)$
0	0
1	1

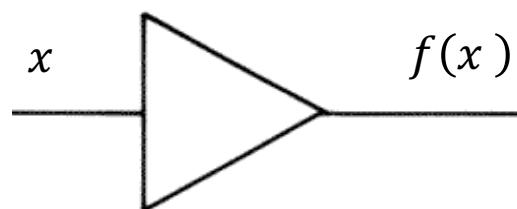


Always On gate:

$x$	$f(x)$
0	1
1	1

Inverter (Not) gate:

$x$	$f(x)$
0	1
1	0

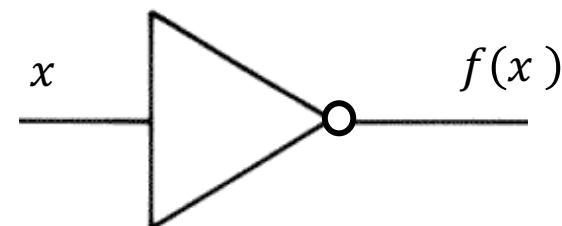


Always Off gate:

$x$	$f(x)$
0	0
1	0

# What About Two bits input?

- Two Bit Input:

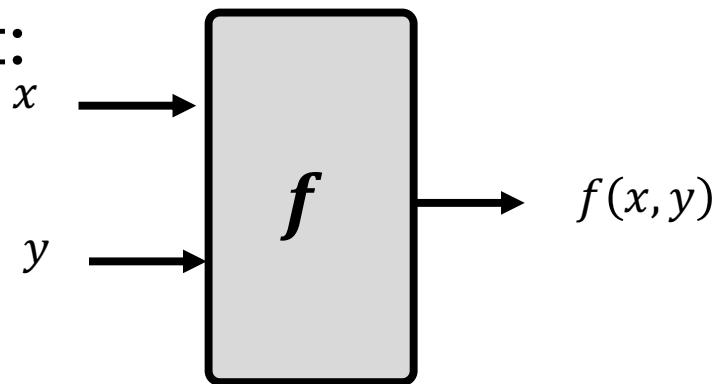

- How many possible 2-bit functions exist?


# 2-bit functions:

$$f(x, y)$$

$x$	$y$	$f(x, y)$
0	0	$f(0,0)$
0	1	$f(0,1)$
1	0	$f(1,0)$
1	1	$f(1,1)$

$2^4 = 16$  possible functions exist

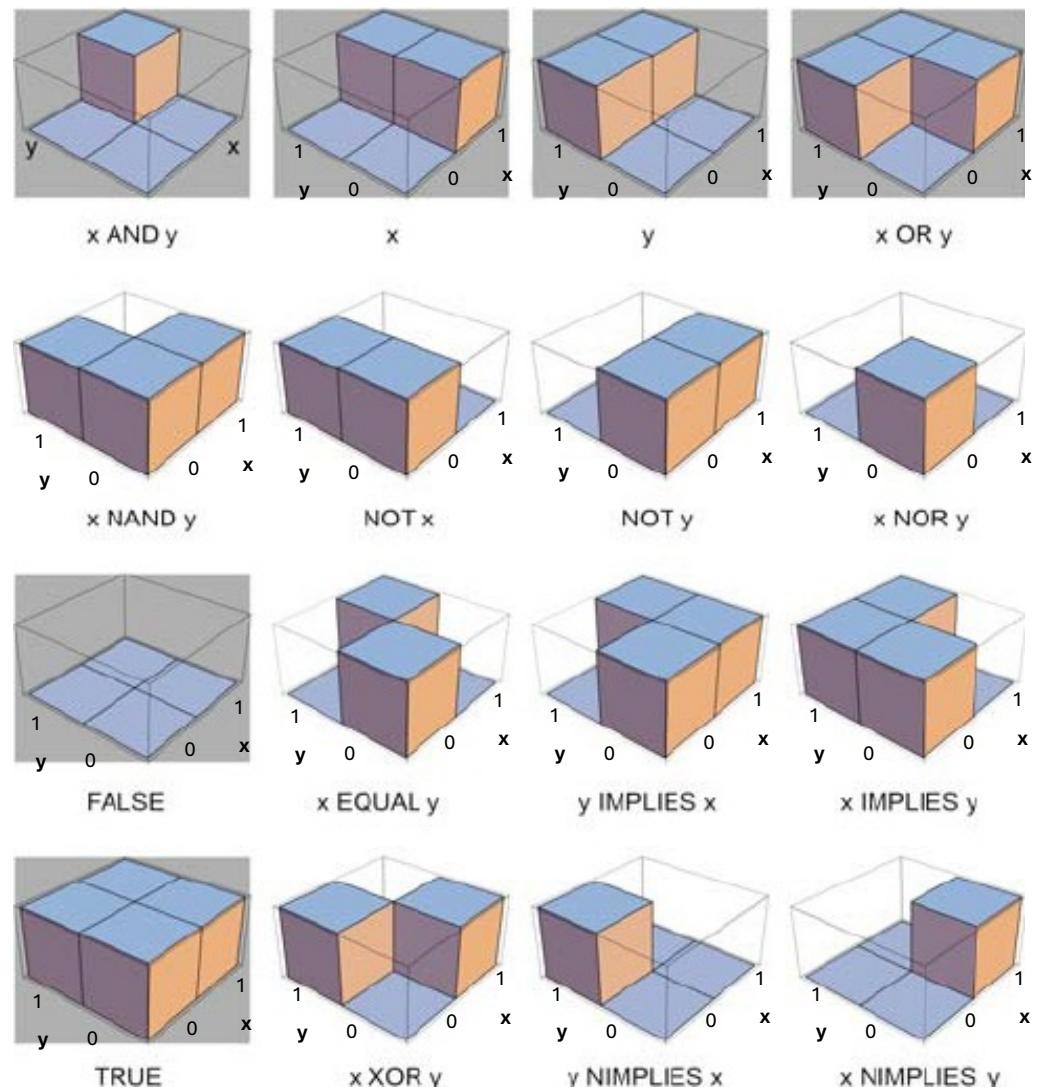Stated another way: there are 16 unique 1-0 combinations for:  
 $f(0,0)$ ,  $f(0,1)$ ,  $f(1,0)$ , and  $f(1,1)$



Mayo, Avi & Setty, Yaki & Shavit, Seagull & Zaslaver, Alon & Alon, Uri. (2006).

Plasticity of the cis-Regulatory Input Function of a Gene. PLoS biology. 4. e45. 10.1371/journal.pbio.0040045.

# Simple Truth Tables

- For a single-input system, there are four possible mappings (two non-negligible)
- For a two input system, you have 4 input combinations and 16 possible truth tables
- There is a lot of complexity that these give us

YES



INPUT	OUTPUT
A	
0	0
1	1

NOT



INPUT	OUTPUT
A	
0	1
1	0

AND



INPUT	OUTPUT	
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

OR



INPUT	OUTPUT	
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

XOR



INPUT	OUTPUT	
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

NAND



INPUT	OUTPUT	
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

NOR



INPUT	OUTPUT	
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

XNOR



INPUT	OUTPUT	
A	B	
0	0	1
1	0	0
0	1	0
1	1	1

Abels and Khisamutdinov, 2015,


[https://www.researchgate.net/publication/291418819\\_Nucleic\\_Acid\\_Computing\\_and\\_its\\_Potential\\_to\\_Transform\\_Silicon-Based\\_Technology](https://www.researchgate.net/publication/291418819_Nucleic_Acid_Computing_and_its_Potential_to_Transform_Silicon-Based_Technology)

# Logical Reduction

- All high level operations we may want can be reduced down to combinations of these simpler logical operations
- We just need to start to see how.
- Don't just think of the "AND" gate as "AND" in the quasi-grammar sense of the term. A lot of things we'd want to do when writing high-level logic/programs rely on it, even if we don't name it that explicitly.
- Same with "OR" or "XOR"
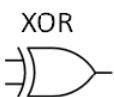
# Consider just one of these truth tables “XOR”

- If 0 and 1 are numbers, XOR performs base 2 addition:
  - $0+0=0$
  - $0+1=1$
  - $1+0=1$
  - $1+1=0$  (carry 1)
- Or, if 0 means positive and 1 means negative, XOR performs sign determination of multiplication:
  - $0 \times 0 = 0$  (positive  $\times$  positive = positive)
  - $0 \times 1 = 1$  (positive  $\times$  negative = negative)
  - $1 \times 0 = 1$  (negative  $\times$  positive = negative)
  - $1 \times 1 = 0$  (negative  $\times$  negative = positive)



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

# Or still thinking about ways of using XOR

- XOR expresses the if/else check:


if( $A==1$ ):

    output =  $\neg B$

else:

    output =  $B$

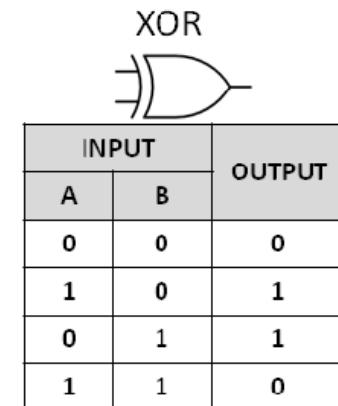- XOR it does the check:  $A \neq B$
- XOR does others
- All high-level algorithmic needs find their basic implementation in these fundamental functions



# But this is backwards...


- We usually have a thing we want to build and we need to figure out how to make it.
- We do not generally start with some random logic circuit and assign meaning to it like a piece of literature.

# Truth Tables and Sum of Product Expressions

- The most purest, truest, guaranteed way to represent digital functions is by either writing out their Truth Table or their Sum of Products (SOP)



INPUT		Y
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

 
$$Y = A \cdot B$$

*SOP is a OR-ing ("sum") of every non-zero row (product) in the truth table*

# Truth Tables and Sum of Product Expressions

- The most purest, truest, guaranteed way to represent digital functions is by either writing out their Truth Table or their Sum of Products (SOP)

INPUT		Y
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

$$Y = A \cdot \bar{B} + \bar{A} \cdot B$$

*SOP is a OR-ing ("sum") of every non-zero row (product) in the truth table*

# As an engineer you'd generally start with...

- Some sort of user-specified truth table.
- You could always use the resulting SOP as a recipe of what to build...
- BUT the SOP is very often NOT in the most simplified form.
- So your job would be to use the Boolean laws to reduce your equations (and therefore designs) down to the minimal number of gates to save costs (financial, time, emotional, etc...)

# So here's a truth table given to you by your boss



Build this:

INPUT		Y
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

Start with SOP and let's use Boolean Laws to get to the purest circuit form!!!

# More Complicated Circuit



Build a circuit with three inputs  $a, b, c$  and one output  $y$ .

$y$  should be high if  $a$  is on or if  $b$  is on with  $c$  off or if  $c$  is on or if  $b$  is off with  $a$  on.

# Boolean Algebra is Tricky

- **Karnaugh maps** can help us out here!
- A higher-dimensional representation of truth tables which can be used to graphically simplify Boolean Expressions

# Karnaugh Map


- Instead of doing truth table like this:

INPUT		Y
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

- Do like this:

Single box is full-term product


$$a\bar{b}$$

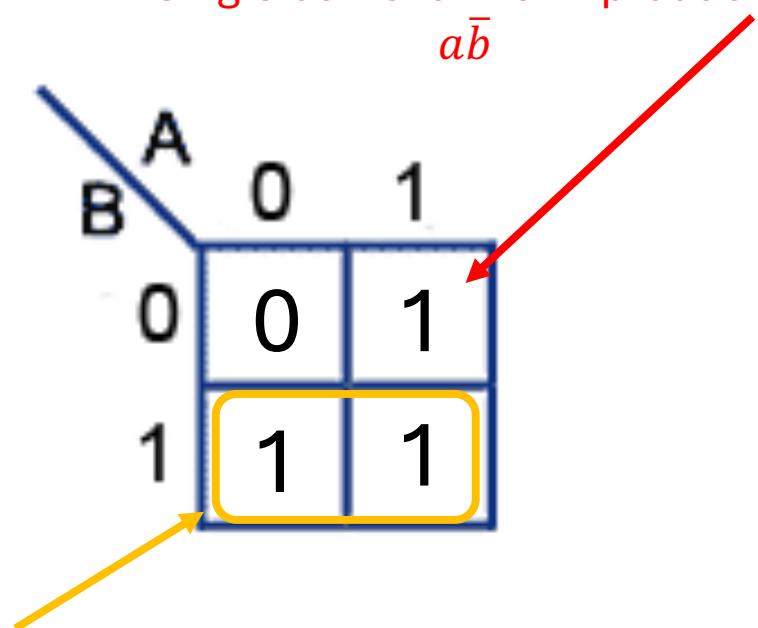


Larger continuous power-of-two rectangles are simplified terms... In this case this is  $b$
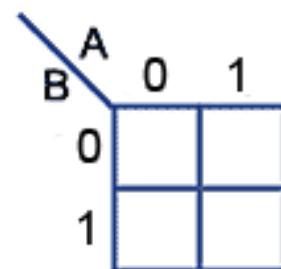
# For more inputs, can have larger K-maps


- Input sequences are broken up and listed out in Grey-code count
- Same idea. Circle the largest continuous power-of-two-rectangles until all 1's are covered on the board...that's your final SOP



(a)

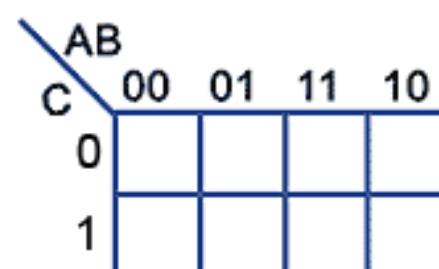

(b)

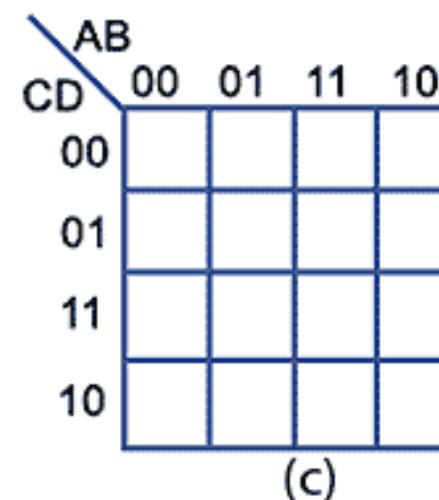

(c)

# OK...Complicating the More Complicated Circuit



Good job on designing the previous circuit. You get a bonus of 1600 dollars.\*

Unfortunately we are not splurging on three-input OR gates. All we have are 7400 chips which we buy in bulk. Build the circuit using just those.

You do that, we'll make your bonus 2400 dollars.\*\*

\*enough to buy a brand new Volkswagen Beetle in 1966

\*\*enough to buy a new base-model Ford Mustang in 1966.

# Remember De Morgan!!

## DeMorgan's Theorems

InstrumentationTools.com




# Gee that seems silly

- Yeah, but early on,
- In very very mission-critical things it was hard to rigorously quality-control lots of different specialized chips.
- The most mission-critical thing of all in the 1960s was the Apollo program

AGC

- The Apollo Guidance Computer was comprised only of three-input NOR gates

## The tri-NOR-gate “definition”:

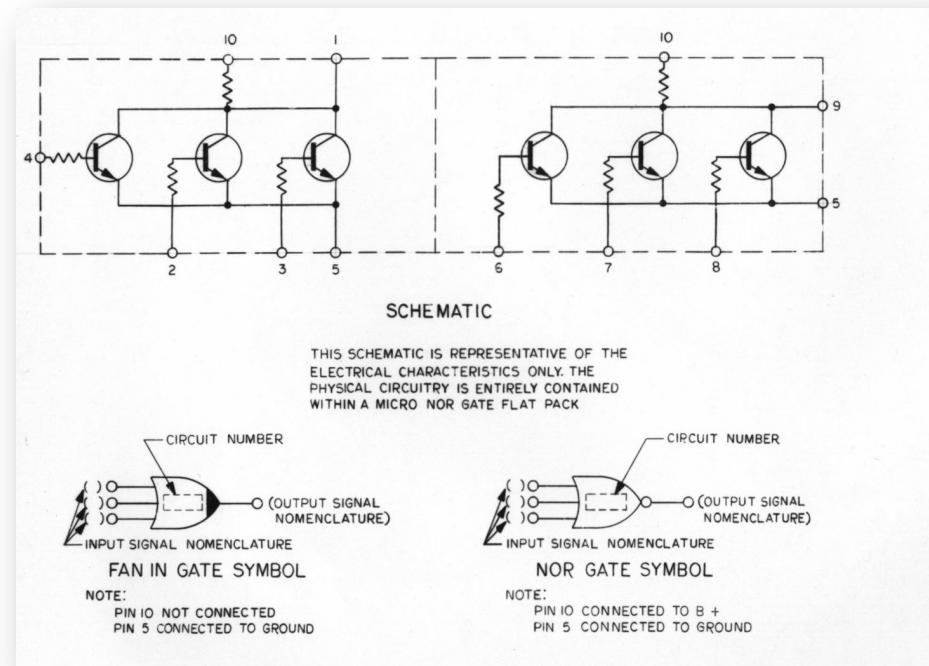


[https://klabs.org/history/ech/agc\\_schematics](https://klabs.org/history/ech/agc_schematics)

# AGC

Everything else is  
design ONLY using  
those NOR gates

Many pages of  
schematics

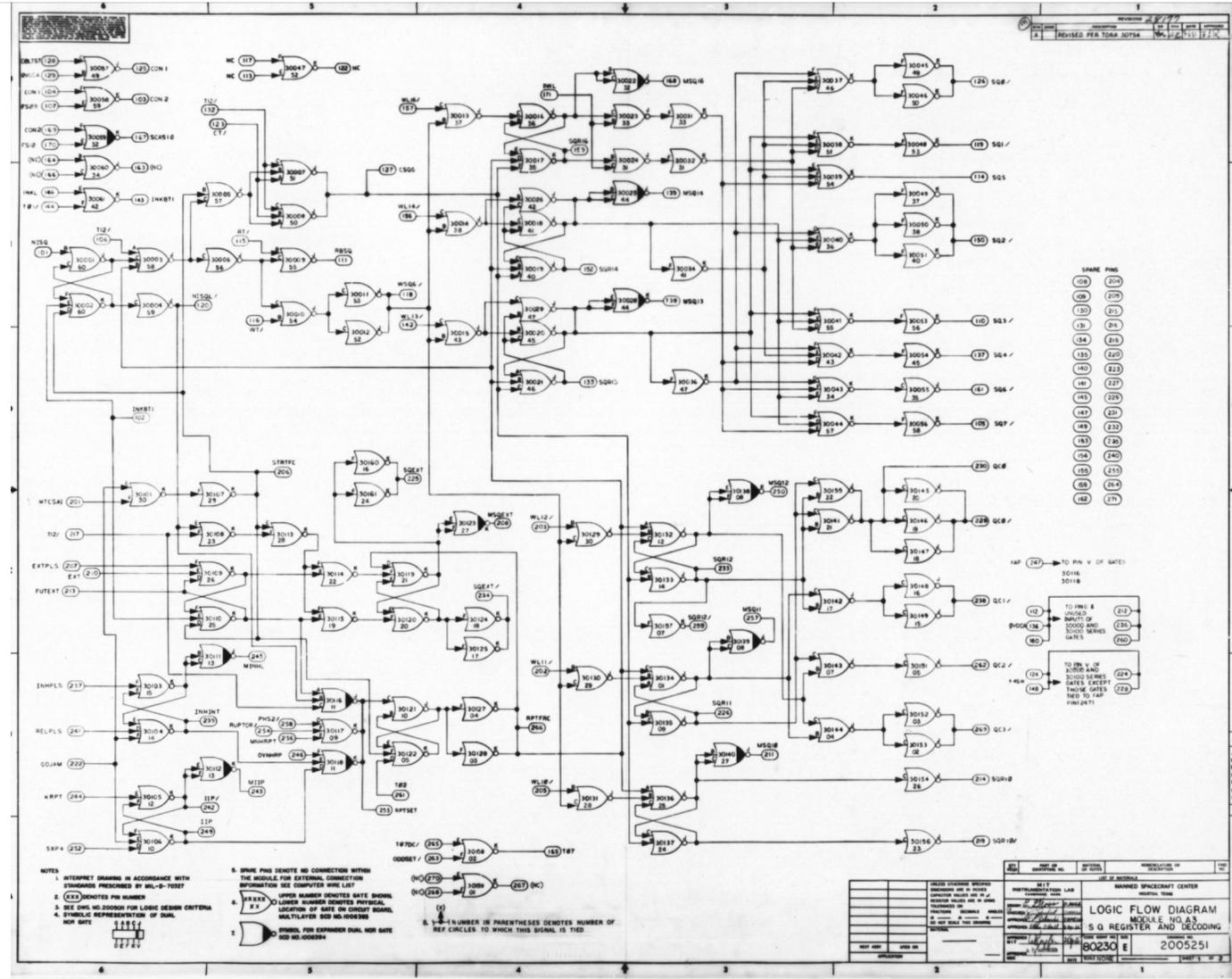


# Binary Numbers

- Each signal is 1 or 0...we can have multiple signals in parallel to represent combined higher level concepts.
- One of those can be numbers.


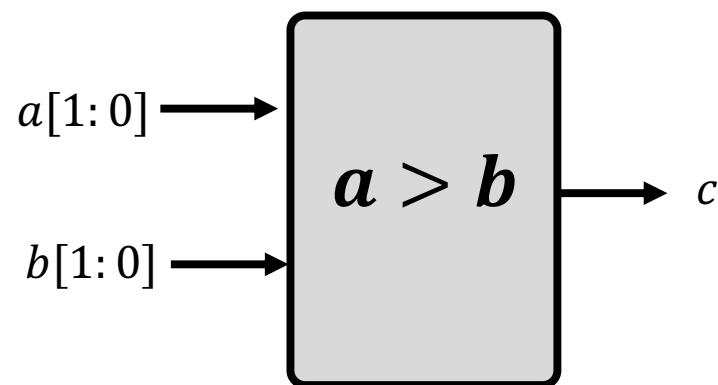
# Let's do the following

- “a” is a two bit number and “b” is a two bit number
- I want a circuit like the following:


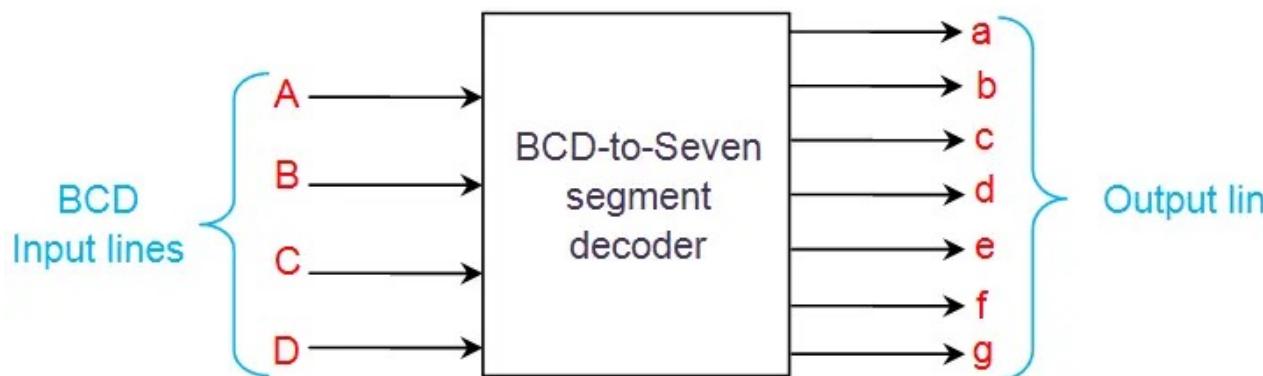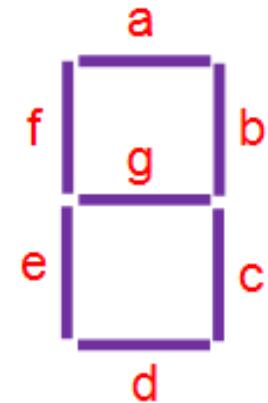
# Binary to Seven-Segment

- Four bits of binary...
- To sixteen symbols...(hexadecimal)
- I need to build this...



<https://blog.tindie.com/2022/03/chainable-seven-segment-display-module/>

<https://electronics.stackexchange.com/questions/351606/7-segment-binary-to-hex>

1/7/26

<https://www.electrical4u.com/bcd-to-seven-segment-decoder/>


6.S188 Eighties Clock

38

# Step 1...

- Derive Truth Table

Inputs				Segments							
A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	For display 0
0	0	0	1	0	1	1	0	0	0	0	For display 1
0	0	1	0	1	1	0	1	1	0	1	For display 2
0	0	1	1	1	1	1	1	0	0	1	For display 3
0	1	0	0	0	1	1	0	0	1	1	For display 4
0	1	0	1	1	0	1	1	0	1	1	For display 5
0	1	1	0	1	0	1	1	1	1	1	For display 6
0	1	1	1	1	1	0	0	0	0	0	For display 7
1	0	0	0	1	1	1	1	1	1	1	For display 8
1	0	0	1	0	1	1	1	0	1	1	For display 9
1	0	1	1	1	1	1	0	1	1	1	For display A
1	1	0	0	0	1	1	1	1	1	0	For display b
1	1	0	1	1	1	1	0	1	1	1	For display C
1	1	1	0	1	1	0	1	1	1	1	For display d
1	1	1	1	0	1	1	1	0	1	1	For display E
1	1	1	1	1	0	0	0	1	1	1	For display F

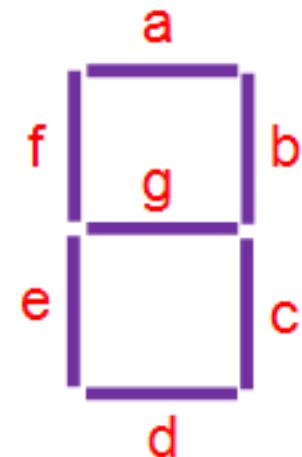


<https://www.electrical4u.com/bcd-to-seven-segment-decoder/>

<https://www.quora.com/Can-we-show-hexa-decimal-using-seven-segment-display>

# Let's do one of those segments...


- Segment a

Inputs				Segments							
A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	For display 0
0	0	0	1	0	1	1	0	0	0	0	For display 1
0	0	1	0	1	1	0	1	1	0	1	For display 2
0	0	1	1	1	1	1	0	0	0	1	For display 3
0	1	0	0	0	1	1	0	0	1	1	For display 4
0	1	0	1	1	0	1	1	0	1	1	For display 5
0	1	1	0	1	0	1	1	1	1	1	For display 6
0	1	1	1	1	0	1	1	1	1	1	For display 7
1	0	0	0	1	1	1	1	1	1	1	For display 8
1	0	0	1	1	1	1	0	1	1	1	For display 9
1	0	1	0	1	1	0	1	1	1	1	For display A
1	1	0	0	0	1	1	1	1	1	1	For display b
1	1	0	1	1	0	1	1	1	1	1	For display C
1	1	1	0	0	1	1	1	1	0	0	For display d
1	1	1	1	0	1	1	1	0	1	1	For display E
1	1	1	0	1	0	0	1	1	1	1	For display F
1	1	1	1	1	0	0	0	1	1	1	

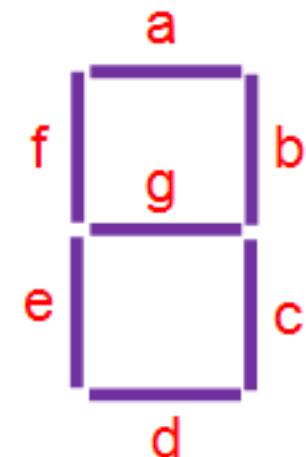
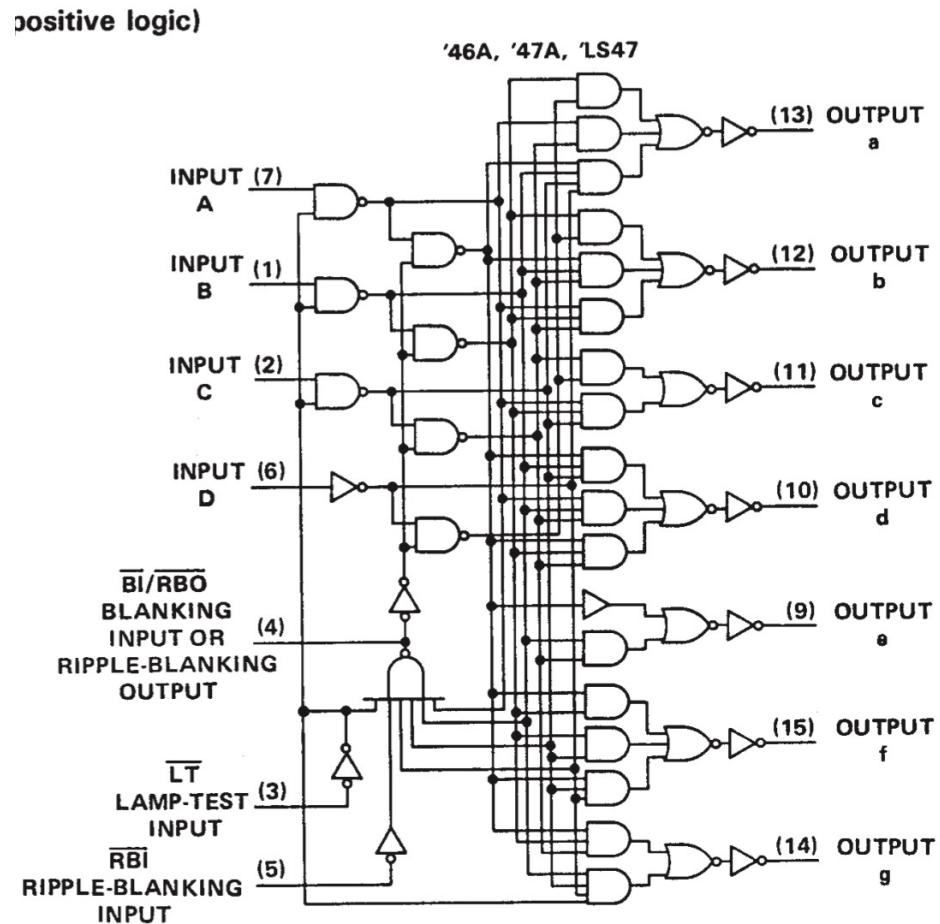
# The 7447

- Only does 0-9
- NOT 0-F
- Pack all this in a chip and make money
- TI was selling these nasty things for about 12 bucks a piece by late 1960s.



# Another Example (Multiplexer)

